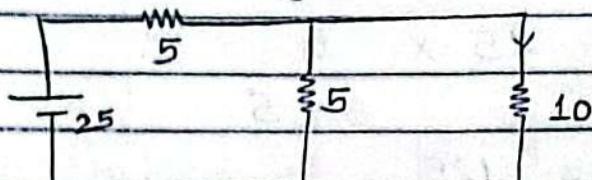


Thevenin's Theorem:



- ① Determine the current across 10Ω resistor using Thevenin's Theorem.



~~Sol:~~ Here,
load resistance (R_L) = 10Ω


Now, to find Thevenin's eq. resistance (R_{th}):

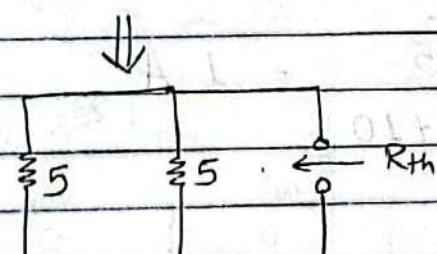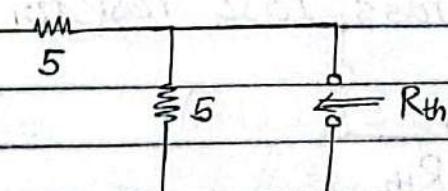The 10Ω resistor is open circuited and voltage source is made inactive as shown below:



$$R_{th} = 5//5 \\ = 2.5\Omega$$

Now, To determine eq. voltage (V_{th}):

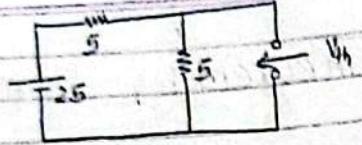


$$V_{th} = V_{5\Omega} = V \times \frac{R_1}{R_1 + R_2}$$

$$= 25 \times \frac{5}{5+5}$$

$$= \frac{125}{10}$$

$$= 12.5 \text{ Volt}$$

∴ Thevenin's Equivalent Circuit is :

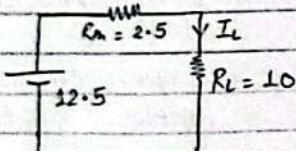


∴ current across 10Ω resistor :

$$I_L = \frac{V_{th}}{R_L + R_{th}}$$

$$= \frac{12.5}{2.5 + 10} = 1 \text{ A}$$

- ② Use Thevenin's Theorem to calculate current across 6Ω resistor.

P.T.O


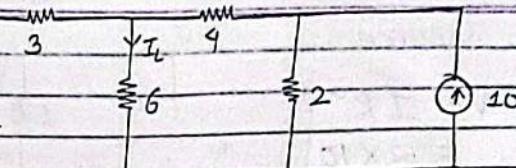


∴ :

Here,


$$R_L = 6\Omega$$

For R_{th} :

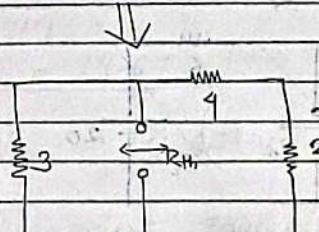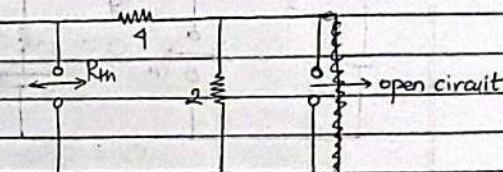

$$\begin{aligned} \therefore R_{th} &= (4+2) // 3 \\ &= 6 // 3 \\ &= 2 \Omega \end{aligned}$$

Now, for V_{th} :

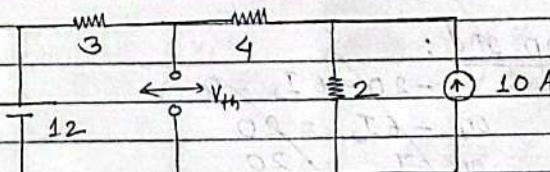


Converting the 10A current source into


voltage source

$$\therefore V = IR \\ = 2 \times 10 \\ = 20 \text{ V}$$

Now, ckt becomes:

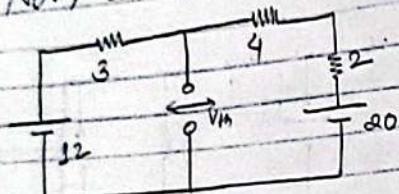

P.T.O.

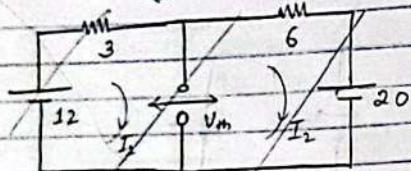

Applying KVL at:

loop 1st:

$$12 - 3I_1 = 0$$

$$\text{or, } 12 = 3I_1$$

$$\therefore I_1 = 4 \text{ A}$$


loop 2nd:

$$-20 - 6I_2 = 0$$

$$\text{or, } -6I_2 = 20$$

$$\text{or, } I_2 = \frac{20}{-6}$$

$$\therefore I_2 = -3.33 \text{ A}$$

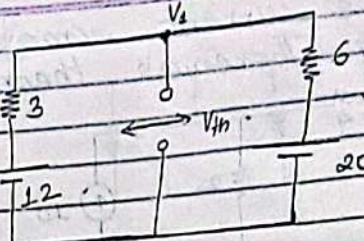

Applying nodal analysis at node 1:

$$\frac{V_1 - 12}{3} + \frac{V_1 - 20}{6} = 0$$


$$\text{or, } 2(V_1 - 12) + V_1 - 20 = 0$$

$$\text{or, } 3V_1 = 44$$

$$\therefore V_1 = 14.67 \text{ V}$$

$$\therefore V_1 = V_{th} = 14.67 \text{ V}$$


Now, Thvenin's equivalent circuit is:

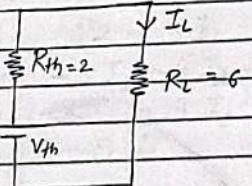


$$\therefore I_L = \frac{V_{th}}{R_L + R_{th}} = \frac{14.67}{6 + 2} \\ = 1.83 \text{ A}$$

(3) Determine the current across 4Ω resistor using Thévenin's theorem.

[Ques 11]
(Smarks)

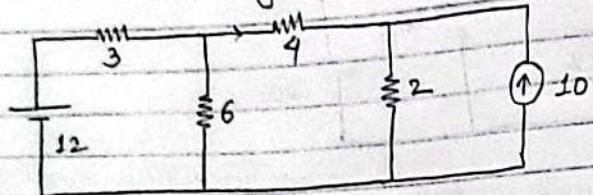


~~Sol:~~ Here,
 $R_L = 4\Omega$

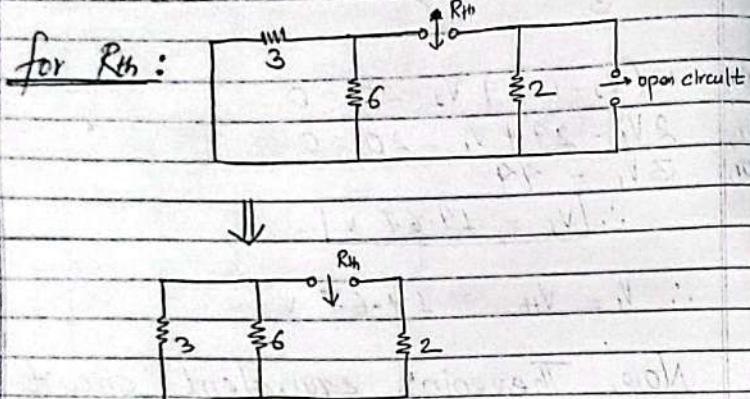


$$R_{th} = \frac{3}{3+6} = \frac{3 \times 6}{3+6} = 2 \Omega$$

\therefore ckt becomes:

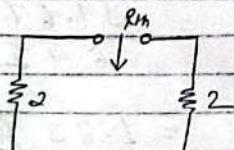

$$\therefore R_{th} = 2 + 2 = 4 \Omega$$


For V_{th} :

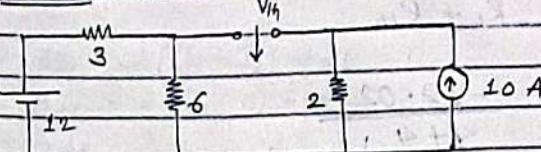

Converting 10A current source into voltage source.

$$\begin{aligned} V &= IR \\ &= 10 \times 2 \\ &= 20 \text{ V} \end{aligned}$$

\therefore ckt becomes:

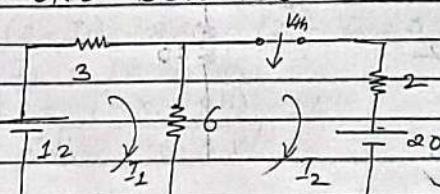

Applying loop analysis. at:

$$\begin{aligned} \text{loop 1st: } & 12 - 3I_1 - 6(I_1 - I_2) = 0 \\ \text{or, } & -3I_1 - 6I_1 + 6I_2 = -12 \\ \text{or, } & -9I_1 + 6 \times 0 = -12 \\ \text{or, } & -9I_1 = -12 \end{aligned}$$

$$\therefore I_1 = 1.33 \text{ A}$$

$$\begin{aligned} \text{loop 2nd: } & -6(I_2 - I_1) - V_{th} - 2I_2 - 20 = 0 \\ \text{or, } & -6I_2 + 6I_1 - V_{th} - 2I_2 = 20 \\ \text{or, } & (-6) \times 0 + 6 \times 1.33 - V_{th} - 2 \times 0 = 20 \\ \text{or, } & 7.98 - V_{th} = 20 \end{aligned}$$


$$\therefore V_{th} = -12.02 \text{ V}$$

$$\therefore I_L = \frac{V_{th}}{R_L + R_{th}}$$

$$= \frac{-12.02}{4+4}$$

$$= -1.5 \text{ A}$$

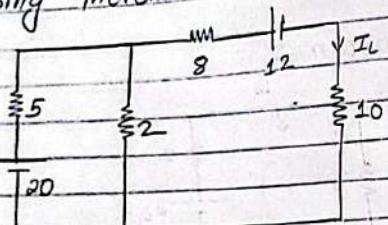
(4) Determine current across 10Ω resistor using Thévenin's theorem.



Soln: Here,


$$R_L = 10\Omega$$

For R_{th} :

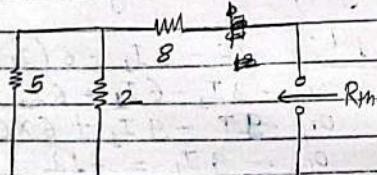

$$R_{th} = \left(\frac{5}{10} \right) + 8 = 9.42 \Omega$$

For V_{th} :

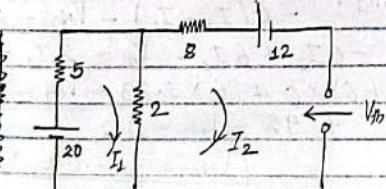

Applying KVL in loop 1st:

$$-5I_1 - 2(I_1 - I_2) + 20 = 0$$

$$-5I_1 - 2(I_1 - 0) = -20$$

$$-5I_1 - 2I_1 = -20$$

$$-7I_1 = -20$$

$$I_1 = -20$$

$$-7$$

$$\therefore I_1 = 2.85 \text{ A}$$

Applying KVL in loop 2nd:

$$-2(I_2 - I_1) - 8I_2 - 12 - V_{th} = 0$$


$$-2(0 - I_1) - 8 \times 0 - 12 - V_{th} = 0$$

$$-2I_1 - 12 = V_{th}$$

$$V_{th} = (2 \times 2.85) - 12$$

$$\therefore V_{th} = -6.3 \text{ V}$$

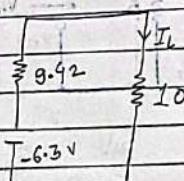
Now, $I_{L_{eq}}$ ~~is~~
Thevenin's equivalent circuit is:



$$\therefore I_L = \frac{V_m}{R_L + R_{th}} = \frac{20 - 6.3}{10 + 9.42}$$

$$= -0.32 \text{ A}$$

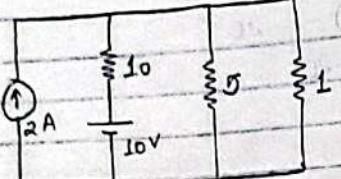
5) Find power loss in 1Ω resistor using Thévenin's Theorem.



Soln:


$$R_L = 1\Omega$$

for R_{th} :

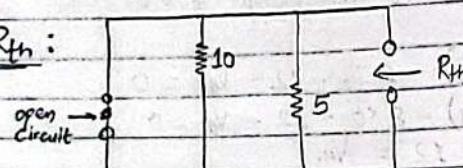

$$\therefore R_{th} = 10//5 \\ = 3.34 \Omega$$

for V_{th} :

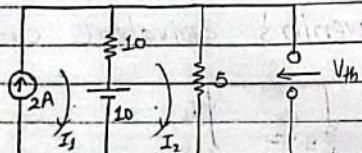

$$V_{th} = 5V$$

Now,

Using mesh analysis at loop 1st:

$$I_1 = 2A$$

Using mesh analysis at loop 2nd:

$$10 - 10(I_2 - I_1) - 5I_2 = 0$$

$$\text{or, } -10I_2 + 10I_1 - 5I_2 = -10 \\ \text{or, } 10I_1 - 15I_2 = -10 \\ \text{or, } 2I_1 - 3I_2 = -2$$

$$\text{or, } 2I_1 - 3I_2 = -2 \quad (\because I_1 = 2)$$

$$\text{or, } 2 \times 2 - 3I_2 = -2$$


$$\text{or, } -3I_2 = -2 - 4$$

$$\text{or, } I_2 = -6$$

$$\therefore I_2 = 2$$

$$\therefore V_{th} = V_{5\Omega} \\ = I_2 \times R \\ = 2 \times 5 \\ = 10V$$

Now, Thévenin's Eq. theorem:

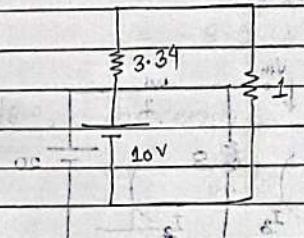


$$\therefore I_L = \frac{V_{th}}{R_L + R_{th}} = \frac{10}{3.34 + 1} = 2.3A$$

$$\therefore \text{power in } 1\Omega = (I_L)^2 \times R$$

$$= (2.3)^2 \times 1 \\ = 5.3 \text{ watt}$$

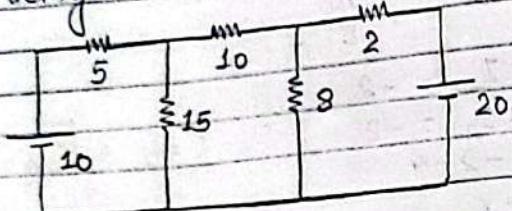
⑥ Determine current across 10Ω resistor using Thevenin's Theorem.



Sol:

$$R_L = 10\Omega$$


For R_{th} :

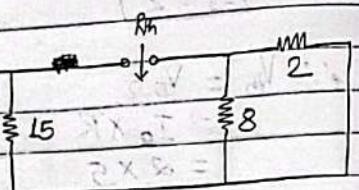

$$\therefore R_{th} = (5//15) + (8//2)$$

$$= 3.75 + 1.6$$

$$= 5.35 \Omega$$

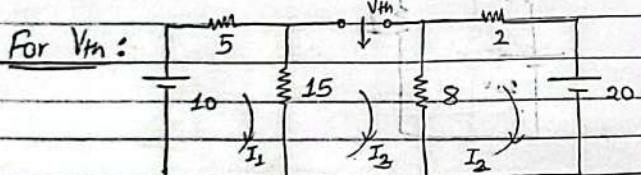

Applying mesh analysis at:

$$\text{loop } i: 10 - 5I_1 - 15(I_1 - I_3) = 0$$

$$\text{or, } -5I_1 - 15I_1 + 15I_3 = -10$$

$$\text{or, } -20I_1 + 15I_3 = -10$$

$$\text{or, } -5(4I_1 - 3I_3) = -10$$

$$\text{or, } 4I_1 - 3I_3 = 2 \longrightarrow ①$$

$$\text{or, } 4I_1 - 3 \times 0 = 2$$

$$\text{or, } I_1 = 2/4 \quad \therefore I_1 = 0.5A$$


$$\begin{aligned} \text{loop } ii: & -15(I_3 - I_1) - V_{th} - 8(I_3 - I_2) = 0 \\ \text{or, } & -15I_3 + 15I_1 - V_{th} - 8I_3 + 8I_2 = 0 \\ \text{or, } & 15I_1 - 23I_3 + 8I_2 = V_{th} \\ \text{or, } & 15I_1 + 8I_2 - 23I_3 = V_{th} \\ \text{or, } & 15 \times 0.5 + 8I_2 - 23 \times 0 = V_{th} \\ \text{or, } & 7.5 + 8I_2 = V_{th} \\ \text{or, } & V_{th} = 7.5 + 8I_2 \end{aligned}$$

$$\begin{aligned} \text{loop } iii: & -20 - 8(I_2 - I_3) - 2I_2 = 0 \\ \text{or, } & -20 - 8(I_2 - 0) - 2I_2 = 0 \\ \text{or, } & -8I_2 - 2I_2 = 20 \\ \text{or, } & -10I_2 = 20 \\ \therefore & I_2 = -2A \end{aligned}$$

Now, from eqn ① :

$$\begin{aligned} V_{th} &= 7.5 + 8 \times (-2) \\ &= 7.5 - 16 \\ &= -8.5V \end{aligned}$$

Now, Thvenin's Eq. ckt is:

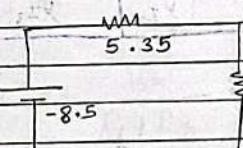

$$0 = (5.35 - 8.5)V_{th} - 10I_2 - 8.5$$

$$R_L + R_{th} = 10 + 5.35$$


$$0.5 = 15.35A - 10$$

$$A = -0.55A$$

$$0 = (5 - 2)8 - 10V - (5 - 2)2A - 10$$

$$0 = (3 - 2)8 - 10V - (3 - 2)2A - 10$$

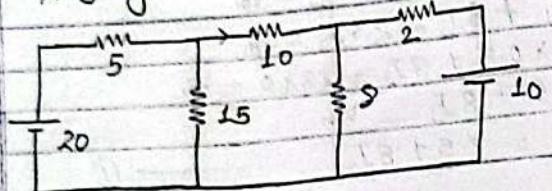
(7) Calculate the current in 10Ω resistor applying Thvenin's Theorem.



Soln: Here,


$$R_L = 10\Omega$$

For R_{Th} :

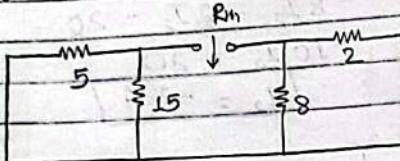

$$\begin{aligned} \therefore R_{Th} &= (5//15) + (8//2) \\ &= 3.75 + 1.6 \\ &= 5.35 \Omega \end{aligned}$$

For V_{Th} :

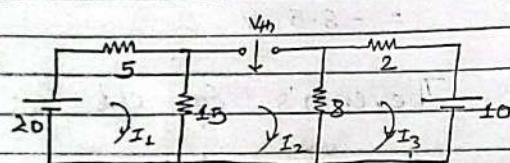

Applying KVL at:

$$\text{loop 1st: } 20 - 5I_1 - 15(I_1 - I_2) = 0$$

$$\text{or, } -5I_1 - 15(I_1 - 0) = -20$$

$$\text{or, } -5I_1 - 15I_1 = -20$$

$$\text{or, } -20I_1 = -20$$

$$\therefore I_1 = 1A$$

$$\text{loop 2nd: } -15(I_2 - I_1) - V_{Th} - 8(I_2 - I_3) = 0$$

$$\text{or, } -15(0 - I_1) - V_{Th} - 8(0 - I_3) = 0$$

$$\text{or, } 15I_1 - V_{Th} + 8I_3 = 0$$

$$\text{or, } 15 \times 1 - V_{Th} + 8I_3 = 0$$

$$\text{or, } 15 + 8I_3 = V_{Th}$$

$$\therefore V_{Th} = 15 + 8I_3$$

(1)

$$\text{loop 3rd: } -10 - 8(I_3 - I_2) - 2I_3 = 0$$

$$\text{or, } -8(I_3 - 0) - 2I_3 = 10$$

$$\text{or, } -8I_3 - 2I_3 = 10$$

$$\text{or, } -10I_3 = 10$$

$$\boxed{I_3 = -1A}$$


\therefore Eqn (1) becomes:

$$V_{Th} = 15 + 8 \times (-1)$$

$$= 15 - 8$$

$$\therefore V_{Th} = 7V$$

Now, Thvenin's Eq. ckt is:

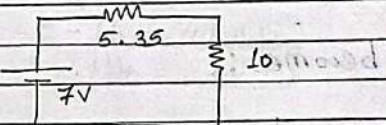


$$\therefore I_L = \frac{V_{Th}}{R_L + R_{Th}} = \frac{7}{10 + 5.35}$$

$$= 0.45 A$$


(8) Apply Thvenin's theorem to find the current flowing through 10Ω resistor.

P.T.O

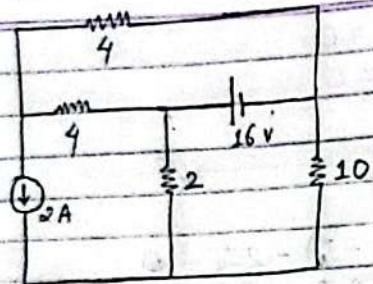

Sol: Here,
 $R_L = 10 \Omega$


for R_{th} :

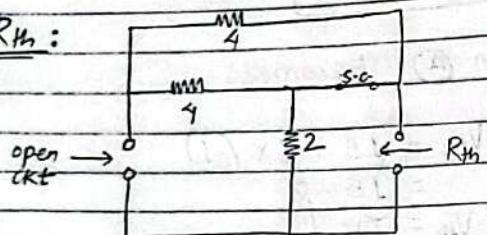


Since, 4Ω & 4Ω are in series then,

$$\text{Req} = 4 + 4 \\ = 8 \Omega$$

New, ckt becomes:

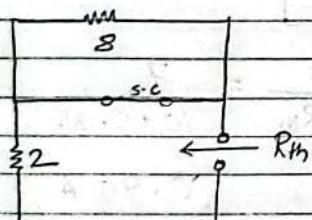


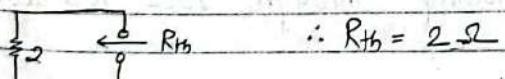∴ Resistor parallel to short circuit is zero,
then ckt becomes:



$\therefore R_{th} = 2 \Omega$

for V_{th} :

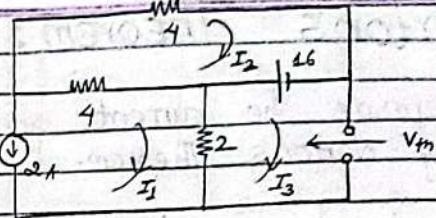

Applying KVL at :

loop 1st: $I_1 = -2 A$

loop 2nd: $-4(I_2 - I_1) - 4I_2 + 16 = 0$

or, $-4(I_2 + 2) - 4I_2 + 16 = 0$

or, $-4I_2 - 8 - 4I_2 = -16$

or, $-8I_2 = -16 + 8$

or, $-8I_2 = -8$

$\therefore I_2 = 1 A$


loop 3rd: $-2(I_3 - I_1) - 16 - V_{th} = 0$

or, $-2(0 + 2) - 16 - V_{th} = 0$

or, $-4 - 16 - V_{th} = 0$

$\therefore V_{th} = -20 V$

Now, Thévenin's Eq. circuit is:

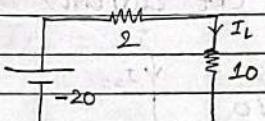

$$\therefore I_L = \frac{V_{th}}{R_L + R_{th}} = \frac{-20}{2 + 10} = -1.67 A$$


I_{sc} is equal to the current flowing through the branch placed across the terminals & it is zero when viewed from there. Open terminals have the same resistance as the source or make them zero. Extra voltage & current sources are removed or made zero.

PAGE DATE

PAGE DATE

Norton's Theorem:

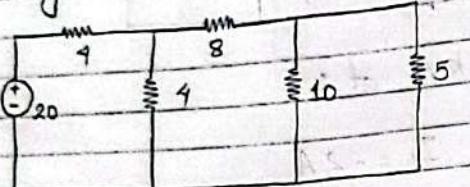
- ① Determine the current across 5Ω resistor using Norton's Theorem.



∴ Here,


$$R_L = 5\Omega$$

For R_o : (open ckt eq. resistance)

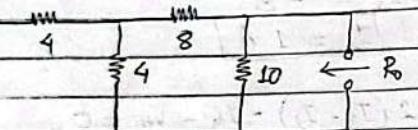


$$\therefore R_o = [(4||4) + 8] \leftrightarrow 10 = 5\Omega$$

For I_{sc} : (short ckt current)

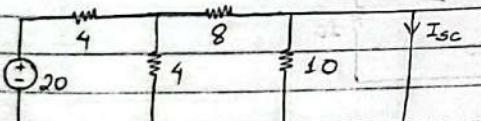

Since, 10Ω becomes zero due to parallel to short circuit.

Now, ckt becomes:

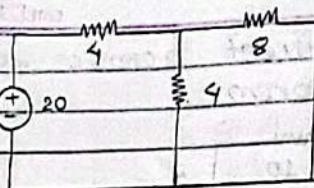


$$\therefore R_{eq} = (8||4) + 4 = 6.67\Omega$$

$$\therefore I = \frac{20}{6.67} = 3A$$

Since, $I_{sc} =$ Current across 8Ω resistor (I_{sc})

$$\therefore I_{sc} = 3 \times \frac{4}{8+4} = 1A$$

Now, Norton's eq. ckt is:

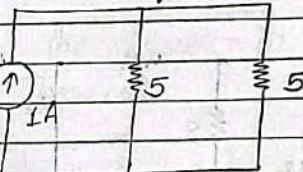


$$\therefore I_L = I \times \frac{R_2}{R_1+R_2}$$


$$= 1 \times \frac{5}{5+5}$$

$$= 0.5A$$

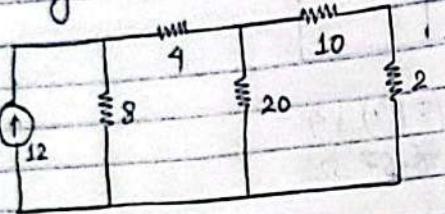
② Determine the current across 20Ω resistor using Norton's Theorem.



Soln: Here,
 $R_L = 20\Omega$

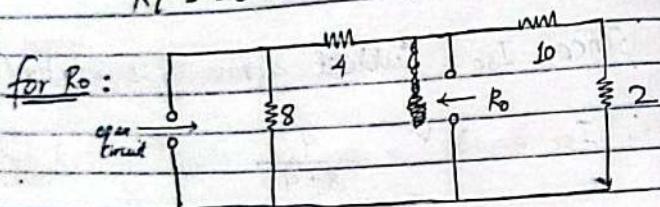

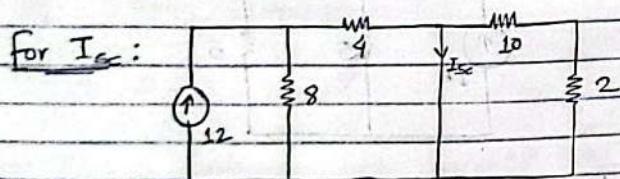
$$\begin{aligned}\therefore R_o &= \cancel{(8+4)} + (8+4) \parallel (10+2) \\ &= 12 \parallel 12 \\ &= 6\Omega\end{aligned}$$




Since, 10Ω & 2Ω becomes zero due to parallel to short circuit.

Then, ckt becomes:

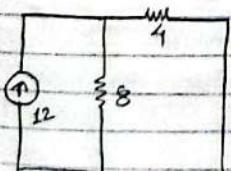


$$\begin{aligned}\therefore I_{eq} &= I_{4\Omega} = \frac{12}{8+4} \times 8 \\ &= 8A\end{aligned}$$

Now, Norton's Eq. ckt :

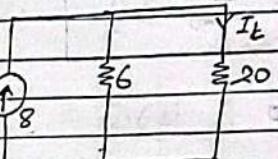


$$\begin{aligned}\therefore I_L &= \frac{I \times R_2}{R_1 + R_2} \\ &= \frac{8 \times 6}{6+20} \\ &= 1.85A\end{aligned}$$

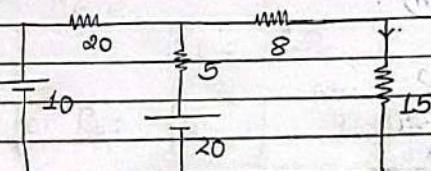③ Determine the power in 15Ω resistor using Norton's Theorem.



Soln: Here,
 $R_L = 15\Omega$

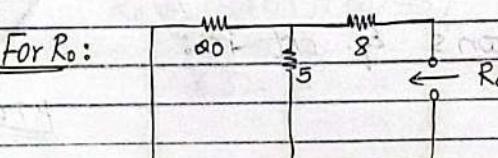


PAGE DATE

$$R_o = (20//5) + 8$$

$$= 12 \Omega$$

for I_{sc} :

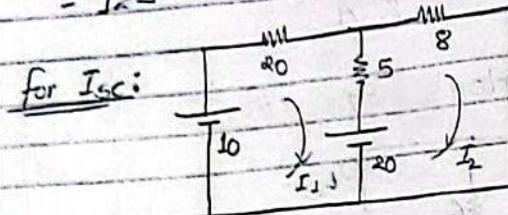

Applying KVL at:

loop 1st: $10 - 20I_1 - 5(I_1 - I_2) - 20 = 0$

or, $-20I_1 - 5I_1 + 5I_2 = 20 - 10$

or, $-25I_1 + 5I_2 = 10$

or, $-5(5I_1 - 8I_2) = 10$

or, $5I_1 - I_2 = -2 \rightarrow (i)$

loop 2nd: $20 - 15I_2 - 8I_1 = 0$

or, $-5(I_2 - I_1) - 8I_1 + 20 = 0$

or, $-5I_2 + 5I_1 - 8I_1 = -20$

or, $5I_1 - 13I_2 = -20 \rightarrow (ii)$

Solving (i) & (ii):

$$5I_1 - I_2 = -2$$

$$5I_1 - 13I_2 = -20$$


$$- + +$$

$$12I_2 = 18$$

$$\therefore I_2 = 1.5 \text{ A}$$

Now, Norton's Eq. ckt is:

P.T.O

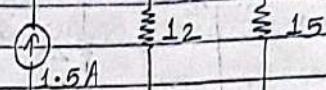

$$\therefore I_L = 1.5 \times \frac{12}{12+15}$$


$$= 0.65 \text{ A}$$

$$\therefore P_{loss} = (0.65)^2 \times 15$$


$$= 6.33 \text{ watt}$$

(4) Determine the current across 6Ω resistor in the given circuit:

2006
(8 marks)

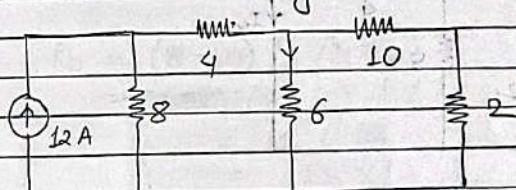

Here, $R_L = 6 \Omega$


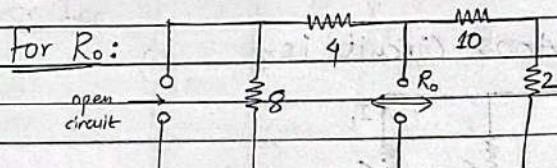


$$\therefore R_o = (8+9) // (10+2)$$


$$= 12 // 12$$

$$= 6 \Omega$$

For I_{sc} :

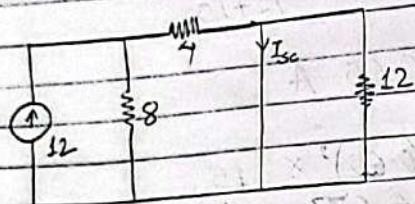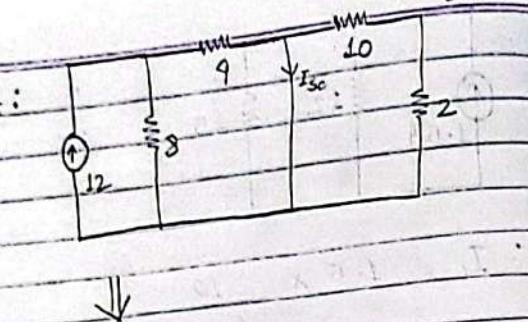


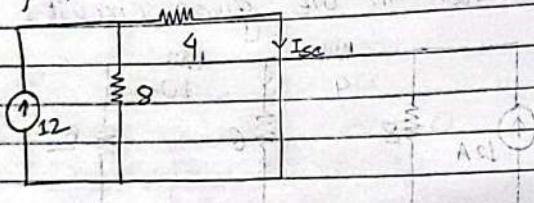∴ 12Ω resistor is parallel to short circuit, so it is zero. Therefore, ckt becomes:



$$\therefore I_{sc} = I_{4\Omega} = \frac{12}{4+8} = 8A$$


Now, Norton's circuit is:

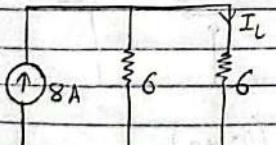

$$\therefore I_L = \frac{8 \times 6}{6+6} = 4A$$

- 5) Determine the power in 6Ω resistor in the given circuit using Norton's Theorem.

(2007
8 marks)

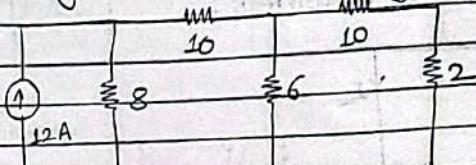


Soln:

Here,


$$R_i = 6\Omega$$

For R_o :

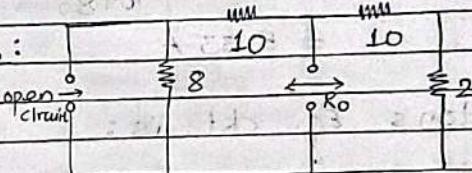


$$\begin{aligned} R_o &= (8+10) // (10+2) \\ &= (8+10) // 12 \\ &= 18 // 12 \\ &= 18 \times 12 / 18 + 12 \\ &= 7.2 \Omega \end{aligned}$$


For I_{sc} :

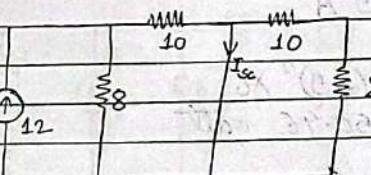

soln:

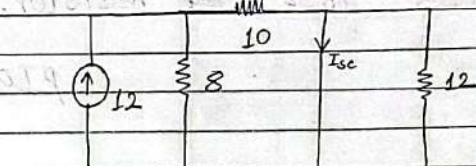


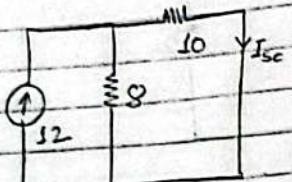PAGE DATE
 ∵ Short circuit & 12Ω resistor are parallel
 & it is zero.
 Then, ckt becomes:



$$\therefore I_{sc} = I_{10A} = \frac{12 \times 8}{10+8} = 5.33 A$$

Now, Norton's Eq. ckt is:

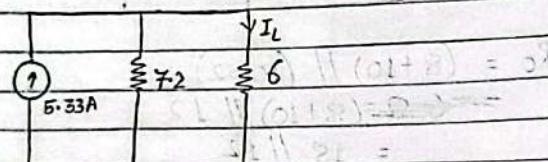


$$\therefore I_L = \frac{5.33 \times 7.2}{7.2+6} = 2.9 A$$

$$\therefore P_{6\Omega} = (2.9)^2 \times 6 = 50.46 \text{ watt}$$

- ⑥ Using Norton's theorem, calculate the voltage across 16Ω resistor.



(2008)
 (Spring)
 3 marks

P.T.O

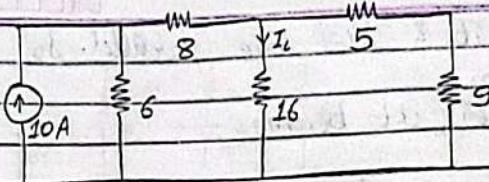



Q6(b): Here,

$$R_L = 16\Omega$$

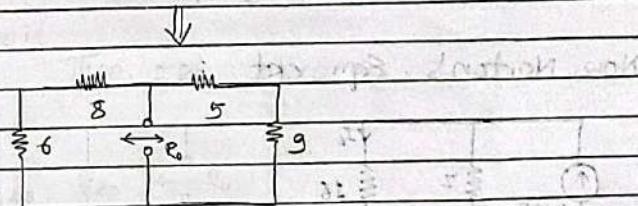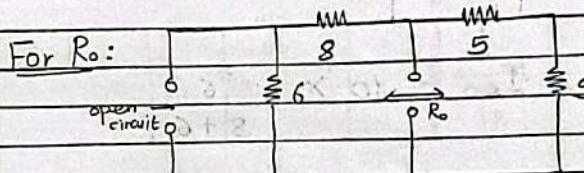


$$\therefore R_0 = (6+8) // (5+9) = 14 // 14 = 7\Omega$$

Now, For I_{sc} :

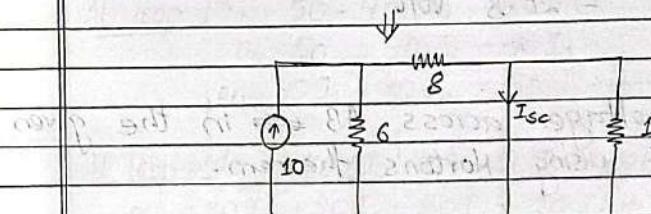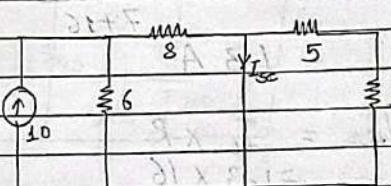

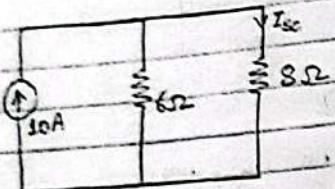
∴ Short circuit & 14Ω are parallel. So 14Ω becomes zero.
Then, ckt becomes:



$$\therefore I_{sc} = I_{8\Omega} = 10 \times \frac{6}{8+6}$$

$$= 4.28 \text{ A}$$

Now, Norton's Eq. ckt is:

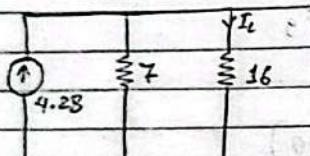

$$\therefore I_L = 4.28 \times \frac{7}{7+16}$$


$$= 1.3 \text{ A}$$

$$\therefore V_{16\Omega} = I_L \times R$$

$$= 1.3 \times 16$$


$$= 20.8 \text{ volt}$$

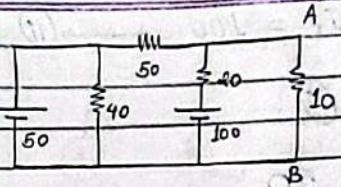- ⑦ find voltage across AB in the given circuit using Norton's theorem.




(Q3): Here,

$$R_L = 10\Omega$$

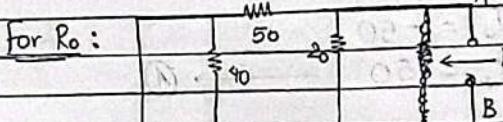


∴ 40Ω becomes zero due to parallel to short circuit.

Then, ckt becomes:

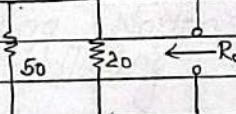
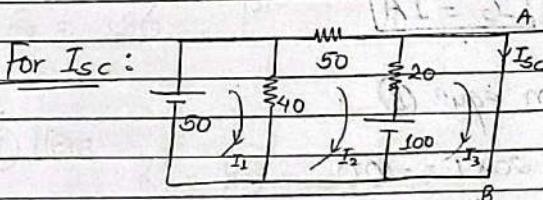
$$\therefore R_0 = 20//50 = 14.28\Omega$$



At loop 1st: $50 - 40(I_1 - I_2) = 0$

or, $50 = 40I_1 - 40I_2$

or, $40I_1 - 40I_2 = 50 \quad \rightarrow (1)$

At loop 2nd: $-40(I_2 - I_1) - 50I_2 - 20(I_2 - I_3) - 100 = 0$

or, $-40I_2 + 40I_1 - 50I_2 - 20I_2 + 20I_3 = 100$

or, $40I_1 - 110I_2 + 20I_3 = 100 \rightarrow (ii)$

Solving eqn (i) & (ii):

$$40I_1 - 40I_2 = 50$$

$$20I_3 + 40I_1 - 110I_2 = 100$$

$$-20I_3 + 70I_2 = -50$$

or, $20I_3 - 70I_2 = 50 \rightarrow (A)$

At loop 3rd: $100 - 20(I_3 - I_2) = 0$

$$\text{or, } 100 - 20I_3 + 20I_2 = 0$$

$$\text{or, } -20I_3 + 20I_2 = -100 \rightarrow (B)$$

Solving eqn (A) & (B)

$$80I_3 - 70I_2 = 50$$

$$-20I_3 + 20I_2 = -100$$

$$-50I_3 = -50$$

$$\therefore I_3 = 1A$$

Now, from eqn (B):

$$-20I_3 + 20 \times 1 = -100$$


$$\text{or, } -20I_3 = -100 - 20$$

$$\text{or, } -20I_3 = -120$$

$$\therefore I_3 = 6A$$

$$\therefore I_{sc} = 6A$$

Note, Norton's Eq. ckt is:

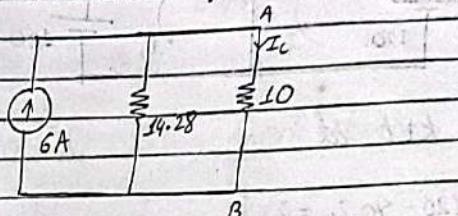


$$I_L = 6 \times \frac{14.28}{10 + 14.28} = 3.52 A$$

∴ Voltage across 10Ω is:


$$V_{10\Omega} = 3.52 \times 10 \\ = 35.2 \text{ Volt}$$

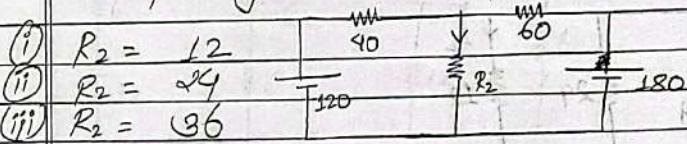(B) Using Norton's theorem, find current flowing in R_2 when




Given:

(i) Here, $R_L = R_2 = 12 \Omega$

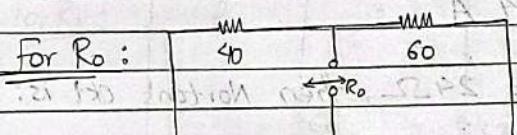

$$R_o = 60 / 40 = 15 \Omega$$

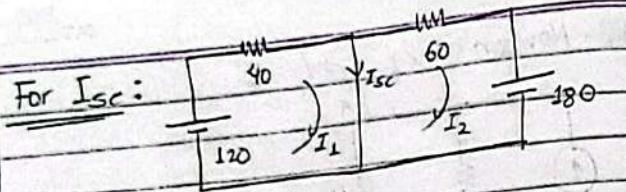


Applying KVL at:

$$\begin{aligned} \text{loop 1st: } & 120 - 40I_1 = 0 \\ \text{or, } & 120 = I_1 \\ & 120 \\ \therefore & I_1 = 3A \end{aligned}$$

$$\begin{aligned} \text{loop 2nd: } & -60I_2 - 180 = 0 \\ \text{or, } & -180 = 60I_2 \\ \therefore & I_2 = -3A \end{aligned}$$


$$\therefore I_{sc} = I_1 - I_2 = 3 - (-3) = 6A$$

Now, Norton's eq. ckt is:

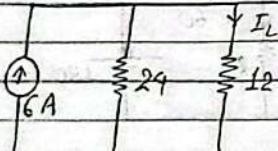


$$\begin{aligned} \therefore I_1 &= 6 \times \frac{24}{12+24} \\ &= 4A \end{aligned}$$

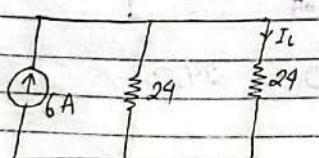(ii) When $R_L = 24\Omega$, then Norton's ckt is:




$$\begin{aligned} \therefore I_L &= 6 \times \frac{24}{24+24} \\ &= 3A \end{aligned}$$

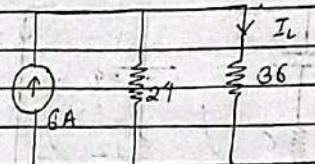(iii) When $R_L = 36\Omega$, then Norton's eq. ckt is:




$$\therefore I_1 = 6 \times \frac{24}{24+36} = 2.4A$$

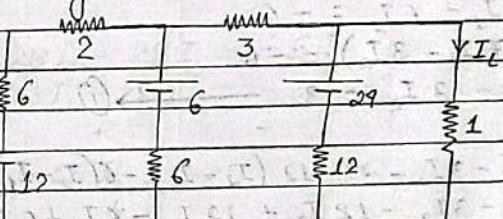③ Determine current across 1Ω resistor using Norton's Theorem in the given ckt.



Ans: Here,

$$R_L = 1\Omega$$

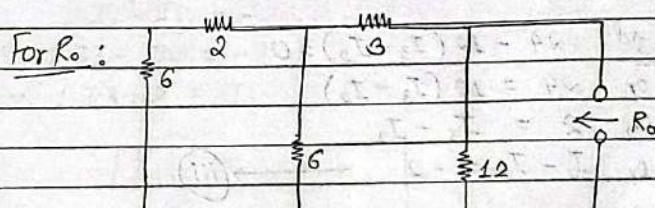


$$\therefore R_o = [(6+2)\parallel 6 + 3]\parallel 12$$

$$= [(8 \parallel 6) + 3] \parallel 12$$

$$= (3 \cdot 9.2 + 3) \parallel 12$$

$$= 6.42 \parallel 12 = 4.18 \Omega$$

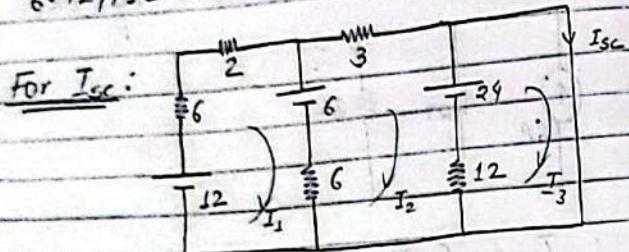

Applying KVL at:

$$\text{Loop 1st: } 12 - 6I_1 - 2I_2 - 6(I_1 - I_2) - 6 = 0$$

$$\text{or, } -8I_1 - 6I_2 + 6I_1 = -12 + 6$$

$$\text{or, } -2I_1 - 6I_2 = -6$$

$$\text{or, } -2(7I_1 - 3I_2) = -6$$

$$\text{or, } 7I_1 - 3I_2 = 3 \quad \rightarrow \textcircled{i}$$

$$\text{Loop 2nd: } 6 - 3I_2 - 24 - 12(I_2 - I_3) - 6(I_2 - I_1) = 0$$

$$\text{or, } -18 - 3I_2 - 12I_2 + 12I_3 - 6I_2 + 6I_1 = 0$$

$$\text{or, } 6I_1 - 21I_2 + 12I_3 = 18$$

$$\text{or, } 3(2I_1 - 7I_2 + 4I_3) = 18$$

$$\text{or, } 2I_1 - 7I_2 + 4I_3 = 6 \quad \rightarrow \textcircled{ii}$$

$$\text{Loop 3rd: } 24 - 12(I_3 - I_2) = 0$$

$$\text{or, } 24 = 12(I_3 - I_2)$$

$$\text{or, } 2 = I_3 - I_2$$

$$\text{or, } I_2 - I_3 = -2 \quad \rightarrow \textcircled{iii}$$

Solving eqns \textcircled{i} & \textcircled{ii}

$$7I_1 - 3I_2 = 3 \quad \rightarrow \textcircled{i}$$

$$4I_3 + 2I_2 \leftarrow 7I_2 = 6 \quad \rightarrow \textcircled{ii}$$

Multiplying \textcircled{i} by 2 & \textcircled{ii} by 7 & solving them:

$$14I_1 - 6I_2 = 6$$

$$28I_3 + 14I_2 - 49I_2 = 42$$

$$-28I_3 + 43I_2 = -36$$

$$43I_2 - 28I_3 = -36 \quad \rightarrow \textcircled{iv}$$

Solving \textcircled{iv} & \textcircled{iii} :

$$(I_2 - I_3 = -2 \quad \textcircled{iii}) \times 28$$

$$43I_2 - 28I_3 = -36 \quad \rightarrow \textcircled{iv}$$

$$28I_2 - 28I_3 = -56$$

$$43I_2 - 28I_3 = -36$$

$$-15I_2 = -20$$

$$\therefore I_2 = 1.33A$$

From eqn \textcircled{iii} :

$$I_2 - I_3 = -2 \leftarrow 0 + (-1 + 1) \leftarrow 0$$


$$\text{or, } 1.33 - I_3 = -2 \leftarrow I_3 - I_2 + I_2 - I_3 \leftarrow 0$$

$$\text{or, } 1.33 + 2 = I_3 \leftarrow 0 - = 1.33 - I_3 \leftarrow 0$$

$$\therefore I_3 = 3.33A$$


∴ $I_{sc} = I_3 = 3.33 A$

Now, Norton's Eq. ckt is:

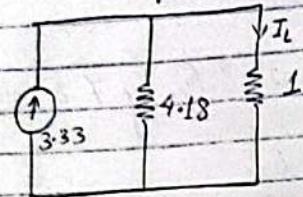

$$\therefore I_L = \frac{3.33 \times 4.18}{4.18 + 1} = 2.68 \text{ A}$$

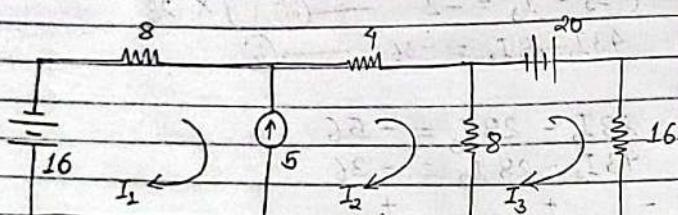- (ii) Use the concept of supermesh to find I_1 , I_2 and I_3 :



Soln: Supermesh equation:

$$I_2 - I_1 = 5 \quad \text{(i)}$$


At loop 3rd: (KVL apply)

$$-8(I_3 - I_2) + 20 - 16I_3 = 0$$

$$\text{or, } -8I_3 + 8I_2 - 16I_3 = -20$$

$$\text{or, } 8I_2 - 24I_3 = -20 \quad \text{(ii)}$$

Applying KVL at supermesh:

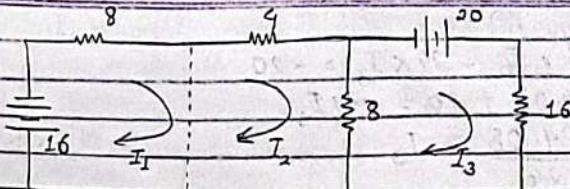

$$\begin{aligned} & -16 - 8I_1 - 4I_2 - 8(I_2 - I_3) = 0 \\ \text{or, } & -8I_1 - 4I_2 - 8I_2 + 8I_3 = 16 \\ \text{or, } & -8I_1 - 12I_2 + 8I_3 = 16 \quad \text{--- (iii)} \end{aligned}$$

Solving eqn (i) & (iii):

$$\begin{aligned} I_2 - I_1 &= 5 \quad | \times 8 \Rightarrow -8I_1 + 8I_2 = 40 \\ -8I_1 - 12I_2 + 8I_3 &= 16 \Rightarrow -8I_1 - 12I_2 + 8I_3 = 16 \quad + + - \end{aligned}$$

cancel $-8I_1$ from both sides
consequently add both sides then we get minimum
 $20I_2 - 8I_3 = 24 \quad \text{--- (iv)}$

Solving (ii) & (iv):

$$\begin{aligned} 8I_2 - 24I_3 &= -20 \Rightarrow 8I_2 - 24I_3 = -20 \\ 20I_2 - 8I_3 &= 24 \quad | \times 3 \Rightarrow 60I_2 - 24I_3 = 72 \quad - + - \end{aligned}$$

$$-52I_2 = -92$$

$$I_2 = \frac{-92}{-52}$$

$$\therefore I_2 = 1.76 \text{ A}$$

Now,

from eqn (i):

$$1.76 - I_1 = 5$$

$$1.76 - 5 = I_1$$

$$\therefore I_1 = -3.24 \text{ A}$$

from eqn (ii):

$$8 \times 1.76 - 24 \times I_3 = -20$$

$$\text{or, } 14.08 + 20 = 24I_3$$

$$\text{or, } \frac{34.08}{24} = I_3$$

$$\therefore I_3 = 1.42 \text{ A}$$

Hence,


$$I_1 = 1.76 \text{ A}$$

$$I_2 = -3.29 \text{ A}$$


$$I_3 = 1.42 \text{ A}$$

Maximum Power Transfer Theorem:

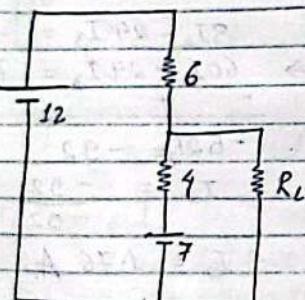- (i) Find the value of R_L so that it transfer maximum power and also find the maximum power.




Sol:

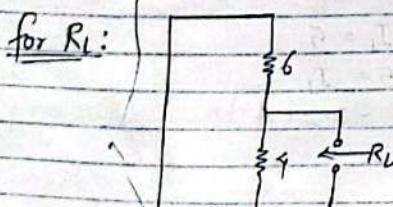

$$\therefore R_L = 6/4$$

$$= 1.5 \Omega$$

for V_S :

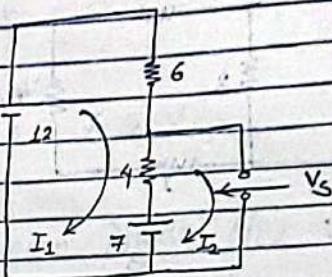

At loop (i):

$$12 - 6I_1 - 4(I_1 - I_2) - 7 = 0$$

$$\text{or, } 12 - 6I_1 - 4I_1 - 7 = 0$$

$$\text{or, } 5 - 10I_1 = 0$$

$$\text{or, } 5 = 10I_1$$

$$\therefore I_1 = 0.5 \text{ A}$$

At loop (ii):

$$-4(I_2 - I_1) - V_S + 7 = 0$$

$$\text{or, } 4I_1 + 7 = V_S$$

$$\text{or, } 4 \times 0.5 + 7 = V_S$$

$$\therefore |V_S| = 9 \text{ V}$$


Maximum power, $P_i = \frac{V_S^2}{4R_L}$

$$P_i = \frac{(9)^2}{4 \times 2.9}$$


$$= \frac{81}{9.6}$$

$$= 8.43 \text{ watt}$$

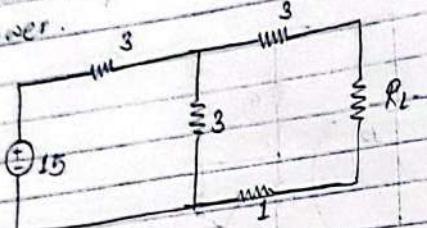(2) Find the value of R_L so that it transfers maximum power and also find the maximum power.




Sol: for R_L :

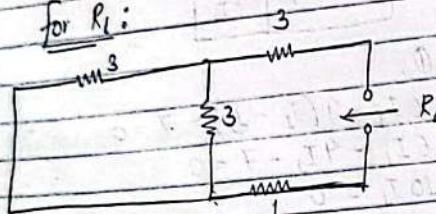

$$\begin{aligned} R_L &= (3//3) + 3 + 1 \\ &= 1.5 + 4 \\ &= 5.5 \Omega \end{aligned}$$

for V_s :

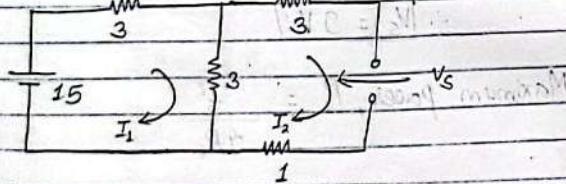

Applying KVL at loop 1st:

$$15 - 3I_1 - 3(I_1 - I_2) = 0$$

$$0_1, 15 - 3I_1 - 3I_1 = 0$$

$$0_1, 15 = 6I_1$$

$$\therefore I_1 = 2.5 \text{ A}$$

Applying KVL at loop 2nd:

$$-3(I_2 - I_1) - 3I_2 - V_s - I_2 = 0$$

$$0_1, 3I_1 - 0 - V_s - 0 = 0$$

$$0_2, 3I_1 = V_s$$

$$0_3, 3 \times 2.5 = V_s$$

$$\therefore V_s = 7.5 \text{ V}$$

$$\text{Now, Maximum Power } (P_i) = \frac{V_s^2}{4R_L}$$

$$= \frac{(7.5)^2}{4 \times 5.5}$$


$$= 2.55 \text{ watt}$$

Single Phase AC Circuit Analysis:

① Determine the average value and effective value of the square voltage wave as shown below:

[2006/2009 (spring)]

(7 marks)

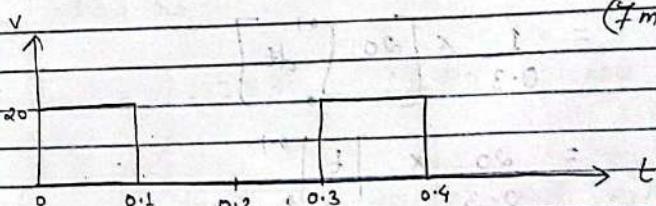

7/10

$$V_m = V(t) = 20$$

Time period of given wave (T) = 0.3

Now, Average value of voltage is given by:

$$V_{av} = \frac{1}{T} \int_0^T V(t) dt$$

$$= \frac{1}{0.3} \int_0^{0.3} V(t) dt$$

$$= \frac{1}{0.3} \left[\int_0^{0.1} V_1(t) dt + \int_{0.1}^{0.2} V_2(t) dt + \int_{0.2}^{0.3} V_3(t) dt \right]$$

~~From~~ From above wave form, we have:

$$V_1(t) = 20$$

$$V_2(t) = 0$$

$$V_3(t) = 0$$

$$\therefore V_{av} = \frac{1}{0.3} \left[\int_0^{0.1} 20 dt + 0 + 0 \right]$$

$$= \frac{1}{0.3} \times \left[20 \int_0^{0.1} dt \right]$$

$$= \frac{20}{0.3} \times |t| \Big|_0^{0.1}$$

$$= \frac{20}{0.3} \times (0.1 - 0) = 6.67 V$$

Now,

$$V_{rms} = \frac{1}{T} \int_0^T V^2(t) dt$$

$$= \frac{1}{0.3} \int_0^{0.3} V^2(t) dt$$

$$= \frac{1}{0.3} \left[\int_0^{0.1} V_1^2(t) dt + \int_{0.1}^{0.2} V_2^2(t) dt + \int_{0.2}^{0.3} V_3^2(t) dt \right]$$

$$= \frac{1}{0.3} \left[\int_0^{0.1} (20)^2 dt + 0 + 0 \right]$$

$$= \frac{1}{0.3} \times \left[400 \int_0^{0.1} dt \right]$$

$$= \frac{400}{0.3} \times |t| \Big|_0^{0.1}$$


$$= \frac{400}{0.3} \times (0.1 - 0)$$

$$= 133.33$$

$$\therefore V_{rms} = \sqrt{133.33} = 11.54 V$$

②

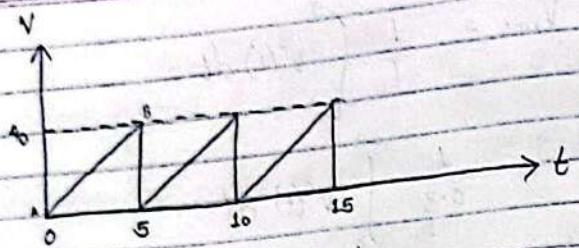Determine the form factor and peak factor of the given saw-tooth wave form:



Soln: Here,
Time period of the given waveform(T) = 5

Now, Average value of voltage is :

$$V_{av} = \frac{1}{T} \int_0^T v(t) dt$$

$$\text{or, } V_{av} = \frac{1}{5} \int_0^5 v(t) dt \quad \text{(i)}$$

& $v(t)$ at $(0-5)$ is : A(0,0), B(5,40)

Using two point formula:

$$y - y_1 = \frac{y_2 - y_1}{x_2 - x_1} (x - x_1)$$

$$\text{or, } y - 0 = \frac{40 - 0}{5 - 0} (x - 0)$$

$$\text{or, } y = 8(x - 0)$$

$$\text{or, } y = 8x$$

Since, $y = V$ & $x = t$

$$\therefore v(t) = 8t$$

putting value of $v(t)$ in eqn (i) :

$$V_{av} = \frac{1}{5} \int_0^5 8t dt$$

$$= \frac{8}{5} \times \int_0^5 t dt$$

$$= \frac{8}{5} \times \left[\frac{t^2}{2} \right]_0^5$$

$$= \frac{8}{5} \times \frac{1}{2} \times (25 - 0)$$

$$\therefore V_{av} = 20 \text{ V}$$

$$\text{Now, } V_{rms}^2 = \frac{1}{T} \int_0^T v^2(t) dt$$

$$= \frac{1}{5} \int_0^5 (8t)^2 dt$$

$$= \frac{1}{5} \int_0^5 64t^2 dt$$

$$= \frac{64}{5} \times \left[\frac{t^3}{3} \right]_0^5$$

$$= \frac{64}{5} \times \frac{1}{3} (125 - 0)$$

$$V_{rms}^2 = 533.33 \Rightarrow V_{rms} = 23.09 \text{ V}$$

DATE PAGE

New, form factor (k_f) = $\frac{\text{RMS value.}}{\text{Average value}}$

$$= \frac{23.09}{20}$$


$$= 1.15$$

Ind, peak fact (k_a) = $\frac{\text{Maximum value}}{\text{RMS value}}$

$$= \frac{40}{23.09}$$

$$= 1.73$$

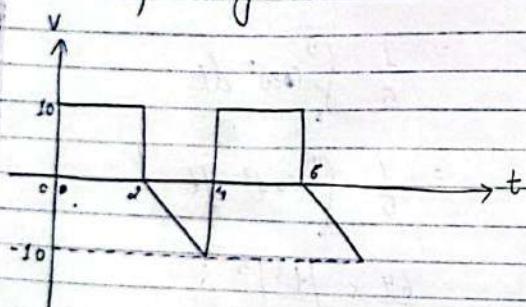③ Determine the average and effective value of the given saw-tooth wave form:



Soln: Time period of given waveform (T) = 4
Now, Average value of voltage is given by:

DATE PAGE

$$\text{Var} = \frac{1}{T} \int_0^T V(t) dt$$

$$= \frac{1}{4} \int_0^4 V(t) dt$$

$$= \frac{1}{4} \left[\int_0^2 V_1(t) dt + \int_2^4 V_2(t) dt \right] \quad \dots \dots (i)$$

From above waveform, we have:

$$V_1(t) = 10$$

$$V_2(t) \text{ at } (2-4) = A(2, 10), B(4, -10)$$

Using two point formula:

$$\frac{y-y_1}{x-x_1} = \frac{y_2-y_1}{x_2-x_1}$$

$$\therefore \frac{y-0}{x-2} = \frac{-10-0}{4-2}$$

$$\therefore y = -5(x-2)$$

$$\therefore y = -5x + 10$$

Since, $y = V(t)$ & $x = t$.

$$\therefore V(t) = -5t + 10$$

Substituting the value of $v_1(t)$ & $v_2(t)$
in eqn (i) :

$$V_{av} = \frac{1}{4} \left[\int_0^2 20 dt + \int_2^4 (-5t+10) dt \right]$$

$$= \frac{1}{4} \left[20 \int_0^2 dt - 5 \int_2^4 t dt + 10 \int_2^4 dt \right]$$

$$= \frac{1}{4} \left[20 \left| t \right|_0^2 - 5 \left| \frac{t^2}{2} \right|_2^4 + 10 \left| t \right|_2^4 \right]$$

$$= \frac{1}{4} \left[10x(2-0) - \frac{5}{2} (16-4) + 10 (4-2) \right]$$

$$= \frac{1}{4} [20 - 30 + 20]$$

$$= \frac{1}{4} \times 10$$

$$\therefore V_{av} = 2.5 V$$

Now, $V_{rms} = \frac{1}{T} \int_0^T V^2(t) dt$

$$= \frac{1}{4} \int_0^4 V^2(t) dt$$

P.9.0

$$= \frac{1}{4} \left[\int_0^2 v_1^2(t) dt + \int_2^4 v_2^2(t) dt \right]$$

$$= \frac{1}{4} \left[\int_0^2 (10)^2 dt + \int_2^4 (-5t+10)^2 dt \right]$$

$$= \frac{1}{4} \left[100 \int_0^2 dt + \int_2^4 (25t^2 - 100t + 100) dt \right]$$

$$= \frac{1}{4} \left[100x \left| t \right|_0^2 + \int_2^4 (25t^2 - 100t + 100) dt \right]$$

$$= \frac{1}{4} \left[100x(2-0) + 25 \int_2^4 t^2 dt - 100 \int_2^4 t dt + 100 \int_2^4 dt \right]$$

$$= \frac{1}{4} \left[200 + 25x \left| \frac{t^3}{3} \right|_2^4 - 100x \left| \frac{t^2}{2} \right|_2^4 + 100 \int_2^4 dt \right]$$


$$= \frac{1}{4} \left[200 + \frac{25}{3} (64-8) - \frac{100}{2} (16-4) + 100(4-2) \right]$$

$$= \frac{1}{4} \left[200 + \frac{400}{3} - 600 + 200 \right]$$

$$= \frac{1}{4} \left[200 + \frac{400}{3} \right]$$

$$\begin{aligned}
 & \frac{1}{\sqrt{2}} \times \frac{400}{3} = \frac{800}{4 \times 3} \\
 & V_{rms}^2 = 66.67 \\
 & V_{rms} = 8.16 \text{ V} \\
 & \therefore V_{rms} = 5.77 \text{ V}
 \end{aligned}$$

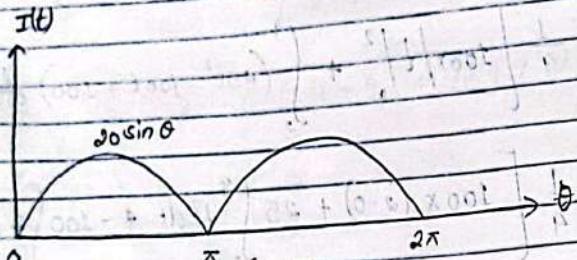⑦ Determine average & rms value of the given waveform:



Ans:

$$\text{Time period } (T) = \pi$$

$$I = 20 \sin \theta$$

Now, Average value of current is :

$$I_{av} = \frac{1}{T} \int_0^T I(t) dt$$

$$= \frac{1}{\pi} \int_0^\pi 20 \sin \theta d\theta$$

$$= \frac{200}{\pi} \int_0^\pi \sin \theta d\theta$$

$$= \frac{200}{\pi} \left[-\cos \theta \right]_0^\pi$$

$$= -\frac{200}{\pi} (\cos \pi - \cos 0)$$

$$= -\frac{200}{\pi} \times (-1 - 1)$$

$$= \frac{400}{\pi} = 12.73 \text{ A}$$

$$\text{Now, } I_{rms}^2 = \frac{1}{T} \int_0^T I^2(t) dt$$

$$= \frac{1}{\pi} \int_0^\pi (20 \sin \theta)^2 d\theta$$

$$= \frac{1}{\pi} \times 400 \int_0^\pi \sin^2 \theta d\theta$$

$$= \frac{400 \times 1}{\pi \cdot 2} \int_0^\pi 2 \sin^2 \theta d\theta$$

$$= \frac{200}{\pi} \int_0^\pi (1 - \cos 2\theta) d\theta$$

$$= \frac{200}{\pi} \left[\theta - \frac{1}{2} \sin 2\theta \right]_0^\pi$$

$$= \frac{200}{\pi} \left[10 \Big|_0^\pi - \frac{1}{2} \int_0^\pi \sin 2\theta d\theta \right]$$

$$= \frac{200}{\pi} \left[(\pi - 0) - \frac{1}{2} (\sin 2\pi - \sin 0) \right]$$

$$= \frac{200}{\pi} \left[\pi - \frac{1}{2} \times 0 \right]$$


$$= \frac{200}{\pi} \times \pi$$

$$= 200$$

$$I_{rms} = \sqrt{200}$$

$$= 14.14$$

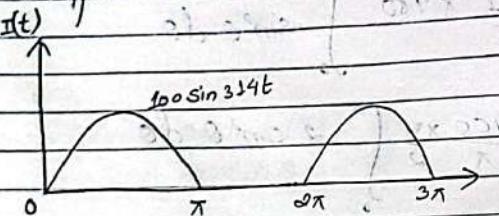(5) Determine the form factor of the given waveform.



Sol: Time period (T) = 2π

$$I(t) = 100 \sin 314t \quad (\text{let, } 314t = \theta)$$

$$= 100 \sin \theta$$

Now,

Average current is given by:

$$I_{av} = \frac{1}{T} \int_0^T I(t) dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} I(t) dt$$

$$= \frac{1}{2\pi} \left[\int_0^{\pi} I_1(t) dt + \int_{\pi}^{2\pi} I_2(t) dt \right]$$

$$= \frac{1}{2\pi} \left[\int_0^{\pi} 100 \sin \theta d\theta + 0 \right]$$

$$= \frac{1}{2\pi} \times 100 \int_0^{\pi} \sin \theta d\theta$$

$$= \frac{1}{2\pi} \times 100 \left[-\cos \theta \Big|_0^{\pi} \right]$$

$$= -\frac{50}{\pi} \times (\cos \pi - \cos 0)$$

$$= -\frac{50}{\pi} \times (-1 - 1)$$

$$= \frac{100}{\pi}$$

$$= 31.83 \text{ A}$$

Now,

$$I_{rms} = \frac{1}{T} \int_0^T I^2(t) dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} I^2(t) dt$$

$$= \frac{1}{2\pi} \left[\int_0^{\pi} I_s(t) dt + \int_{\pi}^{2\pi} I_s^2(t) dt \right]$$

$$= \frac{1}{2\pi} \left[\int_0^{\pi} (300 \sin \theta)^2 d\theta + \int_{\pi}^{2\pi} 0 d\theta \right]$$

$$= \frac{1}{2\pi} \times 10000 \int_0^{\pi} \sin^2 \theta d\theta$$

$$= \frac{5000}{\pi} \int_0^{\pi} \frac{1}{2} \times 2 \sin^2 \theta d\theta$$

$$= \frac{2500}{\pi} \int_0^{\pi} \theta \sin^2 \theta d\theta$$

$$= \frac{2500}{\pi} \int_0^{\pi} (1 - \cos 2\theta) d\theta$$

$$= \frac{2500}{\pi} \left[\int_0^{\pi} d\theta - \int_0^{\pi} \cos 2\theta d\theta \right]$$

$$= \frac{2500}{\pi} \left[1\theta \Big|_0^{\pi} - \frac{-\sin 2\theta}{2} \Big|_0^{\pi} \right]$$

$$= \frac{2500}{\pi} \left[(\pi - 0) - \frac{1}{2} (\sin 2\pi - \sin 0) \right]$$

$$= \frac{2500}{\pi} \times \left[\pi - \frac{1}{2} \times 0 \right]$$

$$= \frac{2500 \times \pi}{\pi}$$

$$I_{rms}^2 = 2500$$

$$I_{rms} = \sqrt{2500}$$


$$= 50$$

\therefore form factor (k_f) = Rms value
average value

$$= \frac{50}{31.83}$$

$$= 1.5$$

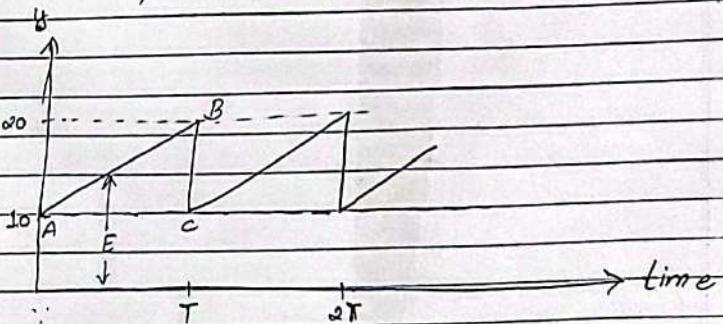⑥ Determine the rms and average value of the waveform shown below:



Soln: Here,
Time period $\boxed{T} = T$

$$\therefore y_{av} = \frac{1}{T} \int y dt \quad \dots \dots \dots (1)$$

The value of y at $0-T$ can be obtained

by A(0, 10) & B(T, 20)

$$\text{Now, } y-10 = \frac{20-10}{T-0} (T-0)$$

$$\text{or, } y-10 = \frac{10}{T} T$$

$$\text{or, } y = \frac{10T}{T} + 10$$

$$\because x=t \text{ then, } y(t) = \frac{10t}{T} + 10$$

from eqn (i)

$$y_{av} = \frac{1}{T} \int_0^T \left(\frac{10t}{T} + 10 \right) dt$$

$$= \frac{1}{T} \left[\int_0^T \frac{10t}{T} dt + \int_0^T 10 dt \right]$$

$$= \frac{1}{T} \left[\frac{10}{T} \int_0^T t dt + 10 \int_0^T dt \right]$$

$$= \frac{1}{T} \left[\frac{10}{T} \cdot \frac{t^2}{2} \Big|_0^T + 10 \cdot t \Big|_0^T \right]$$

$$= \frac{1}{T} \left[\frac{10}{2T} (T^2 - 0) + 10 (T - 0) \right]$$

$$= \frac{1}{T} \left[\frac{5}{T} \times T^2 + 10T \right]$$

$$= \frac{1}{T} [5T + 10T]$$

$$= \frac{1}{T} \times 15T$$

$$= 15$$

$$\text{Now, } y_{rms} = \sqrt{\frac{1}{T} \int_0^T y^2(t) dt}$$

$$= \frac{1}{T} \int_0^T \left(\frac{10t}{T} + 10 \right)^2 dt$$

$$= \frac{1}{T} \int_0^T \left(\frac{100t^2}{T^2} + 2 \times \frac{10t}{T} \times 10 + 100 \right) dt$$

$$= \frac{1}{T} \left[\int_0^T \frac{100t^2}{T^2} dt + \int_0^T \frac{200t}{T} dt + \int_0^T 100 dt \right]$$

$$= \frac{1}{T} \left[\frac{100}{T^2} \int_0^T t^2 dt + \frac{200}{T} \int_0^T t dt + 100 \int_0^T dt \right]$$

$$= \frac{1}{T} \left[\frac{100}{T^2} \cdot \frac{t^3}{3} \Big|_0^T + \frac{200}{T} \cdot \frac{t^2}{2} \Big|_0^T + 100 \cdot t \Big|_0^T \right]$$

$$= \frac{1}{T} \left[\frac{100}{T^2} \cdot \frac{1}{3} (T^3 - 0) + \frac{200}{T} \cdot \frac{1}{2} (T^2 - 0) + 100 \cdot T \right]$$


$$\begin{aligned}
 &= \frac{1}{T} \left[\frac{500}{T^2} \times \frac{1}{3} T^3 + \frac{500}{T} \times \frac{1}{2} \pi T^2 + 100 \times T \right] \\
 &= \frac{1}{T} \left[\frac{500T}{3} + 100T + 100T \right] \\
 &= \frac{1}{T} \left[\frac{500T}{3} + 200T \right] \\
 &= \frac{1}{T} \times \frac{700T}{3} \\
 &= \frac{700}{3}
 \end{aligned}$$

$$y_{\text{rms}} = 233.33$$

$$y_{\text{rms}} = \sqrt{233.33}$$

$$\therefore y_{\text{rms}} = 15.27$$

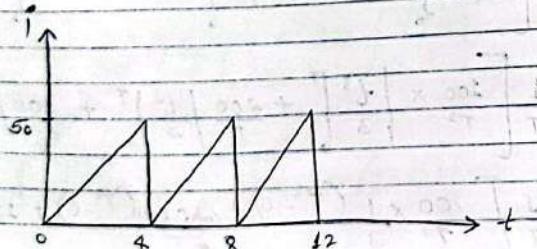⑦ find the form-factor of the wave form given below:



Given: Here,
Time period (T) = 4

Now, Average current is given by:

$$\begin{aligned}
 I_{\text{av}} &= \frac{1}{T} \int_0^T I(t) dt \quad \dots \dots \dots (1) \\
 &= \frac{1}{4} \int_0^4 I(t) dt \quad \dots \dots \dots (1)
 \end{aligned}$$

$I(t)$ at $0-4$ is obtained by $A(0,0)$ & $B(4, 50)$

$$\text{Now, } y-0 = \frac{50-0}{4-0} (x-0)$$

$$\text{or, } y = \frac{50x}{4}$$

$$\therefore I(t) = \frac{50t}{4}$$

Putting value of $I(t)$ in eqn (1):

$$I_{\text{av}} = \frac{1}{4} \int_0^4 \frac{50t}{4} dt$$

$$= \frac{1}{4} \times \frac{50}{4} \int_0^4 t dt$$

$$= \frac{50}{16} \left| \frac{t^2}{2} \right|_0^4$$

$$= \frac{60}{35} \times \frac{1}{2} (4^2 - 0)$$

$$= 25 \text{ A}$$

Now,

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T I^2(t) dt}$$

$$= \sqrt{\frac{1}{4} \int_0^4 \left(\frac{60t}{35}\right)^2 dt}$$

$$= \frac{2500}{4 \times 16} \int_0^4 t^2 dt$$

$$= \frac{2500}{64} \times \left| \frac{t^3}{3} \right|_0^4$$

$$= \frac{2500}{64 \times 3} \times (4^3 - 0)$$

$$= \frac{2500 \times 64}{64 \times 3}$$

$$= 833.33$$


$$I_{\text{rms}} = \sqrt{833.33}$$

$$= 28.86$$

Now, form factor (k_f) = $\frac{\text{RMS value}}{\text{Average value}}$

$$= \frac{28.86}{25} = 1.15$$

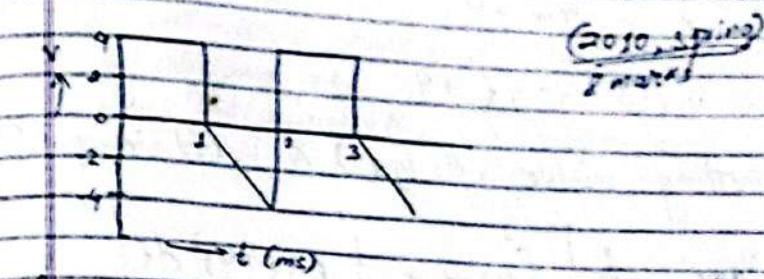Q) Calculate the rms and average value of the voltage wave shown below:



Sol:

Here, Time period (T) = 2

Now, Average value of voltage is given by:

$$\bar{V}_{\text{av}} = \frac{1}{T} \int_0^T V(t) dt$$

$$= \frac{1}{2} \int_0^2 V(t) dt$$

$$= \frac{1}{2} \left[\int_0^1 V_1(t) dt + \int_1^2 V_2(t) dt \right] \dots \dots (1)$$

From above given waveform:

$$V_1(t) = 4$$

$V_2(t)$ at $t=1$ is obtained from $A(1,0) \& B(2,0)$. Then,

$$y-0 = \frac{-4-0}{2-1} (x-1)$$

$$\text{Q1. } g = -4(t-1)$$

$$g = -4t + 4$$

$$v_1(t) = -4t + 4$$

Putting value of $v_1(t)$ & $v_2(t)$ in eqn ①

$$V_{\text{rms}} = \frac{1}{2} \left[\int_0^1 (4)^2 dt + \int_1^2 (-4t+4)^2 dt \right]$$

$$= \frac{1}{2} \left[16 \int_0^1 dt + \int_1^2 (16t^2 - 32t + 16) dt \right]$$

$$= \frac{1}{2} \left[16 |t| \Big|_0^1 + \int_1^2 16t^2 dt - \int_1^2 32t dt + \int_1^2 16 dt \right]$$

$$= \frac{1}{2} \left[16(1-0) + 16 \left| \frac{t^3}{3} \right| \Big|_1^2 - 32 \left| \frac{t^2}{2} \right| \Big|_1^2 + 16|t| \Big|_1^2 \right]$$

$$= \frac{1}{2} \left[16 + \frac{16 \times (8-1)}{3} - \frac{32}{2} \times (4-1) + 16(2-1) \right]$$

$$= \frac{1}{2} \left[16 + \frac{112}{3} - 48 + 16 \right]$$


$$= \frac{1}{2} \left[32 - 48 + \frac{112}{3} \right]$$

$$= \frac{1}{2} \left(\frac{112-48}{3} \right) = \frac{64}{2 \times 3} = 10.67$$

V_{rms} : $\sqrt{30.67} = 3.26 \text{ volt}$

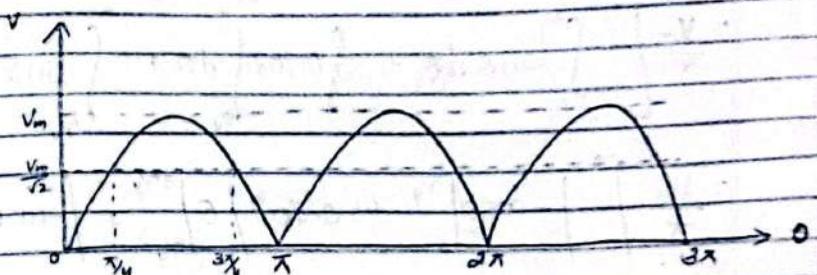(Q3)

A full-wave rectified sinusoidal voltage is clipped at $\frac{1}{\sqrt{2}}$ of its maximum value. Calculate the average and rms values of such a voltage.



Soln:

Here,
Time period (T) = π

The voltage at different intervals are:

$$0 < \theta < \pi/4 : V_{\text{rms}} \sin \theta$$

$$\pi/4 < \theta < 3\pi/4 : V_m/\sqrt{2} = 0.707 V_m$$

$$3\pi/4 < \theta < \pi : V = V_{\text{rms}} \sin \theta$$

Now,

Average voltage is given by:

$$V_{\text{av}} = \frac{1}{T} \int_0^T V(\theta) d\theta$$

$$= \frac{1}{\pi} \int_0^\pi V(\theta) d\theta$$

$$= \frac{1}{\pi} \left[\int_0^{\pi} v_1(\theta) d\theta + \int_{\pi}^{3\pi/4} v_2(\theta) d\theta + \int_{3\pi/4}^{\pi} v_3(\theta) d\theta \right]$$

$$= \frac{1}{\pi} \left[\int_0^{\pi} V_m \sin \theta d\theta + \int_{\pi}^{3\pi/4} 0.707 V_m d\theta + \int_{3\pi/4}^{\pi} V_m \sin \theta d\theta \right]$$

$$= \frac{V_m}{\pi} \left[\int_0^{\pi} \sin \theta d\theta + \int_{\pi}^{3\pi/4} 0.707 d\theta + \int_{3\pi/4}^{\pi} \sin \theta d\theta \right]$$

$$= \frac{V_m}{\pi} \left[\left| -\cos \theta \right|_0^{\pi} + 0.707 \left| \theta \right|_{\pi}^{3\pi/4} + \left| -\cos \theta \right|_{3\pi/4}^{\pi} \right]$$

$$= \frac{V_m}{\pi} \left[(-\cos \pi + \cos 0) + 0.707 \left(\frac{3\pi}{4} - \frac{\pi}{4} \right) + (-\cos \frac{\pi}{4} + \cos \frac{3\pi}{4}) \right]$$

$$= \frac{V_m}{\pi} \left[\left(-\frac{1}{\sqrt{2}} + 1 \right) + \left(0.707 \times \frac{\pi}{2} \right) + \left(1 + \frac{1}{\sqrt{2}} \right) \right]$$

$$= \frac{V_m}{\pi} \left[1 + 1 - \frac{1}{\sqrt{2}} - \frac{1}{\sqrt{2}} + \frac{0.707\pi}{2} \right]$$

$$= \frac{V_m}{\pi} \left[2 - \frac{2}{\sqrt{2}} + \frac{0.707\pi}{2} \right]$$

$$= \frac{V_m}{\pi} \left[2 - \sqrt{2} + \frac{0.707\pi}{2} \right]$$

$$= \frac{V_m}{\pi} (0.585 + j.11)$$

$$\frac{V_m \times 1.696}{\pi}$$

$$= 0.59 V_m$$

Now,

$$V_{rms}^2 = \frac{1}{T} \int_0^T V^2(\theta) d\theta$$

$$= \frac{1}{\pi} \int_0^{\pi} V^2(\theta) d\theta$$

$$= \frac{1}{\pi} \left[\int_0^{\pi/4} V_m^2 \sin^2 \theta d\theta + \int_{\pi/4}^{3\pi/4} (0.707)^2 V_m^2 d\theta + \int_{3\pi/4}^{\pi} V_m^2 \sin^2 \theta d\theta \right]$$

$$= \frac{V_m^2}{\pi} \left[\int_0^{\pi/4} \sin^2 \theta d\theta + 0.499 \int_{\pi/4}^{3\pi/4} d\theta + \int_{3\pi/4}^{\pi} \sin^2 \theta d\theta \right]$$

$$= \frac{V_m^2}{\pi} \left[\frac{1}{2} \int_0^{\pi/4} \cos 2\theta d\theta + 0.499 \int_{\pi/4}^{3\pi/4} d\theta + \frac{1}{2} \int_{3\pi/4}^{\pi} \cos 2\theta d\theta \right]$$

$$= \frac{V_m^2}{\pi} \left[\frac{1}{2} \int_0^{\pi/4} (1 - \cos 2\theta) d\theta + 0.499 \left| \theta \right|_{\pi/4}^{3\pi/4} + \frac{1}{2} \int_{3\pi/4}^{\pi} (1 - \cos 2\theta) d\theta \right]$$

$$\frac{1}{2} \int_{3\pi/4}^{\pi} (1 - \cos 2\theta) d\theta$$

$$= \frac{V_m^2}{\pi} \left[\frac{1}{2} \left(\int_0^{\pi/4} d\theta - \int_0^{\pi/4} \cos 2\theta d\theta \right) + \left(0.499 \times \frac{\pi}{2} \right) \left(\frac{\pi}{4} - \frac{1}{2} \right) \right]$$

$$+ \frac{1}{2} \left(\int_{3\pi/4}^{\pi} d\theta - \int_{3\pi/4}^{\pi} \cos 2\theta d\theta \right)$$

$$= \frac{V_m^2}{\pi} \left[\frac{1}{2} \left(| \theta | \Big|_0^{\pi/4} - \left| \frac{\sin 2\theta}{2} \right| \Big|_0^{\pi/4} \right) + \left(0.499 \times \frac{\pi}{2} \right) \right]$$

$$+ \frac{1}{2} \left(| \theta | \Big|_{3\pi/4}^{\pi} - \left| \frac{\sin 2\theta}{2} \right| \Big|_{3\pi/4}^{\pi} \right)$$

$$= \frac{V_m^2}{\pi} \left[\frac{1}{2} \left(\left(\frac{\pi}{4} - 0 \right) - \frac{1}{2} (\sin \frac{\pi}{2} - \sin 0) \right) + \frac{0.499\pi}{2} \right]$$

$$+ \frac{1}{2} \left(\left(\pi - \frac{3\pi}{4} \right) - \frac{1}{2} (\sin 2\pi - \sin \frac{3\pi}{2}) \right)$$

$$= \frac{V_m^2}{\pi} \left[\frac{1}{2} \left[\frac{\pi}{4} - \frac{1}{2}(1-0) \right] + \frac{0.499\pi}{2} + \frac{1}{2} \left[\frac{\pi}{4} - \frac{1}{2}(0+1) \right] \right]$$

$$= \frac{V_m^2}{\pi} \left[\frac{1}{2} \times \left(\frac{\pi}{4} - \frac{1}{2} \right) + \frac{0.499\pi}{2} + \frac{1}{2} \times \left(\frac{\pi}{4} - \frac{1}{2} \right) \right]$$

$$= \frac{V_m^2}{\pi} \left[\frac{0.285}{2} + \frac{0.499\pi}{2} + \frac{0.285}{2} \right]$$

$$= \frac{V_m^2}{\pi} \times 1.06$$

$$= 0.33 V_m^2$$

$$\therefore V_{rms} = \sqrt{0.33 V_m^2}$$

$$= 0.58 V_m \text{ Ans}$$

(10)

The resistance 20Ω , capacitor $150\mu F$, inductor $0.2H$ are connected in series with $230V, 50Hz$ supply calculate:

- (i) Inductance (X_L)
- (ii) Capacitance (X_C)
- (iii) Impedance (Z)
- (iv) Current (I)

Ques:

Here,

$$R = 20\Omega$$

$$C = 150\mu F = 150 \times 10^{-6} F$$

$$L = 0.2H$$

$$f = 50Hz$$

Now,

$$\begin{aligned} \text{Inductance } (X_L) &= 2\pi f L \\ &= 2\pi \times 50 \times 0.2 \\ &= 62.83 \end{aligned}$$

$$\begin{aligned} \text{Capacitance } (X_C) &= \frac{1}{2\pi f C} \\ &= \frac{1}{2\pi \times 50 \times 150 \times 10^{-6}} \\ &= 21.22 \end{aligned}$$

PAGE /
DATE / /

$$\begin{aligned} \text{Impedance } (z) &= R + j(X_L - X_C) \\ &= 20 + j(62.83 - 21.22) \\ &= 20 + j41.61 \end{aligned}$$

$$I = \frac{V}{Z} = \frac{230}{20 + j41.61} \quad \dots \dots \dots (i)$$

Now,

$$\begin{aligned} |Z| &= \sqrt{(20)^2 + (j41.61)^2} \\ &= \sqrt{(20)^2 + (41.61)^2} \\ &= 46.16 \end{aligned}$$

$$\theta = \tan^{-1} \left(\frac{41.61}{20} \right) = 64.3^\circ$$

$$\therefore z = 46.16 \angle 64.3^\circ \text{ (rectangular)}$$

from eqn (i):

$$\begin{aligned} I &= \frac{230 \angle 0^\circ}{46.16 \angle 64.3^\circ} \\ &= 4.98 \angle -64.3^\circ \end{aligned}$$

Note: When $Z_1 = r_1 < 0$,

$$Z_2 = r_2 < 0$$

$$(i) Z_1 + Z_2 = r_1 \angle \theta_1 + r_2 \angle \theta_2$$

$$\begin{aligned} &= (a_1 + j b_1) + (a_2 + j b_2) \\ &= (a_1 + a_2) + j(b_1 + b_2) \end{aligned}$$

$$(ii) Z_1 \times Z_2 = r_1 \angle \theta_1 \times r_2 \angle \theta_2$$

$$= (r_1 \times r_2) \angle (\theta_1 + \theta_2)$$

$$(iii) \frac{Z_1}{Z_2} = \frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = \frac{r_1}{r_2} \angle (\theta_1 - \theta_2)$$

(11) The resistance 20Ω , inductor $0.2H$ and capacitor $150\mu F$ are connected in series with a supply voltage of $230V, 50Hz$.

- (i) Inductive reactance
- (ii) Capacitive reactance
- (iii) Impedance
- (iv) Admittance
- (v) Current
- (vi) Power factor
- (vii) Active power
- (viii) Reactive power

[8 marks]

Q:

Here,


$$R = 20 \Omega$$

$$L = 0.2 \text{ H}$$

$$C = 150 \text{ } \mu\text{F} = 150 \times 10^{-6} \text{ F}$$

$$V = 230 \text{ V}$$

$$f = 50 \text{ Hz}$$

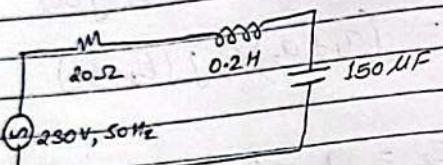

(i) Inductive Reactance (X_L) = $2\pi f L$
= $2\pi \times 50 \times 0.2$
= 62.83

(ii) Capacitive Reactance (X_C) = $\frac{1}{2\pi f C}$
= $\frac{1}{2\pi \times 50 \times 150 \times 10^{-6}}$
= 21.22

(iii) Impedance σ (Z) = $R + j(X_L - X_C)$
= $20 + j(62.83 - 21.22)$
= $20 + j41.61$
= $46.16 \angle 64.3^\circ$

(iv) Admittance (γ) = $\frac{1}{Z}$

$$= \frac{1}{46.16 \angle 64.3^\circ}$$

$$= 0.02 \angle -64.3^\circ$$

(v) Current (I) = $\frac{V}{Z}$

$$= 230 \angle 0$$

$$= 46.16 \angle 64.3^\circ$$

$$= 4.98 \angle -64.3^\circ \text{ A}$$

(vi) Power factor = $\cos \phi$

$$= \cos(\theta_v - \theta_i)$$

$$= \cos(0 - (-64.3))$$

$$= \cos 64.3^\circ$$

$$= 0.43$$

(vii) Active power = $VI \cos \phi$

$$= 230 \times 4.98 \times 0.43$$

$$= 492.5 \text{ watt}$$

(viii) Reactive power = $VI \sin \phi$

$$= 230 \times 4.98 \times \sin(64.3^\circ)$$

$$= 1032.09 \text{ VAR}$$

$$= 1032 \text{ KVAR}$$


(ii) An impedance $(20+j5)\Omega$ & $(30+j8)\Omega$ are connected in series across a 200V, 50Hz supply. Calculate: Current, active power, apparent power & reactive power, and voltage across Z_1 & Z_2 .

$$S.f.: V = 200V$$

$$f = 50\text{Hz}$$

$$Z_1 = (20+j5)\Omega$$

$$Z_2 = (30+j8)\Omega$$

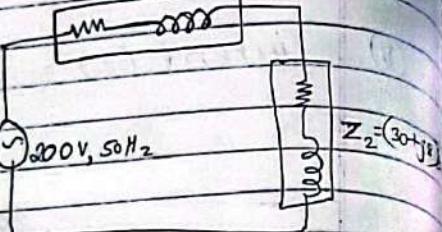

Now,

$$\text{Total impedance } (Z) = Z_1 + Z_2$$

$$\begin{aligned} &= (20+j5) + (30+j8) \\ &= 20+j5 + 30+j8 \\ &= 20+30+j(5+8) \\ &= 50+j13 \\ &= 53.66 \angle 14.57^\circ \end{aligned}$$

$$\therefore \text{Current } (I) = \frac{V}{Z}$$

$$= \frac{200}{53.66 \angle 14.57^\circ}$$

$$= 3.87 \angle -14.57^\circ \text{ A}$$

$$\text{Power factor} = \cos \phi$$

$$= \cos(\theta_v - \theta_i)$$

$$= \cos(0 - (-14.57))$$

$$= \cos 14.57^\circ = 0.96$$

$$\text{Active power} = VI \cos \phi$$

$$\begin{aligned} &= 200 \times 3.87 \times 0.96 \cos 14.57^\circ \\ &= 749.1 \text{ watt} \end{aligned}$$

$$\text{Reactive power} = VI \sin \phi$$

$$\begin{aligned} &= 200 \times 3.87 \times \sin 14.57^\circ \\ &= 184.7 \text{ VAR} \end{aligned}$$

$$\text{Apparent power} = VI$$

$$= 200 \times 3.87$$

$$= 774 \text{ volt Ampere}$$

Voltage across Z_2 is given by:

$$V_{Z_2} = I \cdot Z_2$$

$$= (3.87 \angle -14.57^\circ) \times (30+j8)$$

$$= (3.87 \angle -14.57^\circ) \times (31.04 \angle 14.93^\circ)$$

$$= (3.87 \times 31.04) \angle (-14.57 + 14.93)$$

$$= 120.12 \angle 0.36^\circ \text{ volt Ans}$$

Voltage across Z_1 is given by:

$$V_{Z_1} = I \cdot Z_1$$

$$= (3.87 \angle -14.57^\circ) \times (20+j5)$$

$$= (3.87 \angle -14.57^\circ) \times (20.61 \angle 14.03^\circ)$$

$$= (3.87 \times 20.61) \angle (-14.57 + 14.03)$$

$$= 79.76 \angle -0.54^\circ \text{ volt Ans}$$

- (13) An impedance of $(6-j8)\Omega$ is connected in parallel with $(8+j6)\Omega$. The impedances are fed from a 220V, 50Hz supply. Find the current through each branch, total current, total impedance, total admittance, active power, reactive power and power factor of the given circuit.

Soln:


Here,

$$z_1 = (6-j8)\Omega$$

$$z_2 = (8+j6)\Omega$$

$$V = 220 \text{ V}$$

$$f = 50 \text{ Hz}$$

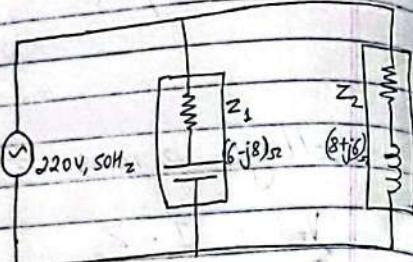

Now,

Branch current:

$$I_1 = \frac{V}{z_1} = \frac{220}{6-j8}$$

$$= \frac{220}{10 \angle -53.13}$$

$$= 22 \angle 53.13 \text{ A}$$

$$I_2 = \frac{V}{z_2} = \frac{220}{8+j6}$$

$$= \frac{220}{10 \angle 36.86}$$

$$= 22 \angle -36.86 \text{ A}$$

$$\text{Total current } -(I) = V$$

$$\text{Total impedance } (Z) = \frac{z_1 \cdot z_2}{z_1 + z_2}$$

$$= \frac{(6-j8) \times (8+j6)}{(6-j8) + (8+j6)}$$

$$= \frac{(10 \angle -53.13) \times (10 \angle 36.86)}{6-j8 + 8+j6}$$

$$= \frac{(10 \angle -53.13) \times (10 \angle 36.86)}{14 \angle -j2}$$

$$= \frac{(10 \angle -53.13) \times (10 \angle 36.86)}{14 \cdot 14 \angle -8 \cdot 13}$$

$$= (100 \times 10) \angle (-53.13 + 36.86)$$

$$= \frac{100 \angle -16.27}{14 \cdot 14 \angle -8 \cdot 13}$$

$$= \frac{100}{14 \cdot 14} \angle (-16.27 + 8 \cdot 13)$$

$$= 7.07 \angle -8.14 \Omega$$

$$\text{Total admittance } (Y) = \frac{1}{Z}$$

$$= \frac{1}{7.07 \angle -8.14}$$

$$= 0.14 \angle 8.14$$

PAGE

Total current (I) = $\frac{V}{Z}$

$$= \frac{220}{7.07 \angle -8.19}$$

$$= 31.1 \angle 8.19$$

Power factor = $\cos \phi$

$$= \cos(\theta_v - \theta_i)$$

$$= \cos(0 - 8.19)$$

$$= \cos(-8.19)$$

$$= 0.98$$

Active power = $VI \cos \phi$

$$= 220 \times 31.1 \times \cos(-8.19)$$

$$= 6773.06 \text{ watt}$$

Reactive power = $VI \sin \phi$

$$= 220 \times 31.1 \times \sin(-8.19)$$

$$= -968.77 \text{ VAR}$$

- (14) An impedances of $(3-j8)$ and $(2+j15)$ are connected in parallel. The circuit is fed from a $230V$, 50Hz supply. Find the current through each branch, total go circuit current, impedance, p.f., active power, reactive power & apparent power?

P.T.O

PAGE


Given : Here,

$$z_1 = (3-j8)$$

$$z_2 = (2+j15)$$

$$V = 230V$$

$$f = 50\text{Hz}$$

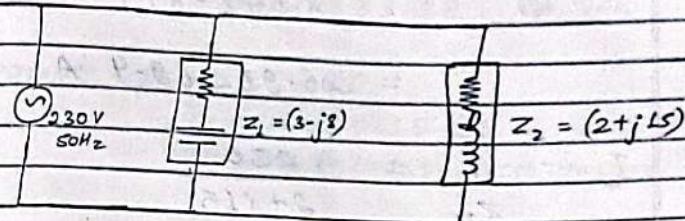

Total impedance (Z) = $\frac{z_1 \times z_2}{z_1 + z_2}$

$$= (3-j8) \times (2+j15)$$

$$3-j8 + 2+j15$$

$$= (8.54 \angle -69.4) \times (15.13 \angle 82.4)$$

$$5+j7$$

$$= (8.54 \times 15.13) \angle (-69.4 + 82.4)$$

$$8.6 \angle 54.4$$

$$= \frac{129.2 \angle 13}{8.6 \angle 54.5}$$

$$= \frac{129.2}{8.6} \angle (13 - 54.5)$$

$$= 15.02 \angle -41.5$$

Branch current:

$$I_1 = \frac{V}{Z_1} = \frac{230}{3-j5}$$
$$= \frac{230}{8.54 \angle -69.4^\circ}$$
$$= 26.93 \angle 69.4^\circ \text{ A}$$

$$I_2 = \frac{V}{Z_2} = \frac{230}{2+j15}$$
$$= \frac{230}{15.13 \angle 82.4^\circ}$$
$$= 15.2 \angle -82.4^\circ \text{ A}$$

$$\text{Total current (I)} = \frac{V}{Z}$$
$$= \frac{230}{15.02 \angle -41.5^\circ}$$
$$= 15.31 \angle 41.5^\circ \text{ A}$$

$$\text{Power factor (P.f)} = \cos \phi$$
$$= \cos (\theta_v - \theta_i)$$
$$= \cos (0 - 41.5^\circ)$$
$$= 0.74$$

Active power = $VI \cos \phi$

$$= 230 \times 15.31 \times \cos (-41.5^\circ)$$
$$= 2637.29 \text{ watt}$$

Reactive power = $VI \sin \phi$

$$= 230 \times 15.31 \times \sin (-41.5^\circ)$$
$$= -2333.28 \text{ VAR}$$

Apparent power = VI

$$= 230 \times 15.31$$
$$= 3521.3 \text{ volt ampere}$$

- (15) Two impedance of $(10+j5)\Omega$ & $(20+j30)\Omega$ are connected in series across a 200V, 50Hz supply. Find current, active power, apparent power and reactive power factor.

Soln.


Ans

$$Z_1 = (10+j5)\Omega$$

$$Z_2 = (20+j30)\Omega$$

$$V = 200V$$

$$f = 50\text{Hz}$$

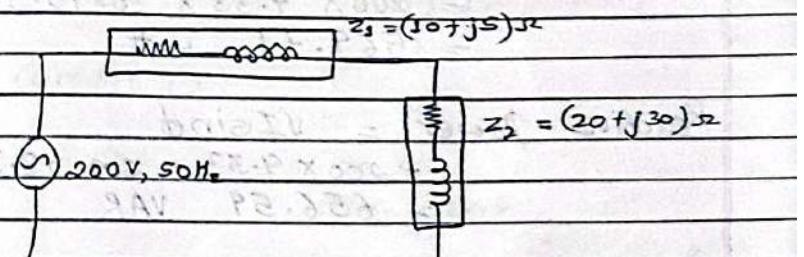

DATE / / PAGE / /

$$\begin{aligned} \text{Total Impedance } (Z) &= Z_1 + Z_2 \\ &= (20 + j5) + (30 + j30) \\ &= 10 + 20 + j5 + j30 \\ &= 30 + j35 \\ &= 46.09 \angle 49.3^\circ \end{aligned}$$

$$\begin{aligned} \therefore \text{Current } (I) &= \frac{V}{Z} \\ &= \frac{200}{46.09 \angle 49.3^\circ} \\ &= 4.33 \angle -49.3^\circ \end{aligned}$$

Active Power = $\text{VI cos } \phi$

$$\begin{aligned} \text{Power factor} &= \cos \phi \\ &= \cos (\theta_v - \theta_i) \\ &= \cos (0 - (-49.3)) \\ &= \cos 49.3^\circ \\ &= 0.65 \end{aligned}$$

$$\begin{aligned} \text{Active power} &= \text{VI cos } \phi \\ &= 200 \times 4.33 \times \cos 49.3^\circ \\ &= 564.71 \text{ Watt} \end{aligned}$$

$$\begin{aligned} \text{Reactive power} &= \text{VI sin } \phi \\ &= 200 \times 4.33 \times \sin 49.3^\circ \\ &= 656.54 \text{ VAR} \end{aligned}$$


$$\begin{aligned} \text{Apparent power} &= \text{VI} \\ &= 200 \times 4.33 \\ &= 866 \text{ volt ampere} \end{aligned}$$

(16)
(2008)
Spring
marks

Two impedances of $(20 + j5) \Omega$ and $(30 + j8) \Omega$ are connected in series across a $200V, 50Hz$ supply. Find current, active power, apparent power and reactive power & power factor.

Soln:
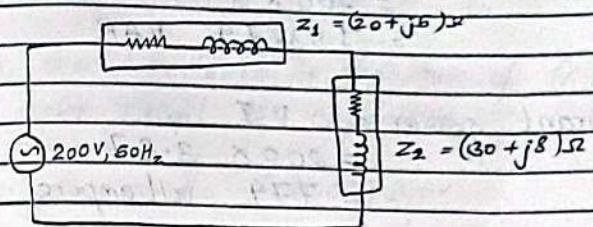
$$\begin{aligned} Z_1 &= (20 + j5) \Omega \\ Z_2 &= (30 + j8) \Omega \\ V &= 200V \\ f &= 50 \text{ Hz} \end{aligned}$$



$$\begin{aligned} \text{Total Impedance } (Z) &= Z_1 + Z_2 \\ &= (20 + j5) + (30 + j8) \\ &= 20 + 30 + j5 + j8 \\ &= 50 + j13 \\ &= 51.66 \angle 14.5^\circ \end{aligned}$$

$$\begin{aligned} \therefore \text{Current } (I) &= \frac{V}{Z} \\ &= \frac{200}{51.66 \angle 14.5^\circ} \\ &= 3.87 \angle -14.5^\circ \end{aligned}$$

PAGE DATE

$$\begin{aligned}
 \text{power factor (p.f)} &= \cos \phi \\
 &= \cos(\theta_v - \theta_i) \\
 &= \cos(0 - (-14.5)) \\
 &= \cos 14.5 \\
 &= 0.96
 \end{aligned}$$

$$\begin{aligned}
 \text{Active power} &= VI \cos \phi \\
 &= 200 \times 3.87 \times \cos 14.5 \\
 &= 749.39 \text{ watt}
 \end{aligned}$$

$$\begin{aligned}
 \text{Reactive power} &= VI \sin \phi \\
 &= 200 \times 3.87 \times \sin 14.5 \\
 &= 193.79 \text{ VAR}
 \end{aligned}$$

$$\begin{aligned}
 \text{Apparent power} &= VI \\
 &= 200 \times 3.87 \\
 &= 774 \text{ volt ampere}
 \end{aligned}$$

(i) An AC voltage of $(80+j60)$ V applied to a circuit result current of $(4+j10)$ A.

Find:

- (i) The impedance of the circuit stating whether it is inductive or capacitive.
- (ii) Power consumed
- (iii) Phase angle
- (iv) Power factor
- (v) Draw a phasor diagram

Sol: Here,

$$V = (80+j60) V = 100 \angle 36.86^\circ$$

$$I = (4+j10) A = 10.77 \angle 68.19^\circ$$

$$I = (4+j10) A$$

$$(80+j60) V$$

$$\begin{aligned}
 (i) Z &= \frac{V}{I} = \frac{100 \angle 36.86^\circ}{10.77 \angle 68.19^\circ} \\
 &= 9.28 \angle -31.33^\circ \\
 &= 7.93 - j4.82
 \end{aligned}$$

Since, the impedance is the form of $(R-jX)$. So the given circuit is capacitive.

$$(ii) \text{power consumed} = \text{Active power}$$

$$\begin{aligned}
 &= VI \cos \phi \\
 &= 100 \times 10.77 \times \cos(-31.33^\circ) \\
 &= 100 \times 10.77 \times \cos(-31.33^\circ) \\
 &= 919.95 \text{ watt}
 \end{aligned}$$

$$(iii) \text{phase angle: } -\phi = \theta_v - \theta_i$$

$$\begin{aligned}
 &= 36.86 - 68.19^\circ \\
 &= -31.33^\circ
 \end{aligned}$$

$$\begin{aligned}
 (iv) \text{power factor} &= \cos \phi \\
 &= \cos(-31.33^\circ) \\
 &= 0.85
 \end{aligned}$$

(v) phasor diagram


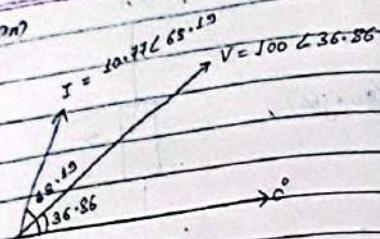


fig: phasor diagram

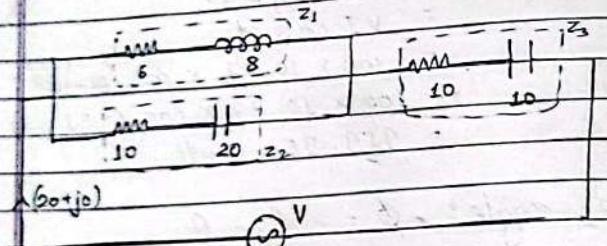- (vi) In the circuit given below total current
 $I = (20 + j0) A$.
Calculate: (i) Branch Current
(ii) Voltage V , V_1 & V_2
(iii) Power factor
(iv) Active & Reactive power
(v) Draw a phasor diagram.



Ques:

$$Z_1 = (6 + j8) \Omega = 10 \angle 53.13^\circ$$

$$Z_2 = (10 - j20) \Omega = 22.36 \angle -63.43^\circ$$

$$Z_3 = (10 - j10) \Omega = 14.14 \angle -45^\circ$$

$$I = (20 + j0) A = 20 A \angle 0^\circ$$

Ques: Total Impedance (Z) = $(Z_1 \parallel Z_2) + Z_3$

$$= \frac{Z_1 \times Z_2}{Z_1 + Z_2} + Z_3$$

$$= (10 \angle 53.13^\circ) \times (22.36 \angle -63.43^\circ) + (10 - j10)$$
$$= 6 + j8 + 10 - j20$$

$$= (10 \times 22.36) \angle (53.13 - 63.43) + (10 - j10)$$
$$= 16 - j12$$

$$= 223.6 \angle -10.3^\circ + (10 - j10)$$
$$= 20 \angle -36.86^\circ$$

$$= 11.18 \angle 26.56^\circ + (10 - j10)$$

$$= 10 + j5 + 10 - j10$$

$$= 20 - j5$$

$$= 20.61 \angle -19.03^\circ$$

Now,

(ii) $V = I \times Z$

$$= (20 \angle 0^\circ) \times (20.61 \angle -19.03^\circ)$$
$$= 412.2 \angle -19.03^\circ$$

$$V_1 = V_{Z_1 Z_2} = I \times (Z_1 \parallel Z_2)$$

$$= (20 \angle 0^\circ) \times (11.18 \angle 26.56^\circ)$$

$$= 223.6 \angle 26.56^\circ$$

$$\begin{aligned}
 V_2 &= V_{Z_3} = I \times Z_3 \\
 &= (20 \angle 0) \times (14.14 \angle -45) \\
 &= 282.8 \angle -45
 \end{aligned}$$

(i) Branch currents:

$$\begin{aligned}
 I_{Z_1} &= \frac{V_1}{Z_1} = \frac{223.6 \angle 26.56}{10 \angle 53.13} \\
 &= 22.36 \angle -26.57
 \end{aligned}$$

$$\begin{aligned}
 I_{Z_2} &= \frac{V_1}{Z_2} = \frac{223.6 \angle 26.56}{22.36 \angle -63.43} \\
 &= 10 \angle 89.99
 \end{aligned}$$

$$\begin{aligned}
 I_{Z_3} &= \frac{V_2}{Z_3} = \frac{282.8 \angle -45}{14.14 \angle -45} \\
 &= 20 \angle 0
 \end{aligned}$$

(iii) power factor (p.f) = $\cos \phi$

$$= \cos (\theta_v - \theta_i)$$

$$= \cos (-14.03 - 0)$$

$$= \cos (-14.03)$$

$$= 0.97$$


(iv) Active power = $VI \cos \phi$

$$\begin{aligned}
 &= 412.2 \times 20 \times \cos (-14.03) \\
 &= 7998.07 \text{ watt.}
 \end{aligned}$$

(v) Reactive power = $VI \sin \phi$

$$\begin{aligned}
 &= 412.2 \times 20 \times \sin (-14.03) \\
 &= -1998.5 \text{ VAR}
 \end{aligned}$$

(vi) phasor diagram

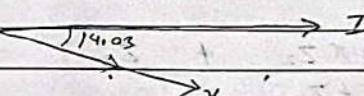

(g) In the circuit given below total current $I = (25 + j0) A$. calculate

(i) Branch current


(ii) Voltage V_1, V_2, V

(iii) Power factor

(iv) Active & Reactive Power

(v) ~~power~~ total power in the circuit & power in each branch.

(vi) phasor diagram

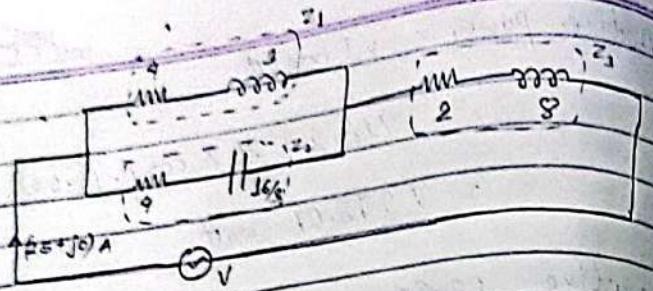

Here,
 $Z_1 = (4 + j3) \Omega = 5 \angle 36.87^\circ$

$$Z_2 = \left(4 - j\frac{16}{3}\right) \Omega = 6.67 \angle -53.13^\circ$$

$$Z_3 = (2 + j8) \Omega = 8.24 \angle 76^\circ$$

$$I = (25 + j0) A = 25 \angle 0^\circ$$

New, Total impedance is:

$$Z = (Z_1 \parallel Z_2) + Z_3$$

$$= \frac{Z_1 \times Z_2}{Z_1 + Z_2} + Z_3$$

$$= (5 \angle 36.87^\circ) \times (6.67 \angle -53.13^\circ) + (2 + j8)$$

$$= 4 + j3 + 9 - j\frac{16}{3}$$

$$= (5 \times 6.67) \angle (36.87 - 53.13) + (2 + j8)$$

$$= 33.35 \angle -16.26^\circ + (2 + j8)$$

$$= 8.33 \angle -16.26^\circ$$

$$= 4 \angle 0^\circ + (2 + j8)$$

$$= 4 + j0 + 2 + j8$$

$$= 6 + j8$$

$$= 10 \angle 53.13^\circ$$

Now,

(i) $V_{z_1 z_2} = V_1 = I \times (Z_1 \parallel Z_2)$

$$= (25 \angle 0^\circ) \times (4 \angle 0^\circ)$$

$$= 100 \angle 0^\circ$$

And, $V_{z_3} = V_2 = I \times Z_3$

$$= (25 \angle 0^\circ) \times (8.24 \angle 76^\circ)$$

$$= 206 \angle 76^\circ$$

And, $V = IZ$

$$= (25 \angle 0^\circ) \times (10 \angle 53.13^\circ)$$

$$= 250 \angle 53.13^\circ$$

(ii) Branch Currents:

$$I_{z_1} = \frac{V_1}{Z_1} = \frac{100 \angle 0^\circ}{5 \angle 36.87^\circ}$$

$$= 20 \angle -36.87^\circ$$

$$I_{z_2} = \frac{V_1}{Z_2} = \frac{100 \angle 0^\circ}{6.67 \angle -53.13^\circ} = 15 \angle 53.13^\circ$$

$$I_{Z_3} = \frac{V_A}{Z_3} = \frac{206 \angle 76^\circ}{8.29 \angle 76^\circ} \\ = 25 \angle 0^\circ$$

N.B.,

$$(iii) \text{ Power factor (P.f)} = \cos \phi \\ = \cos(\theta_V - \theta_I) \\ = \cos(53.13^\circ - 0) \\ = \cos(53.13^\circ) \\ = 0.6$$

$$(iv) \text{ Active power} = VI \cos \phi \\ = 250 \times 25 \times \cos(53.13^\circ) \\ = 3750 \text{ watt}$$

$$\text{Reactive power} = VI \sin \phi \\ = 250 \times 25 \times \sin(53.13^\circ) \\ = 5000 \text{ VAR}$$

(v) Total power in the circuit is:

$$P = I^2 Z \\ = I \times I Z \\ = I \times V \\ = (25 \angle 0^\circ) \times (250 \angle 53.13^\circ) \\ = 6250 \angle 53.13^\circ \\ = 3750 + j5000$$

$$P_{Z_1} = I_{Z_1} \times V_{Z_1} \\ = (20 \angle -36.87^\circ) \times (100 \angle 0^\circ) \\ = 2000 \angle -36.87^\circ = 1600 - j1200$$

$$P_{Z_2} = I_{Z_2} \times V_1$$

$$= (0.15 \angle 53.13^\circ) \times (100 \angle 0^\circ) \\ = 1500 \angle 53.13^\circ \\ = 900 + j1200$$


$$P_{Z_3} = I_{Z_3} \times V_2$$

$$= (25 \angle 0^\circ) \times (206 \angle 76^\circ) \\ = 5150 \angle 76^\circ \\ = 1246 + j4997$$

(vi) phasor diagram

- (20) A total current of 10A flows through the parallel combination of three impedances: $(2-j5)\Omega$, $(6+j3)\Omega$ and $(3+j4)\Omega$. Calculate
 (i) the current flowing through each branch
 (ii) P.f
 (iii) voltage flowing through the circuit (V).

P.T.O.

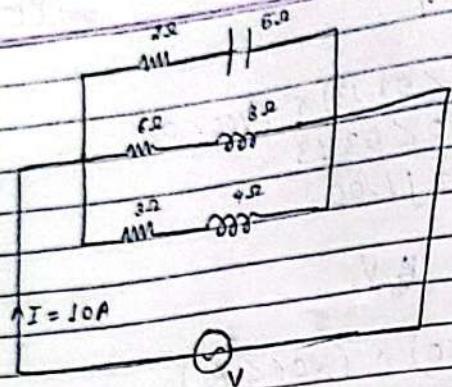

Here,

$$z_1 = (2 - j5) \Omega = 5.38 \angle -68.19^\circ$$

$$z_2 = (6 + j3) \Omega = 6.7 \angle 26.56^\circ$$

$$z_3 = (3 + j4) \Omega = 5 \angle 53.13^\circ$$

$$I = 10 A = (10 \angle 0^\circ) A = 10 \angle 0^\circ$$

$$\text{Now, Total Impedance } (Z) = z_1 \cdot z_2 \cdot z_3 \\ z_1 z_2 + z_2 z_3 + z_3 z_1$$

where,

$$z_1 z_2 = (5.38 \angle -68.19^\circ) \times (6.7 \angle 26.56^\circ) \\ = 36.04 \angle -41.63^\circ \\ = 27 - j29$$

$$z_2 z_3 = (6.7 \angle 26.56^\circ) \times (5 \angle 53.13^\circ) \\ = 33.5 \angle 79.69^\circ \\ = 6 + j33$$

$$z_3 z_1 = (5 \angle 53.13^\circ) \times (5.38 \angle -68.19^\circ) \\ = 26.9 \angle -15.06^\circ \\ = 26 - j7$$

PAGE DATE

$$z_1 z_2 + z_2 z_3 + z_3 z_1 = 27 - j24 + 6 + j33 + 26 - j7 \\ = 27 + 6 + 26 - j24 - j7 + j33 \\ = 59 + j2 \\ = 59.03 \angle 1.94^\circ$$

$$z_1 \cdot z_2 \cdot z_3 = (z_1 \cdot z_2) \cdot z_3 \\ = (36.04 \angle -41.63^\circ) \times (5 \angle 53.13^\circ) \\ = 180.2 \angle 11.5^\circ \\ = 176.5 + j35.92$$

$$\therefore Z = 180.2 \angle 11.5^\circ \\ 59.03 \angle 1.94^\circ$$

$$(2) \cdot 1 = 3.05 \angle 9.56^\circ \\ (\text{e.g. } 3 + j0.5)$$

$$\text{Now, (iii) } V = I \times Z \\ = (10 \angle 0^\circ) \times (3.05 \angle 9.56^\circ) \\ = 30.5 \angle 9.56^\circ$$

(i) Current through each branch:

$$I_1 = I_{z_1} = I \times \frac{1}{z_1} = \frac{10 \angle 0^\circ}{z_1} \\ z_1 z_2 + z_2 z_3 + z_3 z_1 \\ = (10 \angle 0^\circ) \times (33.5 \angle 79.69^\circ) \\ (59.03 \angle 1.94^\circ) \\ = (10 \angle 0^\circ) \times (0.567 \angle 77.75^\circ) \\ = 5.67 \angle 77.75^\circ \\ = 1.2 + j5.5$$

$$I_2 = I_{Z_2} = IX \frac{Z_1 Z_2}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}$$

$$= (10 \angle 0) \times \frac{26.9 \angle -15.06}{59.03 \angle 1.94}$$

$$\begin{aligned} &= (10 \angle 0) \times (0.455 \angle -17) \\ &= 4.55 \angle -17 \\ &= 4.3 - j 1.33 \end{aligned}$$

$$I_3 = I_{Z_3} = IX \frac{Z_1 Z_2}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}$$


$$= (10 \angle 0) \times \frac{(36.04 \angle -41.63)}{(59.03 \angle 1.94)}$$

$$\begin{aligned} &= (10 \angle 0) \times (0.61 \angle -43.57) \\ &= 6.1 \angle -43.57 \\ &= 4.91 - j 4.2 \end{aligned}$$

(ii) p.f. = $\cos \phi$
 $= \cos (\theta_v - \theta_i)$
 $= \cos (9.56 - 0)$
 $= 0.986$

(21) Determine the average power delivered to each of the three boxed network in the given circuit.

P_{T2}

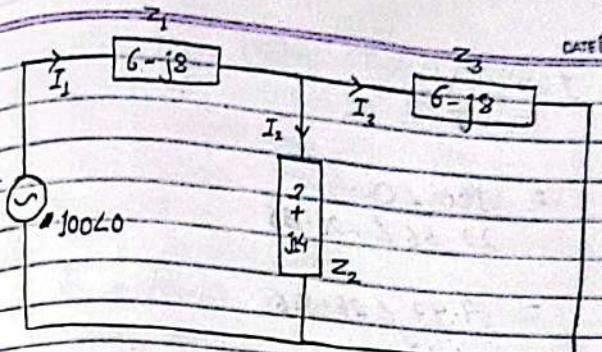

Now:

Here,

$$Z_1 = 6-j8 = 10 \angle -53.13$$

$$Z_2 = 2+j19 = 19.19 \angle 28.79$$

$$Z_3 = 6-j8 = 10 \angle -53.13$$

$$V = 100 + j0 = 100 \angle 0$$

Now, Total Impedance :

$$Z = 8Z_1 + (Z_2 || Z_3)$$

$$\begin{aligned} &= (6-j8) + (19.19 \angle 28.79) \times (10 \angle -53.13) \\ &\quad + 2+j19 + 6-j8 \\ &= (6-j8) + 191.9 \angle 28.79 \\ &\quad + 8+j6 \end{aligned}$$

$$\begin{aligned} &= (6-j8) + 191.9 \angle 28.79 \\ &\quad + 10 \angle 36.86 \end{aligned}$$

$$\begin{aligned} &= 6-j8 + 19.19 \angle -8.12 \\ &= 6-j8 + 14-j2 \\ &= 20-j10 \\ &= 22.36 \angle -26.56 \end{aligned}$$

$$\therefore I = \frac{V}{Z}$$

$$= 100 \angle 0^\circ$$

$$22.36 \angle -26.56^\circ$$

$$= 4.97 \angle 26.56^\circ$$

$$= 4 + j2$$

$$\therefore I = I_1 = 4.97 \angle 26.56^\circ$$

Now,

$$V_{z_1} = I Z_1$$

$$= (4.97 \angle 26.56^\circ) \times (10 \angle -53.13^\circ)$$

$$= 44.7 \angle -26.57^\circ$$

$$= 40 - j20$$

$$V_{z_2 z_3} = I \times (Z_2 \parallel Z_3)$$

$$= (4.97 \angle 26.56^\circ) \times (14.14 \angle -8.12^\circ)$$

$$= 63.2 \angle 18.49^\circ$$

$$= 60 + j20$$

Now,

$$I_2 = \frac{V_{z_2 z_3}}{Z_2} = \frac{63.2 \angle 18.49^\circ}{14.14 \angle 81.87^\circ}$$

$$= 4.97 \angle -63.49^\circ$$

$$I_3 = \frac{V_{z_2 z_3}}{Z_3} = \frac{63.2 \angle 18.49^\circ}{10 \angle -53.13^\circ}$$

$$= 6.32 \angle 71.57^\circ$$

Now,

P_1 = Power across Z_1 :

$$P_1 = V_{z_1} \times I_1 \times \cos \phi_1$$

$$= 44.7 \times 4.97 \times \cos(0_v - \theta_1)$$

$$= 44.7 \times 4.97 \times \cos(-26.57 - 26.56)$$

$$= 44.7 \times 4.97 \times \cos(-53.13)$$

$$= 120 \text{ watt}$$

: Power across Z_2 :

$$P_2 = V_{z_2 z_3} \times I_2 \times \cos \phi_2$$

$$= 63.2 \times 4.97 \times \cos(18.49 + 63.49)$$

$$= 40 \text{ watt}$$

\therefore Power across Z_3 :

$$P_3 = V_{z_2 z_3} \times I_3 \times \cos \phi_3$$

$$= 63.2 \times 4.97 \times \cos(18.49 - 71.57)$$

$$= 240 \text{ watt}$$


\therefore Total power in the circuit is:

$$P = P_1 + P_2 + P_3 = 120 + 40 + 240 = 400 \text{ watt}$$

Resonant frequency:

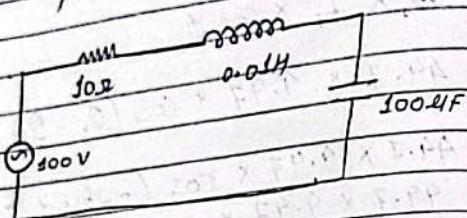(2)

A series R-L-C circuit has 10Ω resistance, $0.01H$ inductance & 100 nF capacitance. A 100 V supply with a frequency of 50 Hz is applied to the circuit. Find the resonant frequency, band width, Q-factor, total current resonance current and voltage across inductor. [2009, fall]



Sol:

Here,

$$R = 10\Omega$$

$$L = 0.01\text{ H}$$

$$C = 100\text{ nF} = 100 \times 10^{-9}\text{ F}$$

$$V = 100\text{ V}$$

$$f = 50\text{ Hz}$$

$$\text{Now, } X_L = 2\pi f L = 2\pi \times 50 \times 0.01 \\ = 3.14$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-9}} \\ = 31.83$$

$$\therefore Z = R + j(X_L - X_C) \\ = 10 + j(3.14 - 31.83) \\ = 10 - j28.69 \\ = 30.38 \angle -70.78^\circ$$

Remember: Bandwidth (BW) = $\frac{\text{Resonant frequency}}{\text{Q-factor}} = \frac{1}{\text{Q}}$
Quality factor (Q)

$$\therefore \text{Total current (I)} = \frac{V}{Z}$$

$$= 100 \angle 0$$

$$= 30.38 \angle -70.78$$

$$= 3.29 \angle -70.78 \text{ A}$$

$$\text{Resonance Current (I}_0) = \frac{V}{R}$$

$$= \frac{100 \angle 0}{30.38 \angle}$$

$$= \frac{100}{10}$$

$$= 10 \text{ A}$$

$$\text{voltage across inductor (V)} = I \times X_L \\ = 3.29 \times 3.14 \\ = 10.33 \text{ volt}$$

$$\text{Resonance frequency (f}_0) = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{0.01 \times 100 \times 10^{-9}}} \\ = 159.15 \text{ Hz}$$

$$\text{Q-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{10} \times \sqrt{\frac{0.01}{100 \times 10^{-9}}} \\ = 1$$


$$\text{Band width } (\Delta\omega) = \frac{R}{L}$$

$$= \frac{10}{0.01}$$

$$= 1000$$

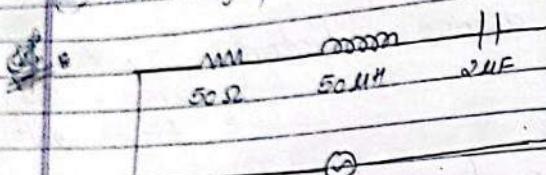(2) For given circuit determine

- Ω -factor
- the new value of capacitor required for resonance at same frequency if inductance is doubled.
- new Ω -factor.



Ans:

$$R = 50\Omega$$

$$L = 50 \mu H = 50 \times 10^{-6} H$$

$$C = 2 \mu F = 2 \times 10^{-6} F$$

$$(i) \Omega\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{50} \sqrt{\frac{50 \times 10^{-6}}{2 \times 10^{-6}}}$$

$$= 0.1$$

Let initial inductor be L_1 , then final inductor be L_2 . Similarly, initial capacitor be C_1 & final capacitor be C_2 .

Accdg to the question:

$$L_2 = 2L_1$$

At resonance: $f = f_0$

$$f = \frac{1}{2\pi\sqrt{L_1 C_1}}$$

But, when inductance is doubled then $L_2 = 2L_1$, so we get:

$$\therefore \frac{1}{2\pi\sqrt{L_1 C_1}} = \frac{1}{2\pi\sqrt{2L_1 C_2}}$$

$$\text{Or, } \frac{1}{\sqrt{L_1 C_1}} = \frac{1}{\sqrt{2L_1 C_2}}$$

$$\text{Or, } \frac{1}{L_1 C_1} = \frac{1}{2L_1 C_2}$$

$$\text{Or, } \frac{1}{C_1} = \frac{1}{2C_2}$$

$$\text{Or, } C_2 = \frac{C_1}{2}$$

$$\text{Or, } C_2 = \frac{2 \times 10^{-6}}{2} \quad \therefore C_2 = 1 \times 10^{-6} F$$


(28) New Q-factor = $\frac{1}{R} \sqrt{\frac{L}{C_2}}$

$$= \frac{1}{R} \sqrt{\frac{2\pi L}{C_2}}$$

$$= \frac{1}{50} \sqrt{\frac{2\pi \times 50 \times 10^{-6}}{5 \times 10^{-6}}}$$

$$= 0.2$$

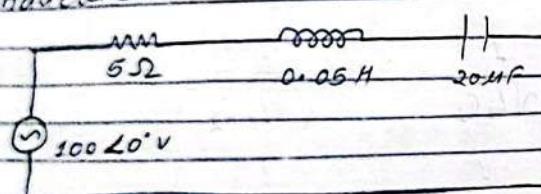(29) In the series circuit shown, the applied voltage is 100V of variable frequency. If the frequency is varied till the resonance occurs in the circuit than find the current, resonant frequency, bandwidth, quality factor and the voltage across the inductors.



Ans:

$$R = 5\Omega$$

$$L = 0.05 \text{ H}$$

$$C = 20 \mu\text{F} = 20 \times 10^{-6} \text{ F}$$

$$V = 100 \angle 0^\circ \text{ V}$$

$$f = 50 \text{ Hz}$$

Now,

$$X_L = 2\pi f L = 2\pi \times 50 \times 0.05$$

$$= 15.71$$

$$X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{2\pi \times 50 \times 20 \times 10^{-6}}$$

$$= 159.15$$

$$\therefore Z = R + j(X_L - X_C)$$

$$= 5 + j(15.71 - 159.15)$$

$$= 5 - j193.44$$

$$= 193.52 \angle -87.78^\circ - 88^\circ$$

$$\therefore \text{Total current } (I) = \frac{V}{Z}$$

$$= \frac{100 \angle 0^\circ}{193.52 \angle -88^\circ}$$

$$= 0.69 \angle 88^\circ \text{ A}$$

$$\therefore \text{Resonance current } (I_0) = \frac{V}{R}$$

$$= \frac{100}{5}$$

$$= 20 \text{ A}$$

$$\text{Resonant frequency } (f_0) = \frac{1}{2\pi \sqrt{LC}}$$

$$= \frac{1}{2\pi \sqrt{0.05 \times 20 \times 10^{-6}}}$$

$$= 159.15 \text{ Hz}$$

$$Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{5} \sqrt{\frac{0.05}{20 \times 10^{-6}}}$$

$$= 10$$

$$\text{Bandwidth } (\Delta\omega) = \frac{R}{L}$$

$$= \frac{10}{0.05} = 100$$

$$\begin{aligned}\text{Voltage across inductors } (V_L) &= I \times X_L \\ &= 0.69 \times 15.71 \\ &= 10.8 \text{ V}\end{aligned}$$

(Q) An AC series circuit has a resistance of 10Ω and an inductance of 0.2H and capacitance of $60\mu\text{F}$. If the applied voltage is 200V , calculate resonant frequency and power at resonance.

Soln: Here,

$$R = 10\Omega$$

$$L = 0.02\text{ H}$$

$$C = 60\mu\text{F} = 60 \times 10^{-6}\text{ F}$$

$$V = 200\text{V}$$

New,

$$\text{Resonant frequency } (f_0) = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{0.2 \times 60 \times 10^{-6}}} = 45.99\text{ Hz}$$

DATE _____
PAGE _____

Resonance Current (I_0) = $\frac{V}{R}$

$$= \frac{200}{10}$$

$$= 20 \text{ A}$$

∴ Power at resonance (P) = $I_0^2 R$

$$= (20)^2 \times 10$$

$$= 4000 \text{ watt}$$

Polyphase AC Circuit Analysis (3-Ø)

Star/Delta Connected System:

① A balanced star connected node of $(10+j5)\Omega$ per phase is connected in a balanced 3-Ø supply of 200V , 50Hz . Determine:

- (i) Line current
- (ii) Phase voltage
- (iii) Power factor
- (iv) Active power

Soln: Here,

$$V_L = 200\text{V}$$

$$f = 50\text{Hz}$$

$$Z = (10+j5)\Omega$$

$$= 11.18 \angle 29.5^\circ$$

In Star(Y) connected system :

$$I_L = I_{ph}$$

$$\text{Ans}, V_L = \sqrt{3} V_{ph}$$

$$\therefore V_{ph} = \frac{V_L}{\sqrt{3}}$$

$$\therefore V_{ph} = \frac{750}{\sqrt{3}}$$

$\therefore [V_{ph} = 230.99]$ → phase voltage

$$\text{Now, } I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.99 \angle 0}{11.18 \angle 29.5}$$

$$\therefore [I_{ph} = 20.65 \angle -29.5]$$

$$\therefore I_L = I_{ph}$$

$$\therefore [I_L = 20.65 \angle -29.5] \rightarrow \text{line current}$$

$$\begin{aligned} \text{Power factor} &= \cos\phi \\ &= \cos(0^\circ - 29.5^\circ) \\ &= \cos(-29.5^\circ) \\ &= \cos(29.5^\circ) \\ &= 0.89 \end{aligned}$$

$$\therefore \text{Active power} = \sqrt{3} V_L I_L \cos\phi$$

$$\begin{aligned} &= \sqrt{3} \times 400 \times 20.65 \times \cos(29.5^\circ) \\ &= 12.7 \text{ kW} \end{aligned}$$


- (2) Each phase of a star connected system consists of a resistance of 100Ω in parallel with a capacitor of $32 \mu F$.

calculate : (i) line current

(ii) Power consumed

(iii) Total kVA (Apparent power)

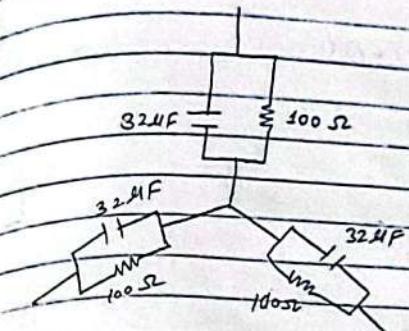(iv) Power factor when connected to a $415V, 50Hz$ 3ϕ supply.



Here,

$$R = 100 \Omega$$

$$C = 32 \mu F = 32 \times 10^{-6} F$$

$$\text{Now, } Z = R // (-jX_C)$$

$$\begin{aligned} \text{Where, } X_C &= \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 32 \times 10^{-6}} \\ &= 99.47 \Omega \end{aligned}$$

$$\therefore Z = R // (-jX_C)$$

$$= 100 // (-j 99.47)$$

$$= \frac{100 \times (-j 99.47)}{100 - j 99.47}$$

$$= \frac{-j 9947}{100 - j 99.47}$$

$$= \frac{99.47 \angle -30^\circ}{141.04 \angle -99.83^\circ} = 0.7052 \angle -60.17^\circ$$

$$Z = 70.52 \angle -60.17^\circ$$

Now,

(i) Line current:

$$\text{Eqn } \frac{V_L}{Z}$$

$$I_L = I_{ph}$$

$$= \frac{V_{ph}}{Z_{ph}}$$

$$= \frac{V_L / \sqrt{3}}{Z_{ph}} \quad [\because V_{ph} = \frac{V_L}{\sqrt{3}}]$$

$$= \frac{V_L}{\sqrt{3} Z_{ph}}$$

$$= \frac{415}{\sqrt{3} \times (70.52 \angle -60.17^\circ)}$$

$$= \frac{239.60}{70.52 \angle -60.17^\circ}$$

$$\therefore I_L = 3.39 \angle 50.17^\circ \text{ A}$$

$$(ii) \text{ Power consumed} = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 415 \times 3.39 \times \cos(60.17^\circ)$$

$$= 1.71 \text{ kW}$$

$$(iii) \text{ Total KVA} = \sqrt{3} V_L I_L$$

$$\begin{aligned} &= \sqrt{3} \times 415 \times 3.39 \\ &= 2436.73 \text{ VA} \\ &= 2.43 \text{ KVA} \end{aligned}$$

P.T.O

(3) When the balance impedance are connected to Δ (delta) across 500V, 50Hz supply, the line current drawn is 20A at a power factor of 0.3 lagging. Calculate the impedance & state whether its capacitive or inductive.

S.F:

$$V_L = 500 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$I_L = 20 \text{ A}$$

$$\text{P.f} = 0.3 \text{ lagging}$$

$$Z = ?$$

For Δ system:

$$V_L = V_{ph} = 500 \text{ V}$$

$$I_L = \sqrt{3} I_{ph}$$

$$\therefore I_{ph} = \frac{I_L}{\sqrt{3}}$$

Now, we know that:

$$I_{ph} = \frac{V_{ph}}{Z}$$

$$\therefore I_L = \frac{500}{Z}$$

$$\therefore \frac{20}{\sqrt{3}} = \frac{500}{Z}$$

$$I_{ph} = 20/\sqrt{3}$$

$$\therefore [I_{ph} = 11.54 \text{ A}]$$

We have:

$$Z = \frac{V_{ph}}{I_{ph}}$$

$$= \frac{500}{11.54}$$

$$= 43.32 \Omega$$

$$\frac{R}{Z} = \cos \phi = \text{power factor}$$

$$\frac{x_L}{Z} = \sin \phi = \text{reactive factor}$$

$$Z = \frac{500\sqrt{3}}{20}$$

$$\therefore [Z_{ph} = 243.3 \Omega]$$

$$\text{Now, P.f} = 0.3$$

$$\text{or, } \cos \phi = 0.3$$

$$\text{or, } \phi = \cos^{-1}(0.3)$$

$$\therefore \phi = 72.54^\circ$$

Since, P.f is lagging, therefore ϕ is positive and Z is inductive.

$$\text{Now, Resistance (R)} = Z_{ph} \cos \phi \\ = 43.3 \times 0.3 \\ = 12.99 \Omega$$

$$\text{Inductance (X}_L\text{)} = Z_{ph} \sin \phi \\ = 43.3 \times \sin(72.54^\circ) \\ = 39.33 \Omega$$

$$\therefore \text{Required Impedance (Z)} = R + j X_L \\ = 12.99 + j 39.33 \\ = (41.41 \angle 79.69^\circ) \Omega$$

(A) Three equal impedance of $z = 10 \angle 30^\circ$ are connected in star/Hye across 400V 3 ϕ supply. What is the power taken from the supply if the same impedance are now connected in delta across same supply. Compare the results.

(2008, spring)
8 marks

P.T.O

Ans:

$$Z = 10 \angle 30^\circ$$

$$V_L = 400 \text{ V}$$

Star connection:

In this case; we have:

$$I_L = I_{ph} \text{ And, } V_L = \sqrt{3} V_{ph}$$

$$\Rightarrow V_{ph} = \frac{V_L}{\sqrt{3}}$$

$$\text{or, } V_{ph} = \frac{400}{\sqrt{3}}$$

$$\therefore V_{ph} = 230.94 \text{ V}$$

New, we know:

$$\begin{aligned} I_{ph} &= \frac{V_{ph}}{Z} \\ &= \frac{230.94}{10 \angle 30^\circ} \\ &= 23.09 \angle -30^\circ \end{aligned}$$

$$\therefore I_{ph} = I_L = 23.09 \angle -30^\circ$$

$$\therefore P = \sqrt{3} I_L V_L \cos \phi$$

$$\begin{aligned} &= \sqrt{3} \times 23.09 \times 400 \times \cos(0^\circ - 30^\circ) \\ &= \sqrt{3} \times 23.09 \times 400 \times \cos(0 + 30^\circ) \\ &= \sqrt{3} \times 23.09 \times 400 \times \cos(30^\circ) \\ &= 11445 \text{ kW} = 11445 \text{ W} \\ &= 13854 \text{ W} \end{aligned}$$

DATE _____
PAGE _____

Delta Connection:

In this case; we have:

$$V_L = V_{ph} = 400 \text{ V}$$

$$\text{And, } I_L = \sqrt{3} I_{ph}$$

$$= \sqrt{3} \times \frac{V_{ph}}{Z}$$

$$= \sqrt{3} \times \frac{400}{10 \angle 30^\circ}$$

$$\begin{aligned} &= \sqrt{3} \times 40 \angle -30^\circ \\ &= 69.28 \angle -30^\circ \end{aligned}$$

$$\therefore \text{Power (P)} = \sqrt{3} V_L I_L \cos \phi$$

$$\begin{aligned} &= \sqrt{3} \times 400 \times 69.28 \times \cos(0 + 30^\circ) \\ &= \sqrt{3} \times 400 \times 69.28 \times \cos(30^\circ) \\ &= 4276 \text{ kW} = 4276 \text{ W} \end{aligned}$$

Three equal impedance having resistance of 8Ω and inductance of 6Ω are connected in series across a three phase $400 \text{ V}, 50 \text{ Hz}$ supply. If it is connected to (i) star (γ) (ii) Delta (Δ)

Determine: (i) Phase Current

(ii) Line Current

(iii) Power consumed in each case.

Ans:

Here,

$$\begin{aligned} Z &= (8 + j6) \Omega \\ &= 10 \angle 40.96^\circ \end{aligned}$$

$$\begin{aligned} V_L &= 400 \text{ V} \\ f &= 50 \text{ Hz} \end{aligned}$$

(i) Star: In this case:

$$V_L = \sqrt{3} V_{ph}$$

$$\text{A}, V_{ph} = \frac{V}{\sqrt{3}}$$

$$\text{B}, V_{ph} = \frac{400}{\sqrt{3}}$$

$$V_{ph} = 230.99 \text{ V}$$

$$\text{A}, I_L = I_{ph} = \frac{V_{ph}}{Z}$$

$$= \frac{230.99}{10 \angle -40.96}$$

$$I_{ph} = I_L = 23.09 \angle -40.96$$

Now,

$$\text{Power consumed } (P) = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 23.09 \times \cos(0 + 40.96)$$

$$= \sqrt{3} \times 400 \times 23.09 \times \cos(90.96)$$

$$= 12.79 \text{ kW}$$

(ii) Delta:

In this case:

$$V_L = V_{ph} = 400 \text{ V}$$

$$\text{A}, I_L = \sqrt{3} I_{ph}$$

$$= \sqrt{3} \times \frac{V_{ph}}{Z}$$

$$I_{ph} \times 400$$

$$40 \angle -40.96$$

$$= \sqrt{3} \times \frac{100}{10 \angle 40.96}$$

$$= \sqrt{3} \times 90 \angle -40.96$$

$$= 69.28 \angle -40.96$$

$$\therefore I_L = 69.28 \angle -40.96$$

$$\text{And, } I_{ph} = \frac{V_{ph}}{Z}$$

$$= \frac{400}{10 \angle 40.96}$$


$$I_{ph} = 40 \angle -40.96$$

$$\text{Now, power consumed } (P) = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 69.28 \times \cos(90.96)$$

$$= 38.90 \text{ kW}$$

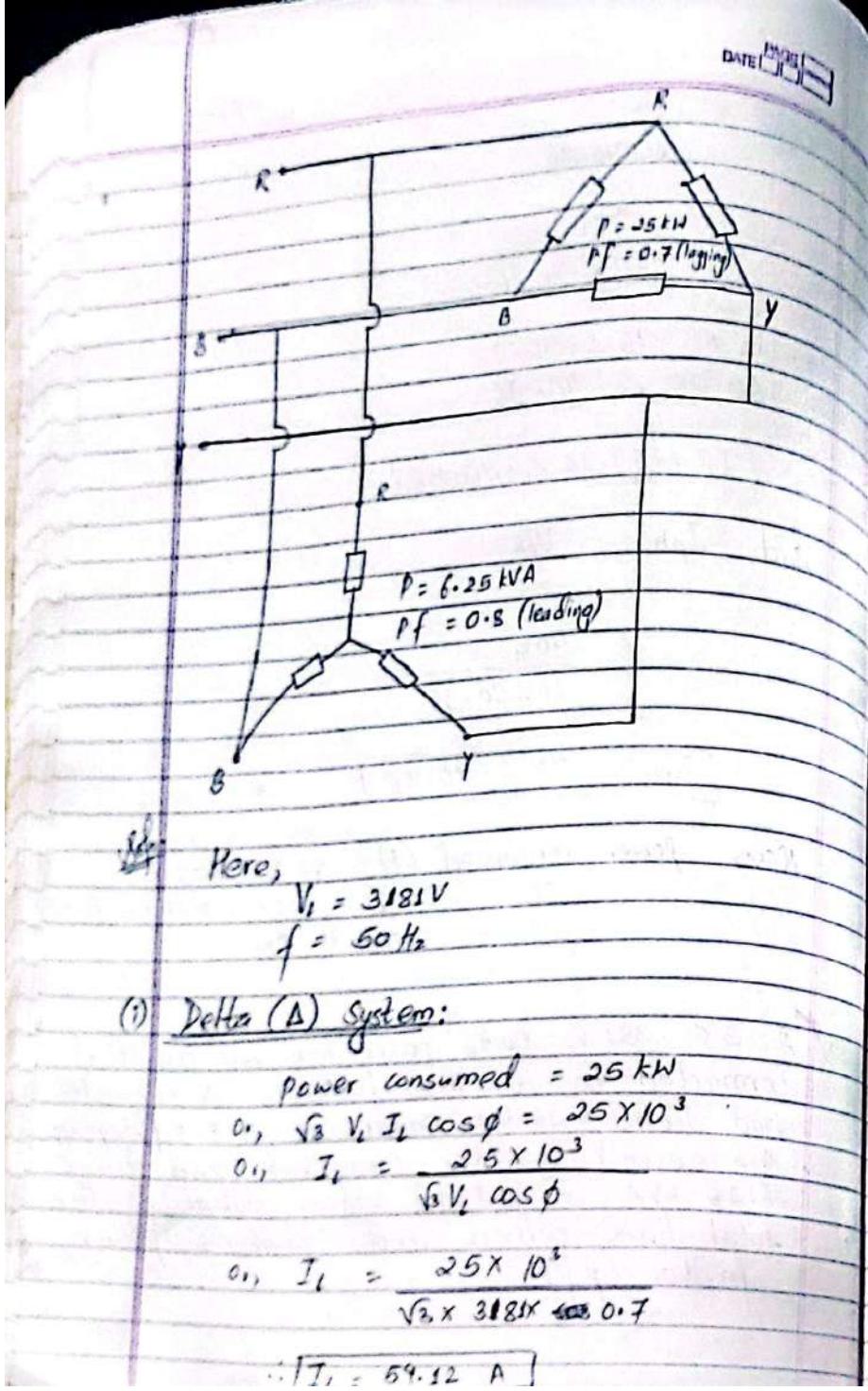Q. A 3-Ø 381 V, 50 Hz power line has two loads connected to it. The first is Δ connected and draws 25 kW power at 0.7 p.f lagging, the second is star connected and draws 6.25 kVA at 0.8 p.f leading. What is the total line current and combine power factor (p.f.)?



Now, $P_f = \cos \phi$

$$\text{or, } 0.7 = \cos \phi$$

$$\text{or, } \phi = \cos^{-1}(0.7)$$

$$\therefore \boxed{\phi = 45.57}$$

(Lagging so it is +ve)

$$\therefore \phi = \theta_v - \theta_i$$

$$\text{or, } 45.57 = \theta_v - \theta_i$$

$$\text{or, } 45.57 = -\theta_i$$

$$\therefore \boxed{\theta_i = -45.57}$$

$$\therefore (I_L)_A = 54.12 \angle -45.57$$

(ii) Star (Y) system:

Power consumed = 6.25 kVA (apparent power)

$$\text{or, } \sqrt{3} V_L I_L = 6.25 \times 10^3 \text{ VA}$$

$$\text{or, } I_L = \frac{6.25 \times 10^3}{\sqrt{3} V_L}$$

$$\text{or, } I_L = \frac{6.25 \times 10^3}{\sqrt{3} \times 381}$$

$$\therefore \boxed{I_L = 9.47 \text{ A}}$$

$P_f = 0.8$ leading means $\phi = -\text{ve}$

which also means capacitive ckt.

so, $P_f = \cos(-\phi)$

$$\text{or, } 0.8 = \cos(-\phi)$$

$$\text{or, } -\phi = \cos^{-1}(0.8)$$

$$\therefore \boxed{\phi = -36.87}$$

(leading so it is -ve)

$$\therefore \phi = \theta_v - \theta_i$$

$$\text{or, } -40.96 = -\theta_i \quad \therefore \boxed{\theta_i = 40.96}$$

$$(I_L)_P = 9.47 \angle 36.87^\circ$$

$$\text{Hence, } (I_L)_{\text{tot}} = 9.47 \angle -40.96^\circ$$

DATE _____ PAGE _____

$$\therefore \text{Total current } (I_L) = (I_L)_D + (I_L)_P$$

$$= (54.12 \angle -45.57^\circ) + (9.47 \angle 36.87^\circ)$$

$$= (54.02 \angle 47^\circ) \angle (-35.07 \angle 30.93^\circ)$$

$$\Rightarrow = (40.83 - j35.51) + (7.57 + j5.3)$$

$$= 48.4 - j29.83$$

$$= 56.85 \angle -35.16^\circ$$

Combined power factor :

$$\cos \phi = \cos(\theta_V - \theta_I)$$

$$= \cos(0 - (-35.16))$$

$$= \cos(35.16)$$

$$= 0.85$$

Electric Machines

Transformer :

(i) 55 kVA transformer has 500 turns on primary winding & 40 turns on secondary winding. The primary winding is connected with 3.3 kV. Calculate

- (i) Primary & secondary current
- (ii) Secondary emf
- (iii) Maximum emf

(q) core loss \Rightarrow due to hysteresis & eddy currents = constant quantity
 copper loss \Rightarrow due to the currents flowing in the primary & secondary windings = has two components

voltage regulation : The way in which the secondary terminal voltage varies with the load depends on the load current, the internal impedance and the load power factor. The change in secondary terminal voltage from no-load to full load at any particular load is termed regulation. It is usually expressed as percentage of the rated no load terminal voltage.

$$\text{Voltage regulation} = \frac{\text{no-load output voltage} - \text{full-load output voltage}}{\text{full-load output voltage}} \times 100\%$$

$$= \frac{V_2(NL) - V_2(FL)}{V_2(FL)} \times 100\%$$

Transformer Efficiency:

The efficiency of a transformer is given by,

$$\text{Efficiency } (\eta) = \frac{P_o}{P_i} \times 100\%$$

$$\eta = \frac{V_2 I_2 \cos \theta_2}{V_1 I_1 \cos \theta_1} \times 100\%$$

Since $P_i = P_o + \text{losses}$

$$\therefore \eta = \frac{P_o}{P_o + \text{losses}} \times 100\%$$

$$\text{or, } \eta = \frac{V_2 I_2 \cos \theta_2}{V_2 I_2 \cos \theta_2 + I_1^2 R_1 + I_2^2 R_2 + P_c}$$

$$\text{or, } E_2 = \frac{3.3 \times 10^3 \times 40}{V_2 I_2 \cos \theta_2 + I_1^2 R_1 + I_2^2 R_2 + P_c} \quad \therefore E_2 = 264$$

Q) A 25 kVA transformer has 500 turns on primary winding & 40 turns on secondary winding. The primary voltage is connected with 3.3 KV. Calculate
 ① Primary and secondary currents
 ② Secondary emf

Given:
 Apparent power (S) = $25 \text{ kVA} = 25 \times 10^3 \text{ VA}$
 Primary voltage (E_1) = $3.3 \text{ KV} = 3.3 \times 10^3 \text{ V}$
 No. of turns in primary side (N_1) = 500
 No. of turns in secondary side (N_2) = 40
 Primary current (I_1) = ?
 Secondary current (I_2) = ?
 Secondary emf (E_2) = ?
 Maximum flux (Φ_{max}) = ?

We know,

$$S = E_1 I_1$$

$$\therefore 25 \times 10^3 = E_1 I_1$$

$$\therefore I_1 = \frac{25 \times 10^3}{3.3 \times 10^3}$$

$$I_1 = 7.58 \text{ A}$$

$$\therefore \frac{I_2}{I_1} = \frac{N_1}{N_2}$$

$$= 10$$

$$\therefore I_2 = \frac{N_1 \times I_1}{N_2}$$

$$= \frac{500 \times 7.58}{40}$$

$$= 94.69 \text{ A}$$

Again, the relationship between Voltages & turns is:

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\therefore \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$E_2 = \frac{3.3 \times 10^3 \times 40}{500}$$

$$= 264 \text{ V}$$

for maximum emf.

The emf equation of transformer is,

$$E = 4.44 f N_1 \Phi_{max}$$

$$\Phi_{max} = \frac{E_1}{4.44 \times 50 \times 600} \quad [\because f = 50 \text{ Hz}]$$

$$= \frac{3.3 \times 10^3}{4.44 \times 50 \times 600} = 0.029 \text{ Wb}$$

$$\therefore E_2 = \frac{3.3 \times 10^3 \times 40}{500} \quad \therefore E_2 = 264$$

Q2 A 30kVA 2400/120 V load, 50Hz transformer has high voltage winding resistance of 0.1Ω and leakage resistance of 0.22Ω . The low voltage winding resistance is 0.035Ω and leakage reactance of 0.012Ω . Find the equivalent winding resistance, reactance and impedance referred to high voltage side and low voltage side.

Given,

$$\text{Apparent power} (S) = 30 \text{ kVA}$$

$$\text{primary/secondary voltages} = 2400/120 \text{ V} (E_1/E_2)$$

$$\text{frequency} (f) = 50 \text{ Hz}$$

$$\text{primary resistance} (R_1) = 0.1\Omega$$

$$\text{" reactance} (X_1) = 0.22\Omega$$

$$\text{secondary resistance} (R_2) = 0.035\Omega$$

$$\text{" reactance} (X_2) = 0.012\Omega$$

To calculate

on high voltage/primary side:

$$\text{equivalent resistance } (R_{eq}) = ?$$


$$\text{" reactance} (X_{eq}) = ?$$

$$\text{" impedance} (Z_{eq}) = ?$$

Now,

$$\text{transformation ratio} (k) = \frac{E_2}{E_1} = \frac{120}{2400} = 0.05$$

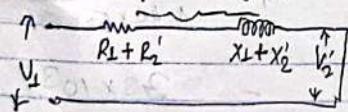The equivalent ckt of transformer referred to primary



First

$$R_{eq} = R_1 + R_2' = ?$$

$$X_{eq} = X_1 + X_2' = ?$$

$$Z_{eq} = R_{eq} + jX_{eq} = ?$$

first

$$R_2' = \frac{R_2}{k^2} \quad (\text{transferred from secondary to primary})$$

$$= 0.035$$

$$0.052$$

$$= 14\Omega$$

$$R_{eq} = 0.1 + 14$$

$$= 14.1\Omega$$

Now

$$X_{eq} = X_1 + X_2'$$

$$= 0.012 + X_2/k^2 = 0.22 + 0.012/0.05^2$$

$$= 0.012 + 0.012 = 5.02\Omega$$

$$Z_{eq} = R_{eq} + jX_{eq}$$


$$= 14.1 + j5.02$$

$$= 14.96 + j9.5$$

$$or, E_2 = \frac{3.3 \times 10^{-3} \times 40}{500} \therefore E_2 = 264$$

Date: 20/11/2023

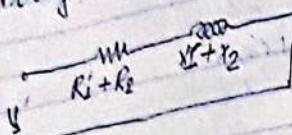the equivalent circuit of transformer referred to secondary side:



$$\begin{aligned}
 R_{eq} &= R'_1 + R_2 \\
 &= R_1 k^2 + R_2 \\
 &= 0.1 \times 0.05^2 + 0.035 \\
 &= 0.03525 \Omega
 \end{aligned}$$

$$\begin{aligned}
 X_{eq} &= X'_1 + X_2 \\
 &= X_1 k^2 + X_2 \\
 &= 0.22 \times 0.05^2 + 0.012 \\
 &= 0.01255 \Omega
 \end{aligned}$$

Equivalent impedance referred to secondary is

$$\begin{aligned}
 Z_{eq} &= R_{eq} + jX_{eq} \\
 &= 0.03525 + j0.01255 \\
 &= 0.037 \angle 19.5^\circ
 \end{aligned}$$

- Ques 3) A single phase transformer has 1000 turns in primary and 200 turns on secondary. The no load power factor of 0.2 lagging. calculate primary current when the secondary current at power factor of 0.8 lagging.

Given

- $N_1 = 1000$ = primary turns
- secondary turns (N_2) = 200
- no-load current (I_0) = 3A
- power factor at primary ($\cos\phi_0$) = 0.2

$$\begin{aligned}
 \cos\phi_0 &= 0.2 \\
 \phi_0 &= \cos^{-1}(0.2)
 \end{aligned}$$

$$= 78.46$$

$$I_0 = 3 \angle 78.46$$

Again

Given, Secondary current (I_2) = 280A
Secondary power factor ($\cos\phi_2$) = 0.8 lagging

$$\cos\phi_2 = 0.8$$


$$\phi_2 = \cos^{-1}(0.8)$$

$$= 36.87$$

$$I_2 = 280 \angle 36.87$$

$$\alpha_1 E_2 = \frac{3.3 \times 10^3 \times 40}{500} \quad \therefore E_2 = 264$$

g

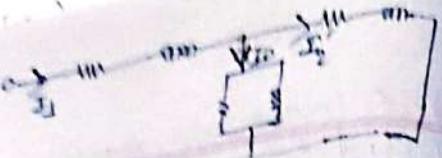

Now, to calculate primary current.

(1) First, $I_2' = I_2/k$ $I_2' = I_2 K$ $\therefore N_1 I_2' = N_2 I_2$
 $\therefore I_2' = k \cdot I_2$

Where, $k = \frac{N_2}{N_1} = \frac{500}{1000} = \frac{5}{5} = 0.2$

$$\begin{aligned}\therefore I_2' &= I_2 K \\ &= 280 \angle 36.87^\circ \times 0.2 \\ &= 56 \angle 36.87^\circ\end{aligned}$$

We know,

$$\begin{aligned}I_1 &= I_0 + I_2' \\ &= 56 \angle 36.87^\circ + 3 \angle 78.46^\circ \\ &= 58.27 \angle 38.82^\circ A\end{aligned}$$

Now, $E_2 = \frac{3.3 \times 10^3 \times 40}{500} \therefore E_2 = 264$

Ques. The primary and secondary winding of 500 KVA, 1-phi transformer have resistance of 0.4 ohm and 0.0015 ohm respectively. The primary and secondary voltages are 6000 and 400 respectively and iron loss is 3.2 kW. calculate the efficiency on

i) full load
ii) half load assuming the pf of the load to be 0.8

Given,

$$\text{Apparent power } (S) = 500 \text{ KVA} = 500 \times 10^3 \text{ VA}$$

$$\text{primary resistance } (R_1) = 0.4 \Omega$$

$$\text{secondary " } (R_2) = 0.0015 \Omega$$

$$\text{primary voltage } (E_1) = 6000 \text{ V}$$

$$\text{secondary " } (E_2) = 400 \text{ V}$$

$$\text{iron loss (or core loss) } (P_c) = 3.2 \text{ kW} = 3.2 \times 10^3 \text{ W}$$

$\eta = ?$ for full load ckt &
 $\eta = ?$ for half load " of transformer
power factor ($\cos\phi$) = $\cos\phi = 0.8$

We know,

$$\text{efficiency } (\eta) = \frac{\text{output voltage}}{\text{output voltage + losses}} \times 100$$

$$= \frac{V_2 I_2 \cos\phi}{V_2 I_2 \cos\phi + I_2^2 R_2 + I_2^2 R_1 + P_c}$$

Where,

$$\cos\phi = 0.8$$

$$S = E_1 I_1$$

$$500 \times 10^3 = 6000 \times I_1$$

$$\therefore I_1 = 83.33 \text{ A}$$

∴ Also,

$$S = E_2 I_2$$

$$\frac{500 \times 10^3}{400} = I_2$$

$$I_2 = 1250 \text{ A}$$

$$\eta = \frac{V_2 I_2 \cos\phi}{V_2 I_2 \cos\phi + I_2^2 R_2 + I_2^2 R_1 + P_c} \times 100$$

$$= \frac{400 \times 1250 \times 0.8}{400 \times 1250 \times 0.8 + 23.33^2 \times 0.4 + 1250^2 \times 0.0015 + 3.2 \times 10^3}$$

$$= 0.979 \times 100$$

$$\eta = 97.96\% \text{ Ans}$$

ii) for half load, then

$$S = \frac{500 \text{ KVA}}{2} = 250 \text{ KVA} = 250 \times 10^3 \text{ VA}$$

Again,

$$250 \times 10^3 = E_1 I_1$$

$$\therefore I_1 = \frac{250 \times 10^3}{6000} = 41.67 \text{ A}$$

$$I_2 = \frac{250 \times 10^3}{400} = 625 \text{ A}$$

$$\eta = \frac{E_2 I_2 \cos\phi}{E_2 I_2 \cos\phi + I_2^2 R_2 + I_2^2 R_1 + P_c} \times 100$$

$$= \frac{400 \times 625 \times 0.8}{400 \times 625 \times 0.8 + 41.67^2 \times 0.4 + 625^2 \times 0.0015 + 3.2 \times 10^3} = 95.411\%$$

$$E_1 \quad E_2 = \frac{3.3 \times 10^3 \times 40}{6000} \quad \therefore E_2 = 264$$

Here,

$$\begin{aligned}\text{Apparent power} &= 25 \text{ kVA} = 25 \times 10^3 \text{ VA} \\ \text{Primary voltage } (V_1 \text{ or } E_1) &= 3.3 \text{ kVA} = 3.3 \times 10^3 \text{ VA} \\ \text{No. of turns in Primary } (N_1) &= 500 \\ \text{No. of turns in Secondary } (N_2) &= 40\end{aligned}$$

$$\begin{aligned}\text{Primary current } (I_1) &=? \\ (\text{Secondary current } I_2) &=?\end{aligned}$$

$$\begin{aligned}\text{Secondary Emf } (E_2) &=? \\ \text{Maximum Emf } (\phi_{max}) &=?\end{aligned}$$

Now,

$$\therefore A.P = V_1 I_1$$

$$\text{or, } 25 \times 10^3 = 3.3 \times 10^3 \times I_1$$

$$\text{or, } I_1 = \frac{25 \times 10^3}{3.3 \times 10^3}$$

$$\therefore I_1 = 7.58$$

$$\therefore \frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$\text{or, } I_2 = \frac{I_1 N_1}{N_2}$$

$$\text{or, } I_2 = \frac{7.58 \times 500}{40}$$

$$\therefore I_2 = 94.75$$

Again,

$$\therefore \frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\text{or, } E_2 = \frac{E_1 N_2}{N_1}$$

$$\text{or, } E_2 = \frac{3.3 \times 10^3 \times 40}{500} \quad \therefore E_2 = 264$$

Eq. equation of transformer is:

$$E = 4.44 f N_1 \Phi_{max}$$

$$\text{or, } \Phi_{max} = \frac{E_1}{4.44 f N_1}$$

$$\text{or, } \Phi_{max} = \frac{3.3 \times 10^4}{4.44 \times 50 \times 500}$$

$$\therefore \Phi_{max} = 0.029 \text{ Tesla}$$

- (Q) A 30 kVA 2900/120 V lead, 50 Hz transformer has a high voltage winding resistance of 0.152 and leakage resistance of 0.22 Ω. The low voltage winding resistance is 0.035 Ω and leakage reactance 0.012 Ω. Find the equivalent winding resistance, reactance and impedance referred to high voltage side and low voltage side.

Ans:

$$\text{Primary Resistance } (R_1) = 0.1 \Omega$$

$$\text{Primary Reactance } (X_1) = 0.22 \Omega$$

$$\text{Secondary Resistance } (R_2) = 0.035 \Omega$$

$$\text{Secondary Reactance } (X_2) = 0.012 \Omega$$

Eq. Winding Resistance referred to primary (R'_1) =

Eq. Winding Reactance referred to primary (X'_1) =

Eq. Winding Impedance referred to primary (Z'_1) =

Eq. Winding Resistance referred to secondary (R'_2) =

Eq. Winding Reactance referred to secondary (X'_2) =

Eq. Winding Impedance referred to secondary (Z'_2) = ?

Now, Voltage Transformation ratio:

$$k = \frac{E_2}{E_1} = \frac{120}{2900} = 0.05$$

Now, Eq. Resistance referred to Primary:

$$\begin{aligned} R'_1 &= R_1 + R_2 \\ &= 0.1 + \frac{R_2}{k^2} \\ &= 0.1 + \frac{0.035}{(0.05)^2} \\ &= 14.1 \Omega \end{aligned}$$

Eq. reactance referred to Primary:

$$\begin{aligned} X'_1 &= X_1 + X_2 \\ &= X_1 + \frac{X_2}{k^2} \\ &= 0.22 + \frac{0.012}{(0.05)^2} \\ &= 5.02 \Omega \end{aligned}$$

P.I.O
Eq. Impedance referred to primary:

$$\begin{aligned} Z'_1 &= \sqrt{R'^2 + X'^2} \\ &= \sqrt{(14.1)^2 + (5.02)^2} \\ &= \sqrt{(14.1)^2 + (5.02)^2} \\ &= \sqrt{202.401} \\ &= 14.17 \Omega \end{aligned}$$

Eq. Impedance referred to primary:

$$Z_1' = R_1 + jX_1'$$
$$= 39.1 + j5.02$$
$$= 41.96 \angle 19.5^\circ$$

Now,

Eq. resistance referred to secondary:

$$R_2' = R_2 + R_1' k^2$$
$$= R_2 + R_1 \times k^2$$
$$= 0.035 + 0.1 \times (0.05)^2$$
$$= 0.03525 \Omega$$

Eq. reactance referred to secondary:

$$X_2' = X_2 + X_1' k^2$$
$$= X_2 + X_1 \times k^2$$
$$= 0.012 + 0.2 \times (0.05)^2$$
$$= 0.01255 \Omega$$

Eq. Impedance referred to secondary:

$$Z_2' = R_2' + jX_2'$$
$$= 0.03525 + j0.01255$$
$$= 0.037 \angle 19.5^\circ$$

A 50kVA 4400/200V load transformer has the parameters $R_1 = 3.45 \Omega$, $R_2 = 0.009 \Omega$, $X_1 = 5.2 \Omega$, $X_2 = 0.015 \Omega$. Calculate the transformer's

Eq. resistance as referred to Primary (R_1') and secondary (R_2').

Eq. resistance as referred to primary (R_1') & secondary (X_2').

Eq. Impedance as referred to primary & secondary (Z_2').

Here,

$$R_1 = 3.45 \Omega$$

$$X_1 = 5.2 \Omega$$

$$R_2 = 0.009 \Omega$$

$$X_2 = 0.015 \Omega$$

Now, Voltage Transformation ratio:

$$K = \frac{E_2}{E_1} = \frac{200}{4400} = 0.045$$

Now,

Eq. resistance as referred to primary:

$$R_1' = R_1 + R_2' k^2$$
$$= R_1 + \frac{R_2}{K^2}$$
$$= 3.45 + \frac{0.009}{(0.045)^2}$$
$$= 7.89 \Omega$$

Eq. reactance as referred to primary:

$$\begin{aligned} X'_s &= X_s + X'_1 \\ &= X_s + \frac{R_s}{k^2} \\ &= 5.2 + \frac{0.015}{(0.045)^2} \\ &= 12.6 \Omega \end{aligned}$$

Eq. Impedance referred to primary:

$$\begin{aligned} Z'_s &= R'_s + jX'_s \\ &= 7.89 + j12.6 \\ &= 19.86 \angle 57.9^\circ \end{aligned}$$

Eq. resistance as referred to secondary:

$$\begin{aligned} R'_2 &= R_2 + R'_1 \\ &= R_2 + R_1 \times k^2 \\ &= 0.009 + 3.45 \times (0.045)^2 \\ &= 15.98 \times 10^{-3} \Omega \end{aligned}$$

Eq. reactance as referred to secondary:

$$\begin{aligned} X'_2 &= X_2 + X'_1 \\ &= X_2 + X_1 \times k^2 \\ &= 0.015 + 5.2 \times (0.045)^2 \\ &= 25.53 \times 10^{-3} \Omega \end{aligned}$$

Eq. Impedance referred to secondary:

$$\begin{aligned} Z'_2 &= R'_2 + jR_2 X'_2 = (15.98 \times 10^{-3}) + j(25.53 \times 10^{-3}) \\ &= 0.03 \angle 57.95^\circ \end{aligned}$$

Numericals of s.c & o.c test are of 1000 PAGE 8

$$\begin{aligned} R'_{sc} &= 15 \text{ m} \Omega \quad X'_{sc} = 34 \text{ m} \Omega \\ B' &= 14.475 \text{ T} \quad Z = 3 X_s = 5.85 \text{ k} \Omega \end{aligned}$$

Emf equation of dc machine:

- (b) A 8 pole dc generator running at 1200 rpm with a flux of 25 mwb per pole generates 440V. calculate the no. of conductor if the armature is (i) lap winding/wounded (ii) wave winding/ "

Here,

$$\begin{aligned} \text{No. of magnetic pole (p)} &= 8 \\ \text{speed of armature (N)} &= 1200 \text{ rpm} \\ \text{magnetic flux per pole (\phi)} &= 25 \text{ mwb} \\ &= 25 \times 10^{-3} \text{ wb} \end{aligned}$$

Back emf (E_b) = 440 V

No. of conductor in armature (z) = ?

For lap winding:

$$A = P = 16 \Omega$$

$$\therefore E_b = \frac{z \phi N}{60} \times \frac{P}{A}$$

$$\text{or, } 440 = \frac{z \times 25 \times 10^{-3} \times 1200}{60} \times \frac{8}{16}$$

$$\frac{440 \times 60}{25 \times 10^{-3} \times 1200} \times 1$$

$\therefore z = 800$

(i) for pole winding:

$$A = 2$$

$$P = 8$$

$$\therefore E_b = \frac{z d N}{60} \times \frac{P}{A}$$

$$\therefore 440 = \frac{z \times 25 \times 10^{-3} \times 1200}{60} \times \frac{8}{2}$$

$$(ii) z = \frac{440 \times 60 \times 2}{25 \times 10^{-3} \times 1200 \times 8}$$

$$z = 220$$

Long shunt compound Generator:

- (ii) A long shunt compound generator delivers 60A to the load at 220V. calculate the emf generated by the armature given that armature winding resistance 0.04Ω, series field resistance 0.06Ω & shunt field winding resistance 110Ω.


Now,

$$\text{load current } (I_L) = 60A$$

$$\text{terminal voltage } (V) = 220V$$

DATE _____
PAGE NO. _____

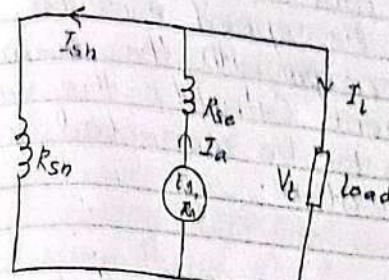Armature resistance (R_a) = 0.04Ω
 series field resistance (R_{se}) = 0.06Ω
 shunt field resistance (R_{sh}) = 110Ω
 Emf generated (E) = ?



We know, for long shunt compound generator, emf induced is:

$$E = V_t + I_a R_a + I_s R_{se} \quad \dots \dots \dots (1)$$

$$\begin{aligned} \therefore V_t &= E - I_a R_a - I_s R_{se} \\ \Rightarrow V_t + I_a R_a + I_s R_{se} &= E \end{aligned}$$

$$\begin{aligned} I_a &= I_{sh} + I_L \\ &= \frac{60}{R_{sh}} + \frac{220}{110} + 60 \\ &= \frac{220}{110} + 60 \\ &= 62A \end{aligned}$$

$$\begin{aligned} \therefore E &= 220 + (62 \times 0.04) + (62 \times 0.06) \\ &= 226.2V \end{aligned}$$

Speed control of dc motor

- (Q) A 220v shunt motor runs at 1450 rpm of full load with an armature current of 11A. The total resistance of armature is 0.6Ω. If the speed is to be reduced to 1000 rpm with the same armature current, calculate the value of resistance to be connected in series with the armature.

Sol: Here,
 supplied voltage (V) = 220V
 no. full load speed (N_1) = 1450 rpm
 no. full load current (I_a) = 11 A
 initial Armature resistance (R_a) = 0.6Ω
 no load speed (N_2) = 1000 rpm
 final Armature current (I_{a2}) = 11 A
 variable Resistance (R_v) = ?

Now, we have:

$$\frac{N_2}{N_1} = \frac{V - I_{a2}(R_a + R_v)}{V - I_a R_a}$$

$$\frac{1000}{1450} = \frac{220 - 11(0.6 + R_v)}{220 - 11 \times 0.6}$$

$$\frac{1000 \times 213.4}{1450} = 220 - 6.6 - 11 R_v$$


$$\frac{213400}{1450} - 220 + 6.6 = -11 R_v$$

$$\frac{-960.30}{1450} \times \frac{1}{-11} = R_v$$

$$R_v = 6.02 \Omega$$

- (Q) A 220v dc has no load speed of 800 rpm and armature current of 2A. calculate the resistance required to insert in series with the field winding resistance so that the motor may run at the speed of 1000 rpm taking the line current of 30A. The armature and field winding resistance are 0.4Ω & 165Ω respectively.

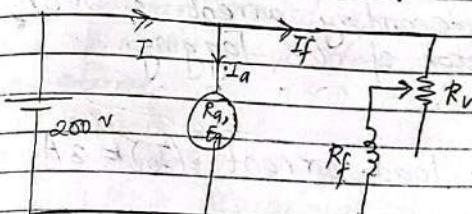Sol: Here,
 supplied voltage (V) = 220V
 no load speed (N_1) = 800 rpm
 Armature current (I_a) = 2A
 full load speed (N_2) = 1000 rpm
 line current (I) = 30 A
 Armature resistance (R_a) = 0.4Ω
 field winding resistance (R_f) = 165Ω
 Resistance to insert in series to increase the speed (R_v) = ?



$$I_a = I_o + I_f$$

$$I_f = \frac{V}{R_f + R_v}$$

we have:

$$\begin{aligned} J &= J_0 + I_f \\ \therefore 30 &= 3 + I_f \\ \therefore I_f &= 30 - 3 \\ \therefore I_f &= 28 \text{ A} \end{aligned}$$

Again,

$$I_f = \frac{V}{R_f + R_p}$$

$$\therefore I_f = \frac{220}{R_p + 165}$$

$$\therefore 28R_p + 4620 = 220$$

$$\therefore R_p = 220 - 4620$$

28

$$\therefore I_f R_p = -157.14 \text{ S.A.}$$

Transformer:

- (12) A single phase transformer has 1000 turns on primary and 500 turns on secondary. The no load current is 3A at a power factor of 0.2 lagging.

Calculate the primary current when the secondary current is 280A at power factor of 0.8 lagging.

Sol:

Here,

$$\text{No load current } (J_0) = 3 \text{ A}$$

P.f at primary $\cos\phi_0 = 0.2$

$$\therefore \phi_0 = \cos^{-1}(0.2)$$

$$\therefore \phi_0 = 78.46$$

$$\therefore J_0 = 3 \angle 78.46$$

Now,

$$J_0 = 280 \text{ A}$$

P.f at secondary $\cos\phi_2 = 0.8$

$$\text{or } \phi_2 = \cos^{-1}(0.8)$$

$$\therefore \phi_2 = 36.87$$

$$\therefore J_2 = 280 \angle 36.87 \quad (V_2 \text{ is taken as reference})$$

$$\& J_2 = J_0 \times K \angle 36.87$$

$$\text{where } K = \frac{N_2}{N_1} = \frac{500}{1000} = 0.2$$

$$\therefore J_2' = (280 \times 0.2) \angle 36.87$$

$$= 56 \angle 36.87$$

$$\begin{aligned} \text{Now, } J_1 &= J_0 + J_2' \\ &= 36 \angle 36.87 + 3 \angle 78.46 \\ &= 58.27 \angle 38.82 \quad \text{Ans} \end{aligned}$$

- (13) The primary and secondary winding of a 500kVA, 1-φ transformer have resistance of 0.4Ω and 0.0015Ω respectively. The primary and secondary voltages are 6000V and 400V respectively and iron loss is 3.2kW. Calculate the efficiency on full load

- (i) half load assuming the p.f of the load to be 0.8.

Q: Here,
 $S = 500 \text{ kVA} = 500 \times 10^3 \text{ VA}$
 primary voltage (V_1) = 6000 V
 Secondary voltage (V_2) = 400 V
 $R_1 = 0.4 \Omega$ & $R_2 = 0.0015 \Omega$
 We know that:

$$\text{Apparent power (S)} = V_1 I_1 = V_2 I_2$$

$$\therefore I_2 = \frac{S}{V_2} = \frac{500 \times 10^3}{400} = 1250 \text{ A}$$

$$\text{Now, } k = \frac{V_2}{V_1} = \frac{400}{6000} = 0.067$$

Ans: Total resistance referred to secondary side:

$$\begin{aligned} R'_2 &= R_2 + R_1 \times k^2 \\ &= R_2 + R_1 \times 0.067^2 \\ &= 0.0015 + 0.4 \times (0.067)^2 \\ &= 0.0032956 \\ &= 3.2956 \times 10^{-3} \Omega \end{aligned}$$

$$\begin{aligned} \text{full load copper loss (W}_c\text{)} &= I_2^2 R'_2 \\ &= (1250)^2 \times 3.2956 \times 10^{-3} \\ &= 5149.375 \text{ W} \\ &= 5.149 \text{ kW} \end{aligned}$$

$$\text{Iron loss (W}_{Fe}\text{)} = 3.2 \text{ kW}$$

DATE
 FACE
 full load output at 0.8 pf ie $\cos\phi = 0.8$

$$= S \times \cos\phi$$

$$= 500 \times 0.8$$

$$= 400 \text{ kW}$$

$$\text{efficiency } (\eta) = \frac{\text{output}}{\text{output} + \text{losses}} \times 100\%$$

$$= \frac{400}{400 + 3.2 + 5.149} \times 100\%$$

$$= 97.95\%$$

Output at half load at 0.8 pf ie $\cos\phi = 0.8$

$$= \frac{1}{2} \times \text{st} \cos\phi$$

$$= \frac{1}{2} \times 500 \times 0.8 = 200 \text{ kW}$$

Efficiency

$$\text{Copper loss at half load} = \left(\frac{1}{2}\right)^2 W_c$$

$$= \left(\frac{1}{2}\right)^2 \times 5.149$$

$$= 1.28725 \text{ kW}$$

$$\text{efficiency } (\eta) = \frac{\text{output}}{\text{output} + \text{iron loss} + \text{copper loss}} \times 100\%$$

$$= \frac{200}{200 + 3.2 + 1.28725} \times 100\%$$

$$= 97.85\%$$

Voltage Regulation: The way in which the secondary terminal voltage varies with the load depends on the load current, the internal impedance and the load power factor. The change in secondary terminal voltage from no load to full load at any particular load is termed regulation. It is usually expressed as a percentage of the rated no load terminal voltage.

$$\text{percentage regulation} = \frac{\text{terminal voltage on no-load} - \text{terminal voltage on load}}{\text{no-load terminal voltage}}$$

for lagging pf:

$$\% \text{ regulation} = \frac{I_2 R'_2 \cos \phi + I_2 X'_2 \sin \phi}{E_2} \times 100\%$$

$$= \left(\frac{I_2 R'_2 \cos \phi + I_2 X'_2 \sin \phi}{E_2} \right) \times 100\%$$

$$= \frac{I_2 R'_2 \times 100 \times \cos \phi + I_2 X'_2 \times 100 \times \sin \phi}{E_2}$$

$$= \% R \cos \phi + \% X \sin \phi$$

for leading pf:

$$\% \text{ Regulation} = \left(\frac{I_2 R'_2 \cos \phi - I_2 X'_2 \sin \phi}{E_2} \right) \times 100\%$$

The primary and secondary windings of 40 kVA, 6600/250 V, 1-φ transformer have resistance of 10Ω and 0.02Ω respectively. The total leakage reactance is 35Ω referred to the primary winding. Find the full load regulation at p.f of 0.8 lagging.

So:

$$S = 40 \text{ kVA} = 40 \times 10^3 \text{ VA}$$

$$R_1 = 10\Omega$$

$$R_2 = 0.02\Omega$$

$$V_1 = 6600 \text{ V}$$

$$V_2 = 250 \text{ V}$$

$$X'_2 = 35\Omega$$

$$\text{Now, } K = \frac{V_2}{V_1}$$

$$\therefore K = \frac{250}{6600}$$

$$\therefore K = 0.0378$$

$$I_2 = \frac{S}{V_2}$$

$$\therefore I_2 = \frac{40 \times 10^3}{250}$$

$$\therefore I_2 = 160 \text{ A}$$

Now, Eq. resistance referred to secondary:

$$R'_2 = R_2 + R_1$$

$$= R_2 + R_1 \times K^2$$

$$= 0.02 + 10 \times (0.0378)^2$$

$$= 0.020342 = 34.28 \times 10^{-3} \Omega$$

Eg. reactance referred to secondary:

$$\begin{aligned}x_s' &= x_2 + x_3' \\&= x_{\text{ext}} \times k^2 \\&= 0 + x_3 \times k^2 \\&= 35 \times (0.0378)^2 \\&= 50.0094 \times 10^{-3} \Omega\end{aligned}$$

Power factor = 0.8
 $\therefore \cos\phi = 0.8$

$$\sin\phi = \sqrt{1 - \cos^2\phi} = \sqrt{1 - (0.8)^2} = 0.6$$

full load regulation is given by:

$$\begin{aligned}&= \frac{I_2 R_2' \cos\phi + I_2 X_2' \sin\phi}{E_2} \times 100\% \\&= \frac{(60 \times 34.28 \times 10^{-3} \times 0.8) + (160 \times 50.0094 \times 10^{-3} \times 0.6)}{250} \times 100\% \\&= 3.67\%\end{aligned}$$

All day efficiency:

- (15) A 400 kVA distribution transformer has full load iron loss of 0.5 kW of copper loss of 3.5 kW. During a day, its load cycle per 24 hours is:

6 hrs 300 kVA at 0.8 p.f

4 hrs 1000 kVA at 0.9 p.f

Determine its all day efficiency.

Given:

$$\begin{aligned}P_F &= 0.5 \text{ kW} \\P_{Cu} &= 3.5 \text{ kW} \\V &= 100 \text{ kVA}\end{aligned}$$

∴ Iron losses is constant for 24 hrs. So energy spent due to iron (Fe) losses for 24 hrs is:

$$\begin{aligned}P_{Fe} &= 0.5 \times 24 \text{ hrs} \\&= 60 \text{ kWh}\end{aligned}$$

Total energy output in a day from give load cycle is:

$$\begin{aligned}\text{Energy output} &= 300 \times 6 \text{ hrs} + 200 \times 10 \text{ hrs} + \\&\quad 100 \times 4 \text{ hrs} \\&= 4800 \text{ kWh}\end{aligned}$$

To calculate energy spent due to copper loss:

(i) load 1 of 300 kW at p.f 0.8 ie $\cos\phi = 0.8$

$$\therefore \text{kVA supplied} = \frac{\text{kW}}{\cos\phi}$$

$$= \frac{300}{0.8} = 375 \text{ kVA}$$

$$\therefore \eta = \text{load kVA} / \text{kVA rating}$$

$$= \frac{375}{400} = 0.9375$$

Copper losses are proportional to square of kVA

ratio i.e. η^2

$$\therefore \text{load } 1 \text{ P}_{cu} = \eta^2 \times (P_{cu}) \\ = (0.9375)^2 \times 3.5 \\ = 3.076 \text{ kW}$$

$$\text{Energy spent} = 30.076 \times 6 \text{ hrs} \\ = 18.457 \text{ kWh}$$

(ii) load 2 of 200kW at $\cos\phi = 0.7$

$$\text{KVA supplied} = \frac{\text{kW}}{\cos\phi} \\ = \frac{200}{0.7} \\ = 285.71 \text{ KVA}$$

$$\eta = \frac{\text{load KVA}}{\text{KVA rating}} \\ = \frac{285.71}{400} \\ = 0.7142$$

$$\therefore \text{load } 2 \text{ P}_{cu} = \eta^2 \times (P_{cu}) \\ = (0.7142)^2 \times 3.5 \\ = 1.785 \text{ kW}$$

$$\therefore \text{Energy spent} = 1.785 \times 10 \\ = 17.85 \text{ kWh}$$

load 3 of 100kW at $\cos\phi = 0.9$

$$\text{KVA supplied} = \frac{\text{kW}}{\cos\phi} = \frac{100}{0.9} = 111.111 \text{ KVA}$$

$$\eta = \frac{\text{load KVA}}{\text{KVA rating}}$$

$$= \frac{100}{111.111} \\ = 0.2778$$

$$\therefore \text{load } 3 \text{ P}_{cu} = \eta^2 \times P_{cu} \\ = (0.2778)^2 \times 3.5 \\ = 0.2701 \text{ kW}$$

$$\text{Energy spent} = 0.2701 \times 4 \\ = 1.0804 \text{ kWh}$$

(iv) No load hence negligible copper losses.

Total energy spent = Energy spent due to
(Iron loss + Copper loss)

$$= 60 + 18.457 + 0.1785 + 1.0804 \\ = 97.3874 \text{ kWh}$$

and Total output = 4000 kWh

All day efficiency (η) = $\frac{\text{Total energy for 24 hrs} \times 100\%}{\text{Total output for 24 hrs} + \text{Total energy spent in 24 hrs}}$

$$\begin{aligned} & 4200 \\ & 4200 + 0.73874 \times 100 \times 1 \\ & = 57.73 \% \quad \underline{\text{Ans}} \end{aligned}$$

Open circuit and short circuit Test:

- ① The no load current of 1-φ transformer is 5 A at a power factor of 0.3. When supplied at 230 V, 50 Hz. The no. of turns in primary winding 200. calculate:
- max value of flux
 - Iron loss of transformer
 - Magnetizing current

Given: Here,
 No load current (I_0) = 5 A
 P.f. $\cos \phi = 0.3$
 Primary voltage (V_1) = 230 V
 Frequency (f) = 50 Hz
 No. of turns in primary winding (N_1) = 200
 Max value of flux $\Phi_{\max} = ?$
 Iron loss (P_{loss}) = ?
 Magnetizing current (I_u) = ?

Now, we know that:

$$E = 4.44 f N_1 \Phi_{\max}$$

$$\therefore \Phi_{\max} = \frac{E}{4.44 f N_1}$$

$$\therefore \Phi_{\max} = \frac{230}{4.44 \times 50 \times 200}$$

$$\therefore \Phi_{\max} = 5.18 \times 10^{-3} \text{ Tesla}$$

Now,

$$\begin{aligned} \text{Iron loss, } & V_1 I_0 \cos \phi \quad (I_w) = I_0 \cos \phi \\ & = 230 \times 5 \times 0.3 \\ & = 345 \text{ watt} \end{aligned}$$

$$\begin{aligned} I^2 &= I_0^2 + I_u^2 \\ I_u &= I_0 \cos \phi \quad | \quad I_u = I_0 \sin \phi \quad | \quad I^2 - I_0^2 = I_u^2 \\ &= 5 \times 0.3 \quad | \quad = 5 \times \sin \phi \quad | \quad I_u^2 = 25 - 2.25 \\ &= 1.5 \text{ A} \quad | \quad \therefore I_u = 4.76 \text{ A} \end{aligned}$$

- ② Calculate the open circuit parameters having 200/400 V, 50 Hz transformer with the given open circuit parameters.

O.C Test : 200 V 0.7 A 70W on L.V side

Given:
 Here,
 Open circuit voltage (V_1) = 200 V
 No load current (I_0) = 0.7 A
 Power (P_0) = 70 W

$$\begin{aligned} \text{Now, } & P_0 = V_1 I_0 \cos \phi \\ \text{or, } & 70 = 200 \times 0.7 \times \cos \phi \\ \text{or, } & \cos \phi = \frac{70}{200 \times 0.7} \\ \text{on } & \cos \phi = \frac{1}{2} \\ \therefore & \phi = 60^\circ \end{aligned}$$

$$\begin{aligned} I_w &= I_0 \cos \phi \\ &= 0.7 \times \cos 60^\circ = 0.35 \text{ A} \end{aligned}$$

$$I_{ul}/I_m = I_0 \sin \phi$$

$$= 0.7 \times \sin 60 = 0.61 A$$

$$R_o = \frac{V_1}{I_0} = \frac{200}{0.35} = 571.42 \Omega$$

$$X_o = \frac{V_1}{I_m} = \frac{200}{0.61} = 327.86 \Omega$$

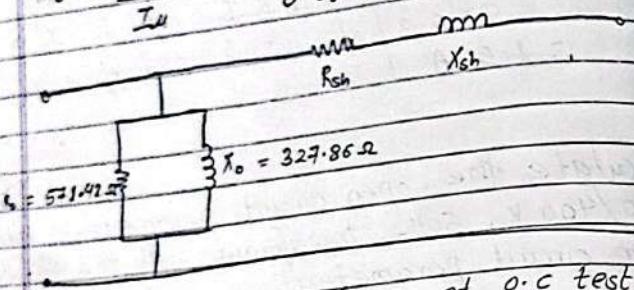


Fig: Eq. circuit of transformer at o.c test.



Note: Open Circuit Parameters:

$$I_{0o} = V_1 I_0 \cos \phi$$

$$I_0 = \sqrt{I_{ul}^2 + I_{0o}^2}$$

$$I_{0o} = I_0 \cos \phi$$

Given:

$$V_1 \text{ (o.c voltage)}$$

$$I_0 \text{ (no load current)}$$

$$W_o \text{ (power)}$$

$$I_{ul}/I_m = I_0 \sin \phi$$

$$R_o = \frac{V_1}{I_{0o}}$$

$$X_o = \frac{V_1}{I_m} \quad \text{or} \quad \frac{V_1}{I_{ul}}$$

Short circuit parameters:

Given:
 V_{sc} (s.c voltage)
 I_{sc} (s.c current)
 W_{sc} (s.c power)

$$R_{sc} = \frac{W_{sc}}{I_{sc}^2}$$

$$Z_{sc} = \frac{V_{sc}}{I_{sc}}$$

$$X_{sc} = \sqrt{Z_{sc}^2 - R_{sc}^2}$$

③ following data were obtained from the test of 30kVA, 2000/110 v, 50Hz 1φ transformer.

O.C Test : 110 v 10.2 A 350 W (L.V side)

S.C Test : 150 v 10 A 600 W (H.V side)

Calculate and draw the equivalent circuit referred to primary side.

For O.C Test (L.V side):

$$\text{O.C Voltage } (V_1) = 110 v$$

$$\text{No load current } (I_0) = 10.2 A$$

$$\text{Power } (W_o) = 350 W$$

$$\therefore W_o = V_1 I_0 \cos \phi$$

$$\text{on } \cos \phi = \frac{W_o}{V_1 I_0}$$

$$\cos \phi = \frac{350}{\sqrt{110} \times 10.2}$$

$$|\phi| = 71.82^\circ$$

$$\begin{aligned} Z_o &= I_o \cos \phi \\ &= 10.2 \times \cos(71.82) \\ &= 3.15 \text{ A} \end{aligned}$$

$$\begin{aligned} I_a/I_m &= I_o \sin \phi \\ &= 10.2 \times \sin(71.82) \\ &= 9.69 \text{ A} \end{aligned}$$

$$R_o = \frac{V_1}{I_o} = \frac{110}{3.15} = 34.59 \Omega$$

$$X_o = \frac{V_1}{I_m} = \frac{110}{9.69} = 11.35 \Omega$$

For S.C Test (H.V side):

secondary voltage (V_{sc}) = 150 V

$P_{sc} = 500 \text{ W}$

$I_{sc} = 10 \text{ A}$

$$\text{Now, } R_{sc} = \frac{P_{sc}}{I_{sc}^2} = \frac{500}{(10)^2} = 5 \Omega$$

$$Z_{sc} = \frac{V_{sc}}{I_{sc}} = \frac{150}{10} = 15 \Omega$$

$$\begin{aligned} X_{sc} &= \sqrt{Z_{sc}^2 - R_{sc}^2} \\ &= \sqrt{(15)^2 - (5)^2} = 14.14 \Omega \end{aligned}$$

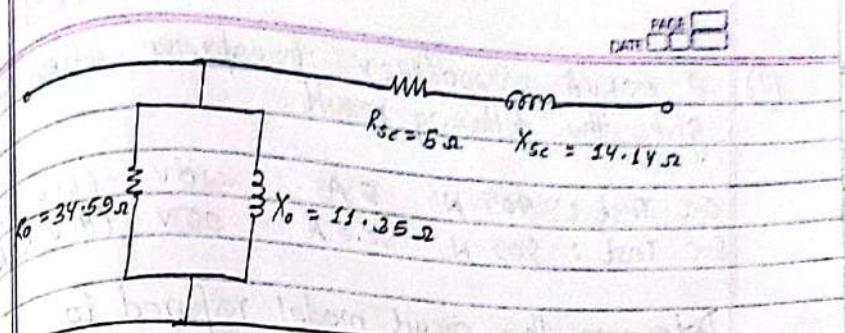


fig: Eq. circuit of transformer


Now, Circuit parameters referred to Primary side (L.V side - H.V side):

Voltage Transformation ratio:

$$k = \frac{E_2}{E_1} = \frac{110}{2000} = 0.055$$

$$R'_o = \frac{R_o}{k^2} = \frac{34.59}{(0.055)^2} = 11.43 \times 10^3 \Omega$$
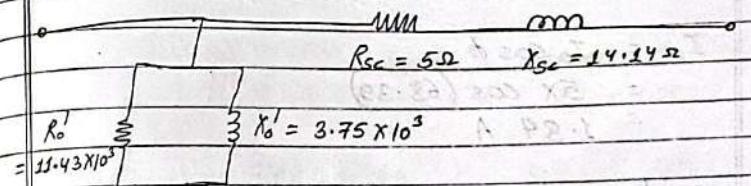
$$X'_o = \frac{X_o}{k^2} = \frac{11.35}{(0.055)^2} = 3.75 \times 10^3 \Omega$$



Eq. circuit of transformer referred to primary side

(i) A 50kVA, 2300/220V transformer when tested gives the following result:

O.C Test : 405 W 5A 220 V (L.V side)
 S.C Test : 805 W 20.2 A 95 V (H.V side)

Determine the circuit model referred to
 (i) primary and (ii) secondary

Sol: Here,
 For O.C Test (L.V side):

$$V_1 = 230 \text{ V}$$

$$I_0 = 5 \text{ A}$$

$$W_0 = 405 \text{ W}$$

$$\text{Now, } W_0 = V_1 I_0 \cos \phi$$

$$\text{or, } \cos \phi = \frac{W_0}{V_1 I_0}$$

$$\text{or, } \cos \phi = \frac{405}{220 \times 5}$$

$$\text{or, } \phi = \cos^{-1} \left(\frac{405}{220 \times 5} \right)$$

$$\therefore \phi = 68.39^\circ$$

$$\begin{aligned} I_{10} &= I_0 \cos \phi \\ &= 5 \times \cos (68.39) \\ &= 1.84 \text{ A} \end{aligned}$$

$$\begin{aligned} I_u / I_m &= I_0 \sin \phi \\ &= 5 \times \sin (68.39) \\ &= 4.64 \end{aligned}$$

$$R_o = \frac{R_{10} V_1}{I_{10}} = \frac{220}{1.84} = 119.56 \Omega$$

$$X_o = \frac{V_1}{I_m} = \frac{220}{4.64} = 47.41 \Omega$$

for S.C Test (H.V side):

$$W_{sc} = 805 \text{ W}$$

$$I_{sc} = 20.2 \text{ A}$$

$$V_{sc} = 95 \text{ V}$$

$$\text{Now, } R_{sc} = \frac{W_{sc}}{I_{sc}^2} = \frac{805}{(20.2)^2} = 1.97 \Omega$$

$$Z_{sc} = \frac{V_{sc}}{I_{sc}} = \frac{95}{20.2} = 4.702 \Omega$$

$$X_{sc} = \sqrt{Z_{sc}^2 - R_{sc}^2}$$

$$= \sqrt{(4.702)^2 - (1.97)^2}$$

at banks of primary flux density (B) = 4.2652

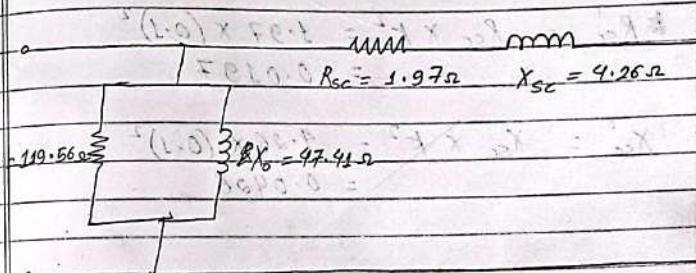


fig: Equivalent circuit of transformer

(i) When circuit parameters referred to primary (L.V side) - H.V side)

$$k = \frac{E_2}{E_1} = \frac{220}{2200} = 0.1$$

$$R'_s = \frac{R_s}{k^2} = \frac{119.56}{(0.1)^2} = 11956 \Omega$$

$$X'_s = \frac{X_s}{k^2} = \frac{47.41}{(0.1)^2} = 4741 \Omega$$

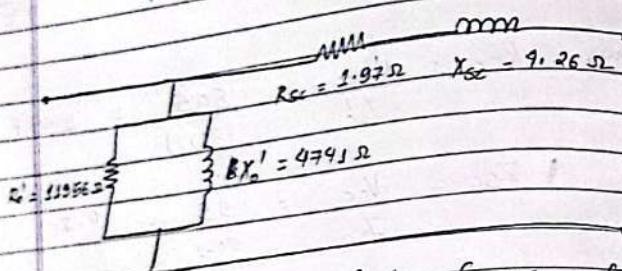


fig: Equivalent circuit of transformer referred to primary.

(ii) When circuit parameters referred to secondary (H.V side) - L.V side)

$$B R'_s = R_s \times k^2 = 1.97 \times (0.1)^2 = 0.0197$$

$$X'_s = X_s \times k^2 = 4.26 \times (0.1)^2 = 0.0426$$

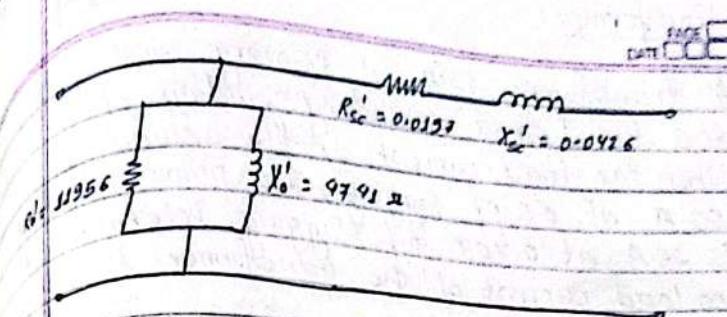


fig: Equivalent circuit of transformer referred to secondary.

Transformer:

- Q) A transformer has a primary winding of 800 turns and secondary winding of 200 turns. When the load current on the secondary is 80 A at 0.8 pf lagging, the primary current is 25 A at 0.707 pf lagging. Determine the no load current of the transformer. Draw the vector diagram.

S.F.

Here,

$$N_s = 800$$

$$N_p = 200$$

$$I_2 = 80 \text{ A}$$

p.f at secondary, $\cos \phi_2 = 0.8$

$$\therefore \phi_2 = 36.86^\circ$$

$$\therefore [I_2 = 80 \angle 36.86^\circ \text{ A}]$$

$$I_2 = 25 \text{ A}$$

p.f at primary, $\cos \phi_1 = 0.707$

$$\phi_1 = 45^\circ$$

$$\therefore [I_1 = 25 \angle 45^\circ \text{ A}]$$

$$\therefore I_1 = I_2 + I_o'$$

$$\Rightarrow I_o = I_1 - I_2'$$

$$\text{Now, } k = \frac{N_2}{N_1} = \frac{200}{800} = 0.25$$

$$\therefore I_o' = 80 \times 0.25 \angle 36.86^\circ$$

$$= 20 \angle 36.86^\circ$$

DATE / /

$$\begin{aligned} \therefore I_o &= I_2 - I_o' \\ &= (25 \angle 45^\circ) - (20 \angle 36.86^\circ) \\ &= (17.67 + j 5.67) - (16 + j 19) \\ &= 1.67 + j 5.67 \\ &= 5.91 \angle 73.5^\circ \end{aligned}$$

vector diagram: A Ao

- Q) A 12 KVA transformer having primary voltage of 2000 V at 50Hz has $N_1 = 180$ & $N_2 = 30$. Find (i) the full load primary & secondary current (ii) The no-load secondary induced emf (iii) the maximum flux in the core.

S.F. Here,

$$N_1 = 180$$

$$N_2 = 30$$

$$E_1 = V_1 = 2000 \text{ V}$$

$$AP = 12 \text{ KVA} = 12 \times 10^3 \text{ VA}$$

$$f = 50 \text{ Hz}$$

$$(i) I_1 = ? \quad \& \quad I_2 = ?$$

$$(ii) \text{secondary emf } (E_2) = ?$$

$$(iii) \text{maximum flux } (\Phi_{\max}) = ?$$

$$\text{Now, } \because AP = 12 \times 10^3$$

$$\text{or, } V_1 I_1 = 12 \times 10^3$$

$$\text{or, } 2000 \times I_2 = 32 \times 10^3$$

$$\text{or, } I_2 = \frac{32 \times 10^3}{2000}$$

$$\boxed{I_2 = 6 \text{ A}}$$

$$\therefore \frac{I_2}{I_1} = \frac{N_2}{N_1}$$

$$\text{or, } I_2 = I_1 \frac{N_2}{N_1}$$

$$\text{or, } I_2 = 6 \times \frac{180}{30}$$

$$\therefore \boxed{I_2 = 36 \text{ A}}$$

New, emf per turn of primary side (E_1) = $\frac{V_1}{\frac{N_1}{N_1}}$

New, we know that :

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{180}{30} = \frac{6}{1}$$

$$\text{or, } E_2 = E_1 \frac{N_2}{N_1}$$

$$\text{or, } E_2 = \frac{2000 \times 30}{180}$$

$$\therefore \boxed{E_2 = 333.33 \text{ V}}$$


New, Emf eqn of transformer is:

$$E_1 = 4.44 f N_1 \phi_{\max}$$

$$\text{or, } \phi_{\max} = \frac{E_1}{4.44 f N_1}$$

$$\text{or, } \phi_{\max} = \frac{2000}{4.44 \times 50 \times 180} \quad \therefore \boxed{\phi_{\max} = 0.05 \text{ Tesla}}$$

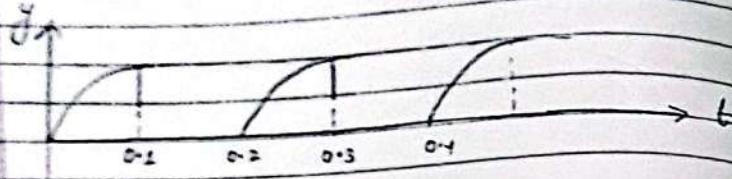Q Determine the peak factor and form factor of the function shown below if it is given that: for $0 \leq t < 0.1$, $y = 10(1 - e^{-100t})$
 $0.1 \leq t < 0.2$, $y = 10 e^{-50(t-0.1)}$



Time period (T) = 0.2

$$\begin{aligned}
 y_{av} &= \frac{1}{0.2} \int_{0.0}^{0.2} y(t) dt \\
 &= \frac{1}{0.2} \left[\int_{0.0}^{0.1} y_1(t) dt + \int_{0.1}^{0.2} y_2(t) dt \right] \\
 &= \frac{1}{0.2} \left[\int_0^{0.1} 10(1 - e^{-100t}) dt + \int_{0.1}^{0.2} 10 e^{-50(t-0.1)} dt \right] \\
 &= \frac{10}{0.2} \left[\int_0^{0.1} (1 - e^{-100t}) dt + \int_{0.1}^{0.2} e^{-50(t-0.1)} dt \right] \\
 &= 50 \left[\left| t - \frac{e^{-100t}}{-100} \right|_0^{0.1} + \int_{0.1}^{0.2} (e^{-50t+5}) dt \right]
 \end{aligned}$$