

Sl. No.	Date	Chapter Name	Page No.	Teacher's Sign. Remarks

Chapter-1 Introduction

DATE PAGE

Role of electricity in modern society:
Electricity is the set of physical phenomena associated with presence and flow of electric charge. It gives a wide variety of well known effects such as lightning, sat (static) electricity, electromagnetic induction and the flow electrical current and creation and reception of electromagnetic radiation such as radio waves.

Today the modern society exists because of electricity; it is one of the greatest invention in the history, because of electricity many things can be possible like medical operations, production, construction & many more are likely to happen even during night time. Almost everything we use function by the help of electricity. Imagine the world without electricity, we can not watch television or play computer games. The essential device and a man's best friend which is the cellular or mobile phone cannot be possible without electricity. Laptops and computers is nothing without electricity and every homes are lightened with the power of this great invention.

Hence progress of human civilization has historically been in proportional to the



CamScanner



CamScanner

ability of humans to use energy. The operation of our technological society depends upon the production and use of large amount of energy. The use of electrical energy has reached such a scale that it is unimaginable to live without it.

#

Energy source & production, generation, transmission & distribution of electrical energy :

There are some basic energy sources that can be used for production of electrical energy. To generate electricity means to convert source of energy into electrical form. The device used for production of electrical energy in large scale is known as generator which converts mechanical energy into electrical form. Electrical energy sources are divided into two types. They are:

(i)

(1) Thermal:

Coal: Coal has been the major source of power generation in the countries around the world where its deposits are substantial. In USA about 45% of total electrical energy generation is from coal and in India it is more than 50%. However in Nepal we do not have any deposits of source and

therefore there is no power stations using coal as a source.

(ii)

Nuclear fission: Nuclear fission of atomic materials such as Uranium produces heat which is utilized to produce station steam turbines, such as power station is called nuclear power station. About 3000 metric tonnes of coal produces the same amount of heat as by the 1kg of nuclear fuel.

(iii)

Geo-Thermal: Heat from the earth's interior and sub-surface water is combine to produce natural steam which can be used to run the turbines and thereby produces electrical energy. California operating at a capacity of about 100 mega watt which is the biggest of this kind. It is an example of geo-thermal source.

(2) Non-Thermal:

Tidal: There are a few sites around the world where it proves economical to convert the change in potential energy caused by tide levels into electrical form. The largest installation of this tide is in France with a rated capacity of 290 Megawatt.

Wind: The wind can be used to drive turbines (air turbines) that turns drive generators to produce electricity. In certain places where the strong winds are common

features, this source of energy may be attractive for the generation of electricity.

(iii) Solar: Semi-conductors expose to solar radiations produces electricity through the solar panels. Because of the high cost of solar cells and low efficiency of this conversion this process be source for the commercial production of electrical energy has not been feasible.

(iv)

Hydro power: Hydro-electricity is another term for power generated by harnessing the power of moving water. Not necessarily falling water, just moving water. There are many famous such generating stations in the world such as Niagara falls, Grand coulee and Bullider Dam. These are just a few of the many examples of energy produced by falling water. Power is generated or manufactured in large scale at power generating stations using the same basic principle as a small grist mill yet on a most larger and vastly improved scale for better efficiency. These electrical generators are attached to turbines which spin at a great speed as a result of water rushing through them. These power stations, turbines are much more efficient at extracting the kinetic energy from the moving water and converting that energy into power through these generators.

The hydro electricity extracted from water depends not only the volume but in the difference in height between the source & the water outflow. The height difference is called head. The amount of P.E. in water is directly proportional to head. To obtain very high head water ~~is~~ for hydraulic turbine may be run through a large pipe. Hence, in this way electricity is generated in hydropower stations.

Chapter - 2

D.C circuit Analysis [30-35 marks]

Electric Circuit :

A circuit is a closed conducting path through which an electric current flows. circuit consists of active and passive elements.


Active elements are those

which have their own energy and they transfer energy to passive elements. And passive elements are those which doesnot have their own energy. They receive energy from active elements.

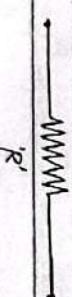Example: Active elements \rightarrow Voltage, Current, passive elements \rightarrow Resistor, capacitor, inductor etc.

Resistor:


It is defined as the property of a substance due to which it opposes the flow of electricity. It is a dissipative element which converts electrical energy into heat energy as current flow through it at any direction.



Symbol of resistor
Its unit is ohm (Ω).

Inductor:

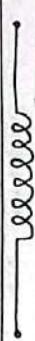It is two terminal storage element in which energy is stored in magnetic flux field. The inductance of a circuit is measured in Henry (H).



Symbol of inductor

Capacitor:

It is a two terminal element that has the capability of energy storage in electric field. The energy stored can be fully restored. Its unit is Farad (F).



Symbol of capacitor

Series & Parallel Resistor:

(1) Series Resistor:

let us consider a circuit having resistors R_1 & R_2 connected in series with their respective voltage V_1 & V_2 .



In this case, total voltage of the circuit is :

$$V = V_1 + V_2$$

$\because V = IR$, so, we get :

$$IR_{\text{eq}} = I_1 R_1 + I_2 R_2$$

Again, $I_1 = I_2 = I$ [\because current is same in series]

$$IR_{\text{eq}} = I R_1 + I R_2$$

$$\boxed{R_{\text{eq}} = R_1 + R_2}$$

For 'n' number of resistors :


$$\boxed{R_{\text{eq}} = R_1 + R_2 + R_3 + \dots + R_n}$$

(2) Parallel Resistor:


Let us consider a circuit having resistance

R_1 & R_2 connected in parallel with their

respective current I_1 & I_2 .

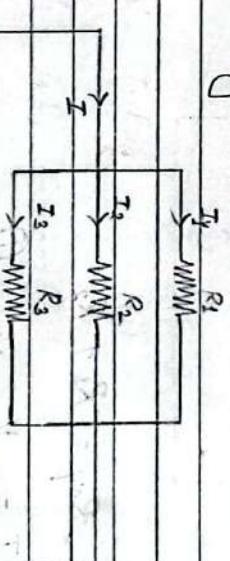

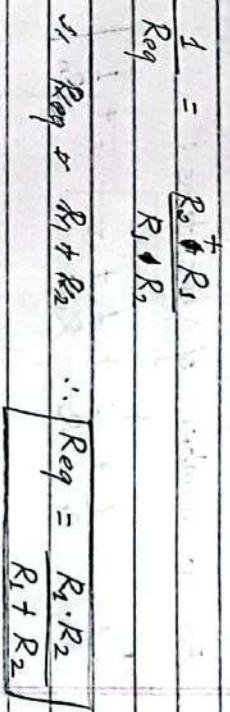If 3 resistors R_1 , R_2 & R_3 are connected in parallel with respective current I_1 , I_2 & I_3 through them.



In this case, total current is :

$$I = I_1 + I_2 + I_3$$

$$\frac{V}{R_{\text{eq}}} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

∴ Voltage is same in parallel, so we have:

$$V_1 = V \times \frac{R_1}{R_{\text{eq}}}$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


$$\frac{1}{R_{\text{eq}}} = \frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 R_2 R_3}$$

$$R_{\text{eq}} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

For n number of resistors:

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

Voltage Divider Formula:

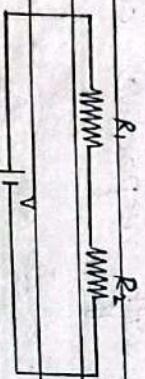

Here,

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V = I \cdot R_{\text{eq}}$$

Here,

$$R_{\text{eq}} = R_1 + R_2$$

$$V_1 = I_1 R_1 \quad \text{--- (i)}$$


$$I = V \quad \text{--- (ii)}$$

$$I_1 = \frac{V_1}{R_1} \quad \text{--- (iii)}$$

Since, current is same in series, so

$$\frac{V}{R_{\text{eq}}} = \frac{V_1}{R_1}$$

Current Divider formula:

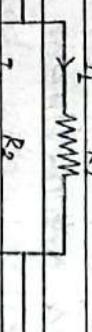

$$\text{Similarly, } V_2 = V \times \frac{R_2}{R_1 + R_2}$$

$$V_1 = V \times \frac{R_1}{R_1 + R_2}$$

$$I_1 = \frac{I \cdot X}{R_1} R_{eq}$$

$$I_1 = I \times \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = I \times \frac{R_2}{R_1 + R_2}$$

Similarly, $I_2 = I \times \frac{R_1}{R_1 + R_2}$

Linear & Non-linear parameters:

For a non-linear element the current passing through it does not change linearly with the linear change in applied voltage or current. Semi-conductor devices are the example of non-linear elements.

Active and passive networks:

Active networks are those which contains one or more than one sources of emf connected with passive elements. Active network is shown below:

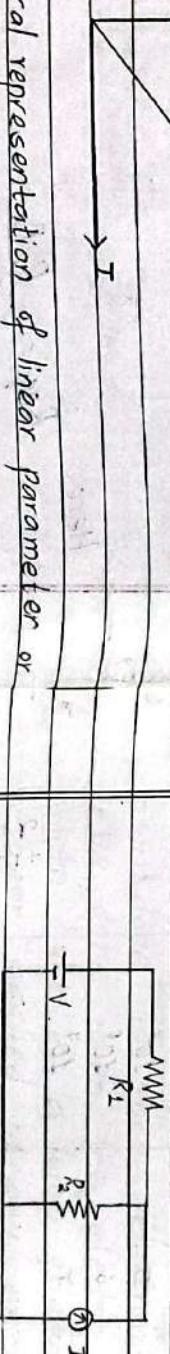


fig: Graphical representation of linear parameter or Ohm's law

fig: Active Network

Passive networks are those which does not contains any active elements. Passive network is the combination of resistor, capacitor or inductor.

fig: o/p of non-linear parameter

A linear element shows linear characteristics of voltage and current. Simple resistors, capacitors and inductors are linear elements and their resistance, inductance and

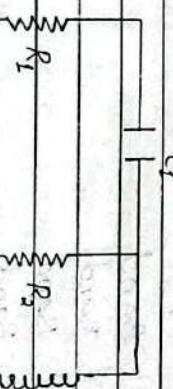


fig: Passive circuit

Resistor Colour Coding :

It is difficult to write the value of resistor on the surface of resistor because of its size. So for simplicity coloured bars are stamped on the surface of resistance or resistor.

Different coloured bar has different values as shown in table below:

Colour	1 st Band	2 nd Band	3 rd Band	4 th Band
Black	0	0	10^0	
Brown	1	1	10^1	
Red	2	2	10^2	$\pm 2\%$
Orange	3	3	10^3	
Yellow	4	4	10^4	
Green	5	5	10^5	
Blue	6	6	10^6	
Violet	7	7	10^7	
Grey			$\pm 2\%$	
White			$\pm 2\%$	
Gold			$\pm 1\%$	
Silver			$\pm 2\%$	

Then, value of resistor is given by:

$$R = AB \times C \pm D$$

where,

A = 1st Band

B = 2nd Band

C = 3rd Band

D = 4th Band

Ohm's Law:

It describes the relationship between voltage or emf and current established by it. Ohm's law states that the voltage in the circuit is directly proportional to current provided that the temperature of the conductor remains constant.

$$\text{ie } V \propto I$$

$$V = IR$$

[where R is constant known as resistance]

Power:

When an electric current flows in a conductor heat is dissipated as a result of work done in moving electrons. Work is said to be done when the electric current is converted into light in a lamp filament or bulb. The power supplied in any electrical component is given by the product of voltage and current.

$$\text{power} = \text{Voltage} \times \text{current}$$

$$P = IR \times I$$

$$P = I^2 R$$

Its unit is watt (W).

Ideal and Practical Voltage Source:

An ideal voltage source is that voltage source which gives a fixed or constant load voltage. An ideal voltage source has zero

internal resistance as shown in figure:

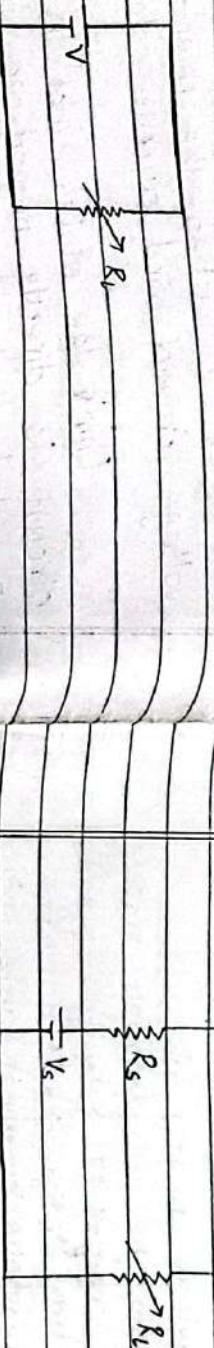


fig: Ideal voltage source

A practical voltage source is one in which there is some internal resistance or impedance which makes the load voltage vary with the load or load current due to drop in internal resistance of the source.

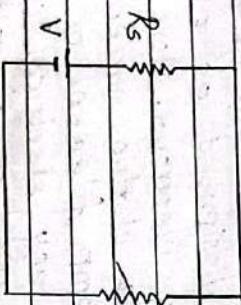


fig: practical voltage source

where,
 $R_S \rightarrow$ Internal resistance
 $R_L \rightarrow$ Load resistance

TOP # Conversion of voltage source into current source:

$$I_S = \frac{V_S}{R_S}$$


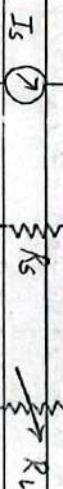


fig: conversion of voltage into current

TOP # Conversion of current source into voltage source:

let us consider a circuit having source voltage ' V_S ' with its internal resistance ' R_S ' and load resistance ' R_L ' as shown below:


shown below:

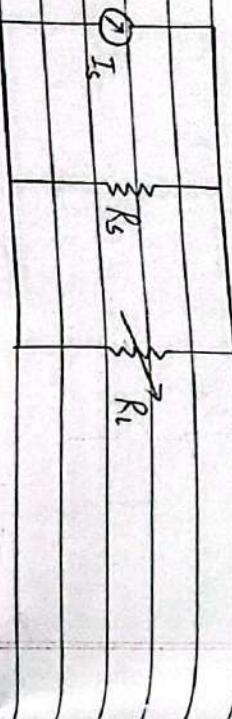

If the parallel resistance R_s is not present in the circuit, then the current source cannot be converted into voltage source or ideal current source cannot be converted into voltage source.

After conversion of current source into voltage source, the parallel resistance is connected in series with voltage source with the same value & the voltage is given by :

$$V_s = I_s R_s$$

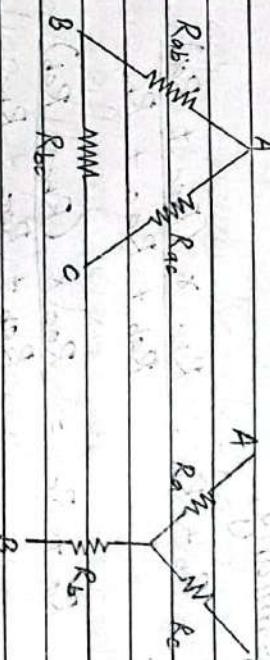

Delta Network (A)

Star Network (Y)

For delta network :

Here, resistor R_{ab} is parallel with $(R_{ac} + R_{bc})$

$$(R_{ab})_d = R_{ab} \parallel (R_{ac} + R_{bc})$$

$$(R_{ab})_d = \frac{R_{ab} \times (R_{ac} + R_{bc})}{R_{ab} + R_{ac} + R_{bc}} \quad \text{--- (i)}$$

For star network :

Equivalent resistance across AB is :

$$(R_{ab})_y = R_a + R_b \quad \text{--- (ii)}$$

fig: Conversion of current into voltage

The equivalence between these two networks for the terminal A & B is established by

Star / Delta Transformation:

In circuit analysis, the topology of some network is so complicated that it is very difficult to reduce into an equivalent structure of series and parallel combination. So star/delta transformation is used to solve such types of complicated networks.

equating the equation (1) & (i);
ie

$$(Rab)_r = (Rab)_s$$

$$Ra + Rb = \frac{Rab \times (Rac + Rbc)}{Rab + Rac + Rbc} \quad \text{--- (A)}$$

similarly,

$$Rb + Rc = \frac{Rbc \times (Rac + Rab)}{Rab + Rac + Rbc} \quad \text{--- (B)}$$

$$Ra + Rc = \frac{Rac \times (Rbc + Rab)}{Rab + Rac + Rbc} \quad \text{--- (C)}$$

Now, solving equation (A), (B) & (C), we get:

$$Ra = \frac{Rab \times Rac}{Rab + Rac + Rbc}$$

$$Rb = \frac{Rbc \times Rac}{Rab + Rac + Rbc} \quad \left. \begin{array}{l} \text{conversion of} \\ \text{delta to star} \end{array} \right\}$$

$$Rc = \frac{Rac \times Rbc}{Rab + Rac + Rbc} \quad \left. \begin{array}{l} \text{conversion of} \\ \text{star to delta} \end{array} \right\}$$

Similarly, for converting star to delta;

$$Rab = Ra Rb + Rb Rc + Ra Rc$$

$$Ra = \frac{Rab - Rb Rc - Ra Rc}{Rb} \quad \& \quad Rac = \frac{Rab + Rb Rc + Ra Rc}{Rb}$$

Kirchhoff's Law:


A German physicist Gustav Kirchhoff observed two conditions for the analysis of any electrical network.

(i) Kirchhoff's Current Law (KCL):

At any instant, the algebraic sum of all the currents at a junction of a point is equal to zero.

Different signs are assigned to the current flowing toward or away from the junction. Incoming currents are assumed to be positive and outgoing currents are assumed to be negative.

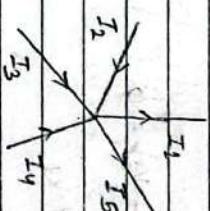Let us consider sources I_1, I_2, I_3, I_4 and I_5 as shown in figure below:



Then, according KCL :

$$I_1 + I_3 + I_4 - I_2 - I_5 = 0$$


$$[I_1 + I_5 = I_2 + I_3 + I_4]$$

Incoming current = Outgoing current.

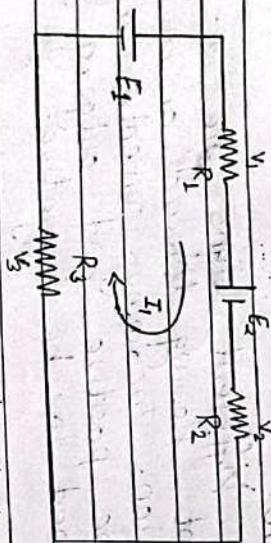(ii) Kirchhoff's Voltage Law (KVL):

At any instant, in a closed loop, the algebraic sum of emf acting around the loop is equal to the sum of potential drop around the loop.

Let us consider a circuit having sources of emf E_1 & E_2 and resistors R_1 , R_2 & R_3 as shown below:



If I_L be the current around the closed path in clockwise direction then applying KVL, we get:

$$+ E_1 - V_1 - E_2 - V_2 - V_3 = 0$$

$$E_1 - E_2 = V_1 + V_2 + V_3$$

$$E_1 - E_2 = I_1 R_1 + I_2 R_2 + I_3 R_3$$

$$| E_1 - E_2 = I_1 (R_1 + R_2 + R_3) |$$

It contains a junction point and the voltage in the circuit must be measured between two terminals.

If it is appropriate and useful to assign one terminal as a reference

Mesh Analysis (Maxwell's Mesh Analysis):

A mesh is the most elementary form of a loop. It is the property of simple network and must be identical that it can not be further divided into other loops.

In this method, a different current is assumed in the loop, and the polarities of drop in each element is determined by the assumed direction (clockwise) of the loop current for that loop. KVL is then applied around each closed loop and current in each loop is determined.

Super-Mesh Analysis:

When the current source appears in between any two loops and the current source can not be converted into voltage source, such type of network is known as super mesh analysis and super mesh analysis is used to solve such type of network.


Nodal Analysis:

It contains a junction point and the voltage in the circuit must be measured between two terminals.

If it is appropriate and useful to assign one terminal as a reference

point, this reference point or reference terminal is called circuit ground.

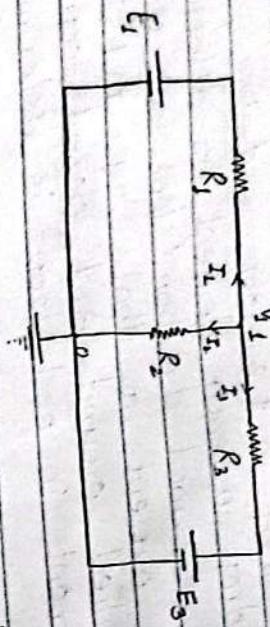Let us consider a circuit as shown below which contains a junction point 1 and a reference point zero.



Let v_i be the voltage at point 'i', then considering outgoing current I_1 , I_2 & I_3 as shown.

Applying KCL at junction node 'i'.

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - E_1}{R_1} + \frac{V_1 - 0}{R_2} + \frac{V_1 - E_3}{R_3} = 0 \quad \text{--- (1)}$$

Super Node:

- With the voltage source between two nodes a difficulty arises in applying KCL in the circuit, an easy way to solve out this difficulty is to treat nodes along

Dependent and Independent Sources:


The voltage or current source which doesn't depend on any other quantity in the circuit are called independent sources.

A dependent voltage or current source is one which depends on the some other quantity in the same network which may be either voltage or current source.

Dependent sources are represented by diamond shaped symbol!



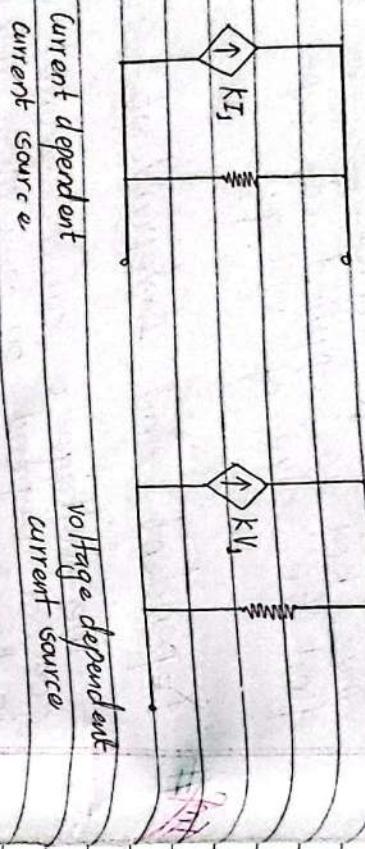Current dependent voltage dependent voltage source



current dependent voltage dependent current source

response caused by each source acting alone while the other source is made inactive.

A voltage source is made inactive by placing a short circuit across the terminals of voltage and making open circuit across a current source.

Network Theorems :

Network theorems are used for the solution of typical electrical networks. on the basis of methods of solving the network, they are divided into following four types.

(1) Superposition Theorem

(2) Thevenin's Theorem

(3) Norton's Theorem

(4) Maximum power transfer theorem (MPT)

(1) Superposition Theorem:

The response at any point in a linear circuit (circuit having voltage, current and resistor) containing more than one independent sources can be obtained by superimposing the

The equivalent voltage source is equal to the p.d measured between two terminals with no external sources connected to these terminals and the series resistance (R_{th}) is equivalent resistance looking into the network from these two terminals with all sources in the network made inactive.

The load current (I_L) is given by :

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

where,

$V_{th} \rightarrow$ Thevenin's equivalent voltage.
 $R_{th} \rightarrow$ Thevenin's equivalent resistance
 $R_L \rightarrow$ load resistance

$I_L \rightarrow$ load current



Thevenin's equivalent network can also be represented by :

circuit with any no. of sources	$\frac{V_{th}}{R_{th}}$
(voltage/current/ resistance)	$\rightarrow T_{V_{th}}$

fig : Norton's equivalent ckt

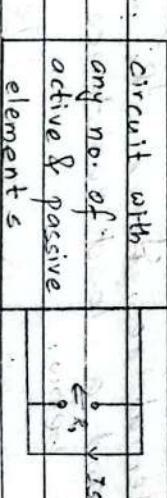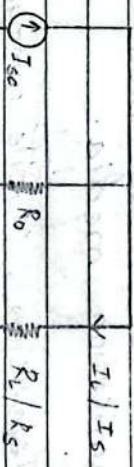
(3) Norton's Theorem : Any two terminal active network containing voltage source, current source and resistance when viewed from its output terminal is equivalent to a constant current source (I_{sc} or short circuit current) and a parallel resistance (R_o). R_o (or open ckt eq. resistance).

The constant current (I_{sc}) is equal to the current which would flow in the short circuit placed across the terminal and parallel resistance (R_o) is the equivalent resistance of the network when viewed from these open circuited terminal after all voltage and current source are removed or made inactive.



The current across load resistor is given by:
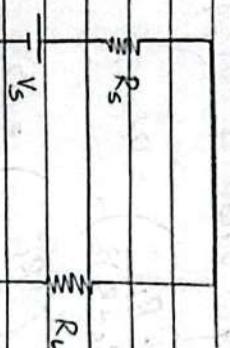
$$I_L = I_{sc} \times \frac{R_L}{R_o + R_L}$$



TOP(4) Maximum Power Transfer Theorem: [MPTT]

An independent voltage source with a series resistance R_s or an independent current source with a parallel resistance R_s delivers maximum power to the load resistor R_L when the source internal resistance is equal to the load resistance ie

$$R_s = R_L$$

It is used in broadcasting & communication media.

Eg: Television, Mobile communication, amplifier.

Proof

Let us consider a Thévenin's equivalent ckt having voltage source 'V_s' with internal resistance R_s as shown below and a load resistance R_L as shown below:

fig: Thévenin's Equivalent circuit

In this case,

current across load resistor is :

$$I_L = \frac{V_s}{R_s + R_L} \quad \text{--- (i)}$$

Now, power across R_L is given by :

$$P_L = I_L^2 R_L$$

$$P_L = \left(\frac{V_s}{R_s + R_L} \right)^2 \times R_L$$

$$P_L = \frac{V_s^2 R_L}{(R_s + R_L)^2} \quad \text{--- (ii)}$$

The power is maximum when,

$$\frac{dP_L}{dR_L} = 0$$

Substituting value of P_L from eqn ①:

$$\frac{d}{dR_L} \left(\frac{V_s^2 R_L}{(R_S + R_L)^2} \right) = 0$$

$$\text{or, } \frac{V_s^2}{R_S + R_L} \times \frac{d}{dR_L} \left(\frac{R_L}{(R_S + R_L)^2} \right) = 0$$

$$\text{or, } \frac{d}{dR_L} \left(\frac{R_L}{(R_S + R_L)^2} \right) = 0$$

$$\text{or, } (R_S + R_L)^2 \times \frac{d}{dR_L} (R_L) - R_L \times \frac{d}{dR_L} (R_S + R_L)^2 = 0$$

$$[(R_S + R_L)^2]^2$$

$$\text{or, } (R_S + R_L)^2 \times 1 - R_L \times 2(R_S + R_L) \times (0+1) = 0$$

$$\text{or, } (R_S + R_L)^2 - 2R_L(R_S + R_L) = 0$$

$$\text{or, } (R_S + R_L)^2 - 2R_L(R_S + R_L) = 0$$

$$\text{or, } (R_S + R_L)^2 - 2R_L(R_S + R_L) = 0$$

$$\text{or, } (R_S + R_L) \{ (R_S + R_L) - 2R_L \}^2 = 0$$

$$\text{or, } (R_S + R_L) - 2R_L = 0$$

$$\text{or, } R_S - R_L = 0$$

$$\therefore R_S = R_L$$

This is the required condition for maximum power transfer to load resistor.

\therefore Eqn ① becomes :

$$P_L = \frac{V_s^2 R_L}{(R_S + R_L)^2}$$

$$= \frac{V_s^2 R_L}{(R_L + R_L)^2}$$

$$= \frac{V_s^2 R_L}{4R_L^2}$$

$$= \frac{V_s^2}{4R_L}$$

$$\therefore P_L = \frac{V_s^2}{4R_L}$$

Unit - 5**Single Phase AC Circuit Analysis**

An alternating current or voltage is one that regularly flows in one direction and then in opposite direction. This reversible flow of current or voltage occurs at regular interval of time. AC circuits are more common than DC circuits because they can be controlled and utilized more easily in general application.

Generation of Alternating Voltage or current :

Alternating voltage may be generated by rotating a coil in a magnetic field or by rotating a magnetic field within a stationary coil.

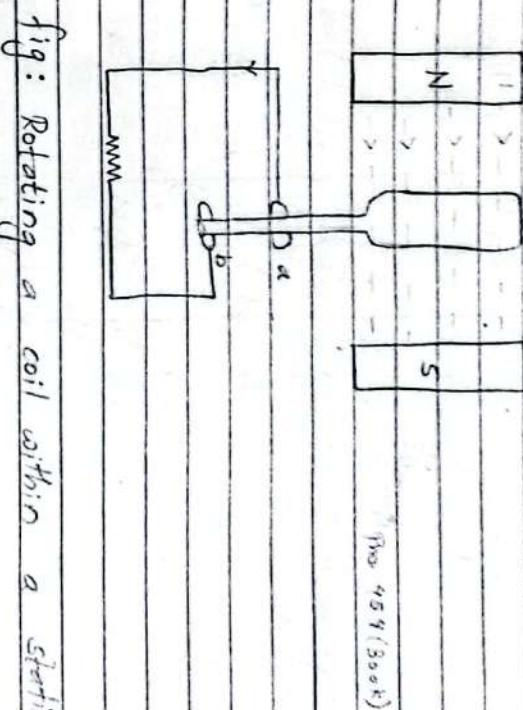
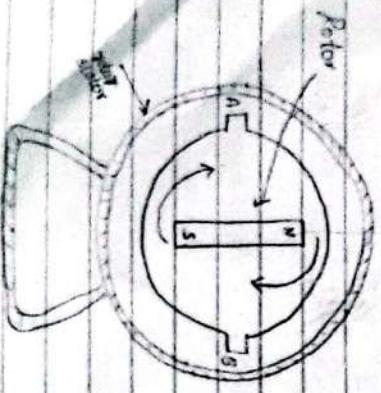


fig: Rotating a coil within a stationary magne

The value of voltage generated depends upon the number of turns 'N' in the coil, strength of field and the speed at which coil or magnet rotates.

Alternating voltage or current may be generated in either of two ways but rotating magnetic field within a stationary coil is one of the most widely used method.

Equation of Alternating Current :

Consider a rectangular coil having 'N' number of turns rotating in a uniform magnetic field with an angular velocity ' ω ' (radian/sec) as shown in figure :

N
mag (faraday)

flux linkage.
i.e.

$$e = -\frac{d}{dt} ND \quad \dots \dots \text{(ii)}$$

Substituting the value of ϕ from eqn (i) :

$$e = -\frac{d}{dt} (N\phi_m \cos\omega t)$$

$$e = -N\phi_m \cdot \frac{d}{dt} (\cos\omega t)$$

$$e = -N\phi_m \cdot (-\sin\omega t) \cdot \omega$$

Let, time be measured in X-axis, the maximum flux (ϕ_m) is linked in coil when its position is at X-axis at time t sec. The coil moves through an angle $\theta = \omega t$, in this position the component of flux which is perpendicular to plane of coil is given by:

$$\phi = \phi_m \cos\omega t \quad \dots \dots \text{(i)}$$

$$\therefore e = N\phi_m \cdot \omega \sin\omega t$$

$$\text{At } \theta = \omega t = 90^\circ, \sin\omega t = 1$$

$$\therefore e = E_m = N\phi_m \omega$$

(iii)

Note : e = $E_m \sin\omega t$. Put $N\phi_m \omega = E_m$ in eqn (i)

If N be the total number of turn in the coil then the maximum flux linkage of the coil at any time is given by $N\phi$.

According to the Faraday's law of electromagnetic induction, the induced emf is given by, the rate of change


$$[E = E_m \sin\omega t]$$

$$V = V_m \sin\omega t$$

$$I = I_m \sin\omega t$$



Sinusoidal function Terminology:

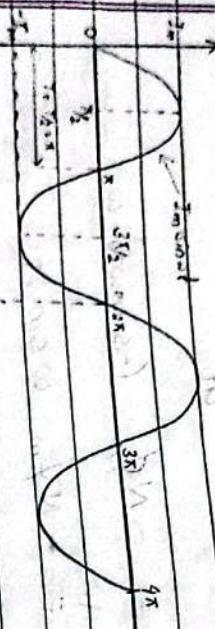

Amplitude: The maximum positive or negative value of alternating quantity is known as amplitude or instantaneous value of that quantity

Average value of an alternating quantity

The average value of alternating current is expressed by that steady current which transfer across any circuit, the same charge is transferred by that alternating current during the same time.

Cycle: One complete set of positive and negative values of alternating quantities (voltage or current) is known as cycle.

Time period: The time taken by an alternating quantity to complete one cycle is known as time period.

for example: A 50Hz alternating current has a time period of $\frac{1}{50}$ sec

Frequency: The numbers of cycles per second is called the frequency of the alternating quantity. Its unit is Hz (Hertz). ie.

$$f = \frac{1}{T}$$

In case of a symmetrical wave form, the average value over a complete cycle is zero. Hence in such case the average value is obtained by adding or integrating the instantaneous values of current over one half cycle ($T = \frac{1}{2}T_0$) but in case of unsymmetrical wave form the average value must be taken over the complete cycle.




Let us consider an alternating current:

$$I = I_m \sin \omega t$$

where, I_m is the maximum value or amplitude of the alternating current
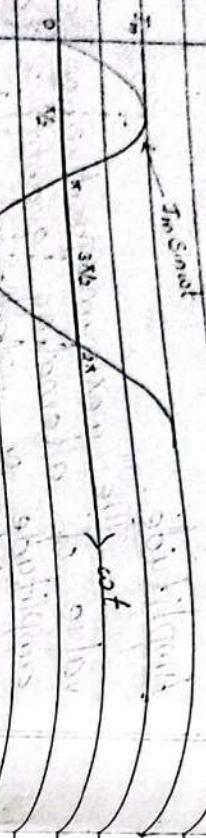
$$= -\frac{I_m}{2\pi} (\cos \omega t - 1)$$



$$\therefore I_{av} = 0$$

Therefore, the average value of symmetric wave form is zero over a complete cycle.

Now, Average value of current is given by:

$$I_{av} = \frac{1}{T} \int_0^T I(t) dt$$

$$= \frac{1}{2\pi}$$

$$\text{i.e. } T = \pi$$

$$\& I_{av} = I_m \sin \omega t$$

Here, from above wave form:

$$T = 2\pi$$

$$I(t) = I_m \sin \omega t$$

$$I_{av} = \frac{1}{2\pi} \int_0^{2\pi} I_m \sin \omega t d(\omega t)$$

Substituting in equ ①, we get:

$$I_{av} = \frac{1}{2\pi} \int_0^{2\pi} I_m \sin \omega t d(\omega t)$$

$$= \frac{I_m}{2\pi} \int_0^{2\pi} \sin \omega t d(\omega t)$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

DATE PAGE



DATE PAGE

$$= -\frac{I_m}{\pi} [\cos \pi - \cos 0]$$

$$= -I_m [-1 - 1]$$

$$\therefore I_{\text{av}} = \frac{2I_m}{\pi} \Rightarrow I_{\text{av}} = 0.637 I_m$$

$$\therefore I_{\text{rms}}^2 = \frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2(\omega t) d(\omega t)$$

$$= \frac{I_m^2}{2\pi} \int_0^{2\pi} \sin^2(\omega t) d(\omega t)$$

$$= \frac{I_m^2}{2\pi} \int_0^{2\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d(\omega t)$$

Root Mean Square (RMS) value:

The RMS value of an alternating quantity is given by that direct current which when flowing through a given circuit for a given time produces the same heat as produced by the alternating current.

The RMS value of alternating current is given by:

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T I^2(t) dt}$$

Squaring both sides:

$$I_{\text{rms}}^2 = \frac{1}{T} \int_0^T I^2(t) dt \dots \dots \dots (1)$$

Here, $T = 2\pi$

$$I(t) = I_m \sin \omega t$$

$$\therefore I_{\text{rms}} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$

$$I_{av} = \frac{2 I_m}{\pi} = 0.637 I_m$$

or, $k_a = \frac{I_m}{0.637 I_m}$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$

$$\therefore k_a = 1.41$$

Similarly, $V_{av} = 0.637 V_m = \frac{2 V_m}{\pi}$

$$V_{rms} = 0.707 V_m = \frac{V_m}{\sqrt{2}}$$

Form factor:

It is defined as the ratio of rms value to the average value.

i.e

$$\text{form factor } (k_f) = \frac{\text{Rms value}}{\text{Average value}}$$

$$= 0.707 I_m$$

Now, Applying KV L:

$$V_s = V_R + V_L + V_C$$

$$I_kf = 1.1$$

$$IZ = IR + IX_L + IX_C$$

Peak factor:

Peak factor is the ratio of maximum value to the RMS value.

i.e

$$\text{peak factor } (k_p) = \frac{\text{Maximum value}}{\text{RMS value}}$$

Let us consider a series RLC circuit as shown below connected with source voltage V_s and frequency 50 Hz .

Admittance is the reciprocal of impedance, it is denoted by Y and given by:

$$Y = \frac{1}{Z} \text{ in mho/Siemens}$$

Reactance:

The analysis of an electric current in an electric circuit (RC circuit) is known as reactance. It is the imaginary part of impedance which is caused by the presence of inductor or capacitor in the circuit. Reactance produces a phase shift between electric current and voltage. It is denoted by X .

Instantaneous power in AC circuit is given by $P = V_m \sin \omega t \cdot I_m \sin(\omega t - \phi)$, while the current is $I = I_m \sin(\omega t - \phi)$. Given by ϕ being the phase difference between the voltage and current at any instant. ϕ is negative when voltage leads and ϕ is positive when voltage lags the current. $\phi = 0$ when the current and voltage are in same phase.

The instantaneous power 'P' is thus given by

$$\begin{aligned} P &= V_m I_m \sin(\omega t - \phi) \\ &= V_m I_m \sin \omega t \cos \phi - V_m I_m \cos \omega t \sin \phi \\ Z &= R + jX_L - jX_C \\ Z &= R + j(X_L - X_C) \\ &\text{Complex/polar form} \end{aligned}$$

Magnitude of Z is, $Z = \sqrt{R^2 + (X_L - X_C)^2}$

Phase/Angle is, $\theta = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$
reactance(X) = $X_L - X_C$

The second term in the right hand side of eqn ① contains a double frequency term and it is evident from this that the magnitude of the average value

of this term is zero since the average of a sinus quantity of double frequency over a complete cycle is zero. Thus the instantaneous power consists only of the passive circuit.

$$P_{av} = \frac{1}{2} V_m I_m \cos \phi$$

$$= \frac{V_m}{2} I_m \cos \phi$$


P_{av}

$$= V_{rms} I_{rms} \cos \phi$$

$$Z = R + jX_L$$

(iii) If $X = 0$ i.e. $X_L = X_C$, then the circuit is "Reactive" resistive

$$Z = R$$

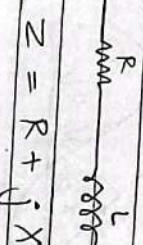

$$Z = jX_L - jX_C$$

$$Z = j(R - jX_C)$$

Instantaneous Power in AC circuit

In an AC circuit analysis let instantaneous Voltage be,

$$V = V_m \sin(\omega t + \theta_v) \quad \dots \dots \dots \quad (i)$$

$$I = I_m \sin(\omega t + \theta_i) \quad \dots \dots \dots \quad (ii)$$

Where, $\theta_v \rightarrow$ Angle of voltage
 $\theta_i \rightarrow$ Angle of current

(ν_v)

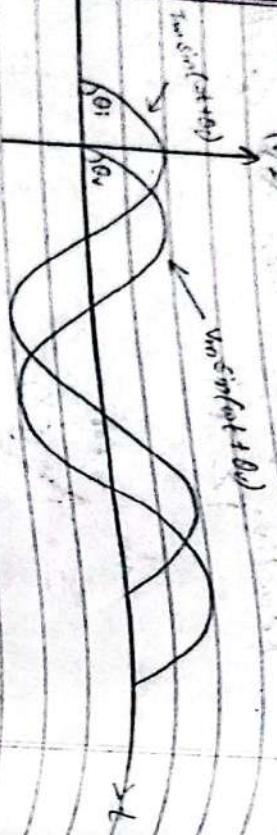


fig: Instantaneous voltage & current

Voltage (v) lead current (I) by an angle θ_v .

current (I) lag current (v) by an angle θ_i .

The instantaneous power in AC is given

by:
 $P = VI$

$$= V_m \sin(\omega t + \theta_v) \times I_m \sin(\omega t + \theta_i)$$

$$= V_m I_m \times \frac{1}{2} [\sin(\omega t + \theta_v) \cdot \sin(\omega t + \theta_i) - \cos(\omega t + \theta_v + \theta_i)]$$

$$= \frac{V_m I_m}{2} \int [\cos(\theta_v - \theta_i) - \cos(2\omega t + \theta_v + \theta_i)]$$

$$\therefore P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) - \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)$$

constant sinusoidal term

The sinusoidal term contains a double frequency, term (2ω), it is evident the magnitude of average value of sinusoidal term is zero over a complete cycle.
Hence, instantaneous power is given by:

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= \frac{\sqrt{2} V_{rms} \times \sqrt{2} I_{rms}}{2} \cos(\theta_v - \theta_i)$$

$$= V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$\boxed{P = VI \cos \phi}$$

where, $\phi = (\theta_v - \theta_i)$ which is angle between voltage & current.

i) Active Power (P)

It is the power which is actually dissipated in the circuit resistance. It is given by:

$$\boxed{\text{Active power} = VI \cos \phi = I^2 R}$$

$$\boxed{P = VI \cos \phi = I^2 R}$$

Its unit is watt.

When the magnitude of ϕ decreases then the value of power factor ($\cos\phi$) improves and the value of reactive factor ($\sin\phi$) decreases.

(ii) Apparent Power: (S)

It is the product of rms value of voltage and current.

$$\text{Apparent power} = VI$$

Its unit is VA (volt Ampere), kVA

$$S = VI = IZ \cdot I \cdot I^2$$

(iii) Reactive Power : 'Q'

It is the power developed in the inductive resistance of the circuit.

$$\text{Reactive power} = VI \sin\phi$$

Its unit is VAR (volt Ampere Reactive)

$$Q = I^2 R_L = I \cdot I \cdot Z \sin\phi$$

Complex Number Representation:

~~Imp #~~ Power factor:

It is the ratio of active power to the apparent power.

$$\text{ie power factor (P.f)} = \frac{VI \cos\phi}{VI} = \cos\phi$$

$$\therefore P.f = \cos\phi = \frac{R}{Z}$$

fig: vector-complex representation

In this case,

$$E = a + jb$$

The term $\cos\phi$ is called power-factor. It is the cosine of angle between


where a is horizontal component &

~~Imp #~~ Significance of power factor:

→ With the reduction of magnitude of angle ϕ , the phase angle between voltage and current is zero. In this condition power in the circuit is maximum. But reactive factor $\sin\phi$ decreases.

→ Improvement of power factor in any AC system is highly desired.

j↑

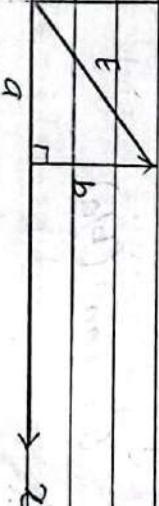

b is vertical component if j is operator.

It indicates that component ' b ' is perpendicular to component ' a ' and the two terms ' a ' and ' b ' are not to be treated as like term in any algebraic terms.

The vector written in this way is said to be written in complex form.

In mathematics, ' a ' represents real part and ' b ' represents imaginary part. But in basic electrical engineering these terms are known as inphase (active) and quadrature (reactive) components respectively.

The numerical value of E is given by:

$$|E| = \sqrt{a^2 + b^2}$$

And the angle with x - component is given by:

$$\theta = \tan^{-1}(b/a)$$

Resonance:

Resonance in electrical circuit consisting of active and passive elements represents a particular state of the circuit. When the

current or voltage in the circuit is maximum or minimum with respect to the magnitude of excitation at a particular frequency, the circuit impedance become minimum or maximum at a power factor of unity.

(1) Resonance of RLC Series Circuit:

Let us consider RLC series circuit as shown below:

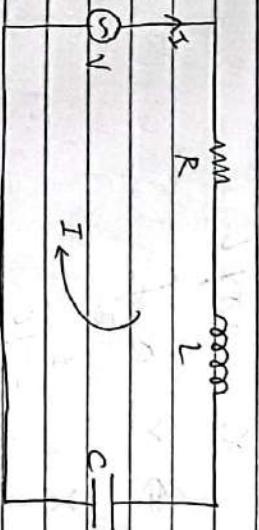


fig: RLC series circuit

Now,

Applying KVL in the circuit:

$$V - IR - jIX_L + jIX_C = 0 \quad V = IR + jX_L + jX_C$$

$$V = IR + jIX_L - jIX_C = IR + j\omega L + j\frac{1}{\omega C} = I(R + j\omega L - j\frac{1}{\omega C})$$

$$V = I \left\{ R + j(X_L - X_C) \right\} = I(R + j(\omega L - \frac{1}{\omega C}))$$

$$Z = R + j(\omega L - \frac{1}{\omega C})$$

$$I = \frac{V}{Z} \quad \dots \quad (i)$$

where, Z = Impedance

X_L = Inductance

X_C = Capacitance

R = Resistance

Impedance varies as the frequency of voltage changes because X_L & X_C both changes with change in frequency.

Since, $X_L = 2\pi f L$

$$\Rightarrow X_L \propto f$$

And, $X_C = \frac{1}{2\pi f C}$

$$\Rightarrow X_C \propto \frac{1}{f}$$

But resistance is independent of frequency.

This is the required expression for Resonance RLC series circuit.

$$2\pi f_0 = \frac{1}{\sqrt{LC}}$$

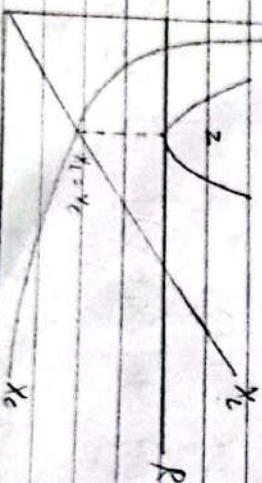


Fig: Variation of R , X_L and X_C with f

From above figure, the variation of X_L is a straight line passing through the origin, X_C with frequency is a curve approaching the two axis. And the resistance is independent of frequency. Hence it is a straight line parallel to frequency axis.

For a particular frequency f_0 the difference of X_L & X_C is equal to zero.
i.e. $X_L - X_C = 0$

$$\text{or, } X_L = X_C$$

$$\text{or, } 2\pi f_0 L = \frac{1}{2\pi f_0 C}$$

$$\text{or, } f_0^2 = \frac{1}{4\pi^2 LC}$$

$$\boxed{f_0 = \frac{1}{2\pi\sqrt{LC}}}$$

Q Resonance for R-L-C parallel circuit:

Let us consider R-L-C parallel circuit as shown below:

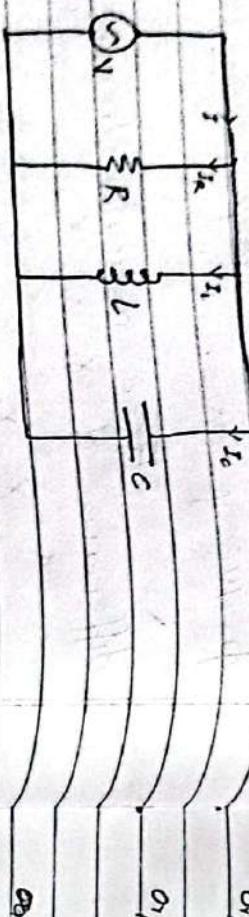


fig: RLC parallel circuit

$$I = I_R + I_L + I_C$$

~~$$I = IR + IL + IC$$~~

$$I = \frac{V}{R} + j \frac{V}{X_L} - j \frac{V}{X_C}$$

$$I = \frac{V}{R} + \frac{V}{jX_L} - \frac{V}{jX_C}$$

$$I = V \left(\frac{1}{R} + \frac{j}{X_L} - \frac{j}{X_C} \right)$$

$$\frac{I}{V} = \frac{1}{R} + \frac{j}{X_L} - \frac{j}{X_C}$$

~~$$\frac{I}{V} = \frac{1}{R} + j \frac{V}{(WC)^{-1}}$$~~

$$\frac{I}{V} = \frac{1}{R} + j \left(\frac{L}{X_L} - \frac{1}{X_C} \right)$$

~~$$\frac{I}{V} = \frac{1}{R} + j \left(\frac{L}{X_L} - \frac{1}{X_C} \right)$$~~

At resonance,

$$At \text{ Resonance}, \frac{1}{X_L} - \frac{1}{X_C} = 0 \quad \omega_C - \frac{1}{\omega_L} = 0$$

$$c_1, \frac{1}{2\pi f_0 L} - 2\pi f_0 C = 0$$

$$1 - 2\pi f_0 C \times 2\pi f_0 L = 0$$

$$2\pi^2 f_0^2 LC = 0$$

$$I = 4\pi^2 f_0^2 LC$$

$$I = f_0^2$$

$$4\pi^2 LC$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Band-width of Resonance Curve:



Band-width of a circuit is given by the band of frequency which lies between two points on either side of resonance frequency curve, where current I_0 decreased to $\frac{1}{\sqrt{2}}$ of maximum value of

current at resonance

PAGE
DATE

$$\Delta f = f_2 - f_1$$

$$I_o = \frac{V}{R}$$

Power at resonance = $I_o^2 R$

Now, At point A & B:

$$I_o = \frac{I_o}{\sqrt{2}}$$

∴ Power at A & B = $\left(\frac{I_o}{\sqrt{2}}\right)^2 \times R$

$$P_A = P_B = \frac{I_o^2 R}{2} = \text{half of power}$$

$$\begin{aligned} R^2 &= R^2 + (X_L - X_C)^2 \\ \therefore R^2 &= R^2 + (X_L - X_C)^2 \end{aligned}$$

Therefore, points A & B are called half-power points.

At any other frequency:

$$I = \frac{V}{Z} = \frac{V}{R+j(X_L-X_C)}$$

$$\text{or, } I = \frac{V}{\sqrt{R^2 + (X_L-X_C)^2}} \quad \dots \dots \quad (1)$$

$$I = \frac{I_o}{\sqrt{2}} = \frac{V}{\sqrt{R^2 + (X_L-X_C)^2}} \quad \dots \dots \quad (ii)$$

$$\therefore \frac{V}{\sqrt{2} R} = \frac{V}{\sqrt{R^2 + (X_L-X_C)^2}} \quad [\text{From (i) & (ii)}]$$

$$\therefore \frac{1}{\sqrt{2} R} = \frac{1}{\sqrt{R^2 + (X_L-X_C)^2}}$$

$$\text{or, } \sqrt{2} R = \sqrt{R^2 + (X_L-X_C)^2}$$

Squaring both sides:

$$\therefore R^2 = R^2 + (X_L - X_C)^2$$

$$\text{or, } R^2 = (X_L - X_C)^2$$

$$\text{or, } R = (X_L - X_C)$$

$$\text{or, } R = \omega L - \frac{1}{\omega C}$$

$$\text{or, } R - \omega L + \frac{1}{\omega C} = 0$$

$$\text{or, } R\omega C - \omega^2 LC + 1 = 0$$

$$\text{or, } LC\omega^2 - R\omega C - 1 = 0$$

At point A & B:

Comparing with $ax^2 + bx + c = 0$

Taking +ve sign:

$$\omega_2 = \omega_0 + \frac{R}{2L}$$

$$\omega = RC \pm \sqrt{R^2 C^2 + 4LC}$$

\therefore Bandwidth $\Delta\omega = \omega_2 - \omega_1$

$$= \frac{R}{2L} \pm \sqrt{\frac{R^2 C^2}{4L^2 C^2} + \frac{4LC}{4L^2 C^2}}$$

$$= \omega_0 + \frac{R}{2L} - \omega_0 + \frac{R}{2L}$$

$$= \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{L}{LC}}$$

$$\boxed{\Delta\omega = \frac{R}{L}}$$

$$= \frac{R}{2L} \text{ If } \frac{R^2}{4L^2} \ll \frac{1}{LC} \text{ then,}$$

Quality factor (Q-factor):

Quality factor gives the quality of resonance in accordance with selectivity of frequency. The large value of quality factor gives the sharp value of frequency or selective frequency and it is numerically given by:

$$Q\text{-factor} = \frac{\omega_0 L}{R}$$

Taking value of ω_0 only positive :

$$\omega = \omega_0 \pm \frac{R}{2L}$$

Now, Taking -ve sign:

$$\omega_1 = \omega_0 - \frac{R}{2L}$$

$$\therefore Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Q. Factor in series RLC resonating circuit:

It is defined as the ratio of voltage across inductor to the voltage at resonance.

It is also the voltage magnification in the resonating circuit.

$$Q\text{-factor} = \frac{V_L}{V}$$

$$= \frac{I_0 X_L}{I_0 R} \quad [\because I_0 = I]$$

$$= \frac{X_L}{R}$$

$$= \frac{\omega_0 L}{R} \quad [\because \omega_0 = \frac{1}{\sqrt{LC}}]$$

$$= \frac{\omega_0 Z}{X_C} \quad (\because V_C = V)$$

$$= \frac{L}{RC} \times \frac{1}{\omega_0 C} \quad (\because Z = \frac{L}{RC})$$

$$= \frac{L}{RC} \times \omega_0^2 C$$

$$= \frac{L}{R} \times \omega_0$$

$$\therefore Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

(ii) Quality factor in parallel RLC resonating circuit:

In parallel resonating circuit, Q-factor is the current magnification of the circuit at resonance.

It is the ratio of no. current across capacitor to the applied current.

$$\boxed{Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}}$$


$$Q\text{-factor} = \frac{I_C}{I}$$

$$= \frac{V_C}{V}$$

Steady state Response :

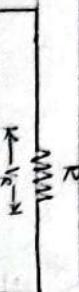(1) R-L Series Circuit :


Let us consider R-L series circuit with supplied AC voltage 'V', frequency f, as shown in figure below:




$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$

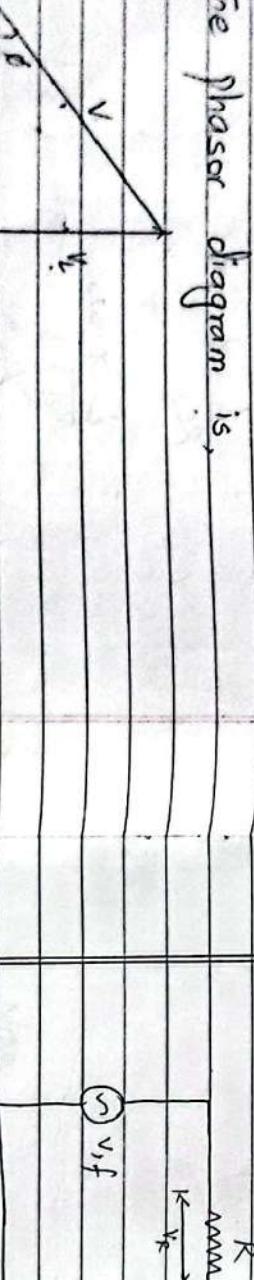(2) R-C Series Circuit :

Let us consider R-C series circuit with supplied AC voltage 'V', frequency f, as shown in figure below:



The phasor diagram is,

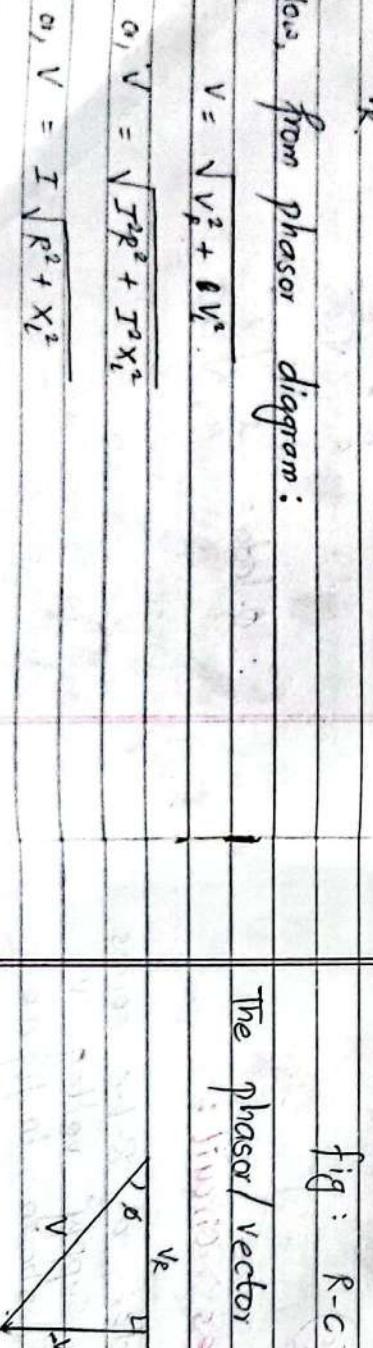

Now, from phasor diagram:

$$V = \sqrt{V_R^2 + V_L^2}$$

$$a_1 V = \sqrt{I^2 R^2 + I^2 X_L^2}$$

$$a_1 V = I \sqrt{R^2 + X_L^2}$$

fig : R-C series circuit

The phasor/ vector diagram is :

$$V = \sqrt{V_R^2 + V_C^2}$$

$$a_1 V = \sqrt{I^2 R^2 + I^2 X_C^2}$$



Now, from phasor diagram:

$$V = \sqrt{V_R^2 + (-V_L)^2}$$

$$\text{Or, } V = \sqrt{I^2 R^2 + I^2 X_L^2}$$


$$\text{Or, } V = I \sqrt{R^2 + X_L^2}$$

$$\text{Or, } V = IZ$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$\text{Now, } \tan \phi = \frac{P}{b}$$

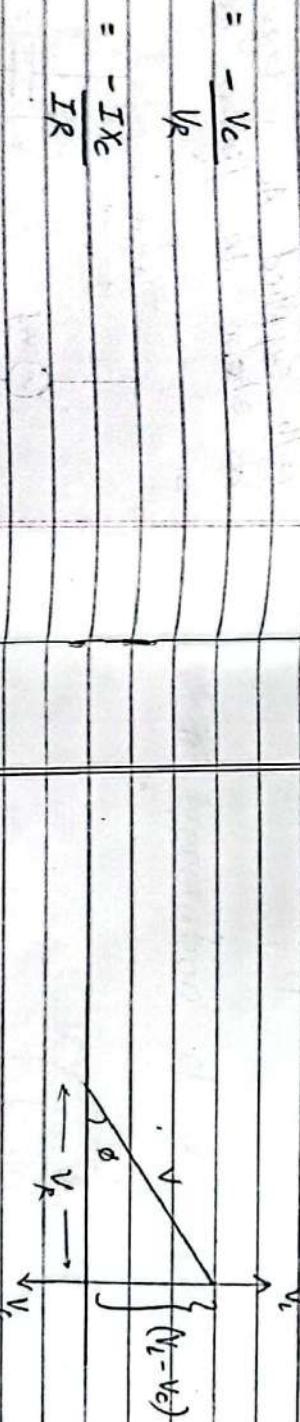The phasor diagram of RLC series circuit is:



Now, From the phasor diagram:

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\therefore \phi = \tan^{-1} \left(\frac{-X_C}{R} \right)$$

(3) **R-L-C series circuit:**

Let us consider a R-L-C series circuit with AC supply voltage 'V', frequency 'f' as shown in figure below:

$$\text{Or, } V = I \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{Or, } V = IZ$$

$$\text{Or, } V = \sqrt{I^2 R^2 + (I X_L - I X_C)^2}$$

Unit - 4**Poly phase AC circuit Analysis (3-Ø)**

[6 hrs]


$$\tan \phi = \frac{P}{b}$$

$$= \frac{V_L - V_C}{V_R}$$

$$= \frac{X_L - X_C}{R}$$

$$\therefore \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

The single phase AC circuit is suitable for most of the domestic applications but in the field of electrical engineering such as power transmission, electrochemical energy large industrial areas where power consumption is high, single phase is not applicable so to overcome this limitation a three phase system is ~~built~~ used.

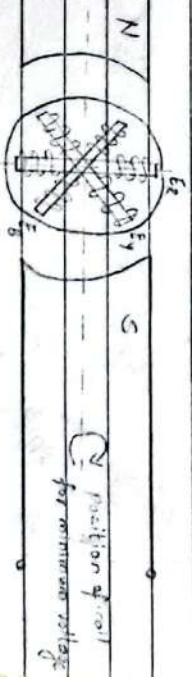Generation of 3-phase voltage/current:

C
Position of coil for maximum voltage

- In three phase system, three coils are mounted or ~~located~~ rotated in the armature which is displaced by $2\pi/3$ radian (120°). These coils have sinusoidally varying electromagnetic force or emf induced in them. The three phase may be

numbered 1, 2 & 3 or a, b & c or they are given three colours. The commercially used colours are Red, Yellow or White & blue, this is called RYB sequence.

The figure above shows the generation of three phase voltage. The graphical representation of three phase voltage is as shown below:

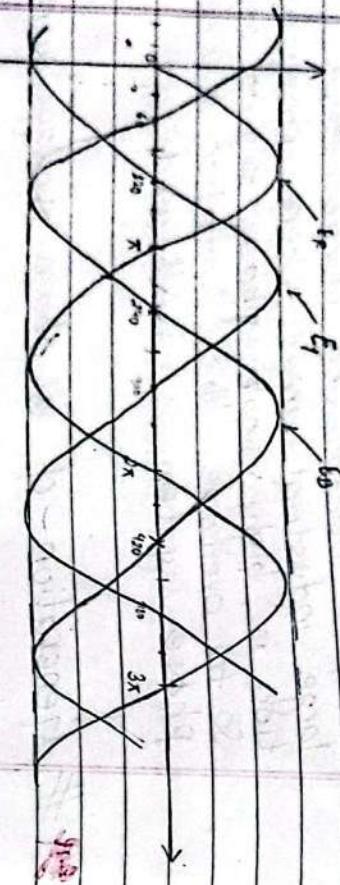


Fig: Graphical representation of 3-φ voltage

In this case,

$$E_R = E_m \sin \omega t$$

$$E_Y = E_m \sin \left(\omega t - \frac{2\pi}{3} \right)$$

$$E_B = E_m \sin \left(\omega t - \frac{4\pi}{3} \right)$$

$$= E_m \sin \left(\omega t + \frac{2\pi}{3} \right)$$

~~Advantages~~

Advantages of 3-φ system:

(i) Domestic and industrial power can be provided from same source.

(ii) Voltage regulation is of 3-φ system is better than single phase system.

(iii) Torque produced by 3-φ voltage is maximum.

(iv) The amount of conductor wire needed to transfer same amount of power is less for three phase system. Thus, it is more economical.

(v) For a given size of frame 3-φ generator provides more output.

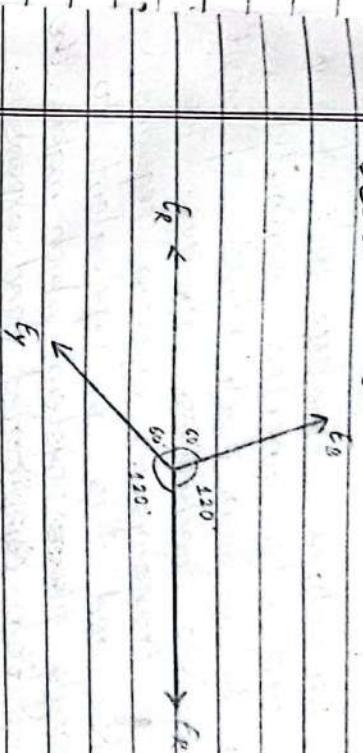


Fig: Phasor diagram of 3-φ system

Interconnection of 3- ϕ system :

If the three armature coils of 3- ϕ system are interconnected separately as shown below then each phase of circuit requires two conductors or wires. The resulting transmission system requires six wires and this is equivalent to three single phase system which makes the whole system complicated and expensive.

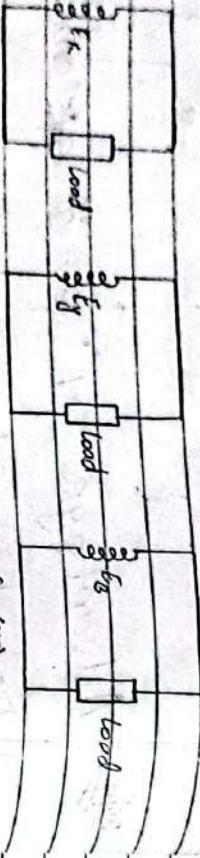


fig (i) fig (ii) fig (iii)

Hence, a 3- ϕ system are generally inter connected which results in the saving of copper wire. The general method of inter connection are:

- Balanced star or Wye (γ) connected system.
- Balanced Delta or mesh (Δ) connected system.

Balanced System:

A balanced system is one in which

- The voltage in all phase are equal in magnitude and offer a phase difference of 120° or $\frac{2\pi}{3}$ radian.

(ii) The current in the three phase are equal in magnitude and offer a phase difference 120° or $(\frac{2\pi}{3})^c$.

(iii) A three phase balance load is one in which load connected across three phases are identical or equal

① Balanced Star or Wye (γ) connected system:

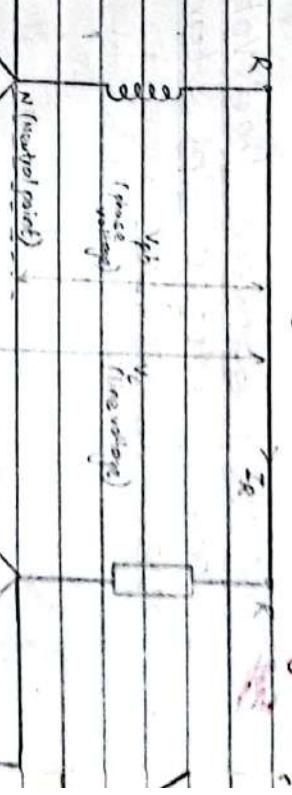


fig : 4-wire 3- ϕ star (γ) connected system


The star connected system is interconnected as shown in figure above, the end of three coils are connected at a point which is known as neutral point. Such an interconnected system is known as 4-wire 3- ϕ star (γ) connected system.

At neutral point,

$$I_N = I_R + I_S + I_Y$$

The emf between any line and neutral point is called phase emf or voltage and the emf between any two lines gives the line-to-line emf or simply line emf. It is denoted by E_L or V_L .

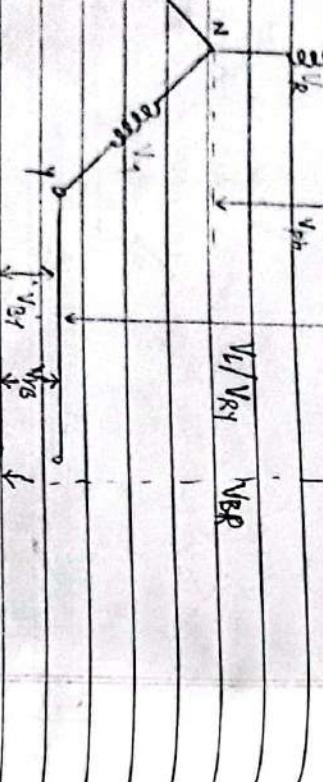Relation Between Line Voltage and Phase voltage in star connected 3-Ø system:



Let V_R , V_Y & V_B be the phase voltage and V_{RR} , V_{YY} & V_{BB} be the line voltage. Then it is observed that the line voltage V_{RR} is vector difference of V_R & V_Y .

$$V_{RR} = V_R - V_Y$$

$$V_{YY} = V_Y - V_B$$

$$V_{BB} = V_B - V_R$$

Now, from parallelogram law of vector addition:

$$V_{RY} = \sqrt{V_R^2 + V_Y^2 + 2V_R V_Y \cos 60^\circ}$$

The phasor diagram of 3-Ø Y-connected system is:

$$V_{RY} = \sqrt{V_R^2 + V_Y^2 + 2V_R V_Y \cos 60^\circ}$$

$$\Rightarrow V_{RY} = \sqrt{V_R^2 + V_Y^2 + 2V_R V_Y \cos 60^\circ}$$

$$\text{or, } V_{ky} = \sqrt{V_k^2 + V_y^2 + 2V_k V_y \times j\beta} \quad \dots \dots \quad (1)$$

$$V_{ky} = \sqrt{V_k^2 + V_y^2 + V_k V_y} \quad \dots \dots$$

F In star (γ) connected system:

$$V_k = V_y = V_B = V_{ph}$$

$$V_{ky} = V_{Bk} = V_{kB} = V$$

: Eqn ① becomes :

$$V_i = \sqrt{V_{ph}^2 + V_{ph}^2 + V_{ph}^2}$$

$$[V_i = \sqrt{3} V_{ph}]$$

$$[I_L = I_{ph}]$$

This is the required relationship between line voltage and phase voltage, line current and phase current in star connected three phase system.

(2) **Balanced Delta (Δ) connected System:**

The phasor diagram of delta connected 3- ϕ system is shown below :


P.7.0

$$I_B = I_{Bk} - I_{By}$$

Now, From figure:


$$I_R = I_{Rk} - I_{Ry}$$

$$I_Y = I_{Yk} - I_{Py}$$

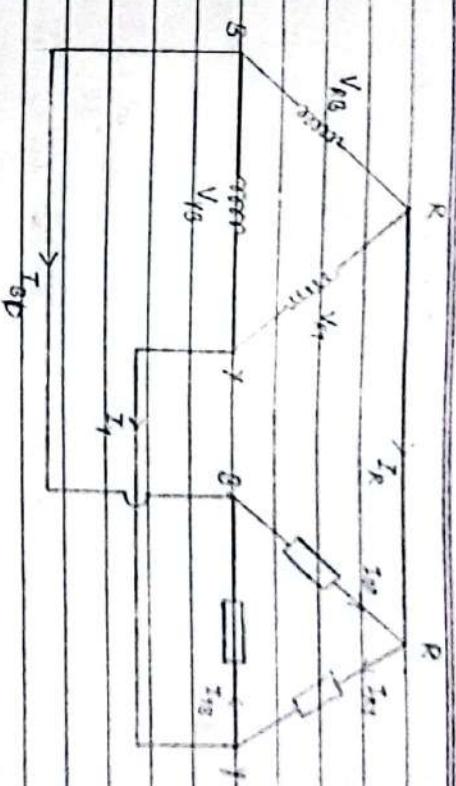

connected 3- ϕ system.

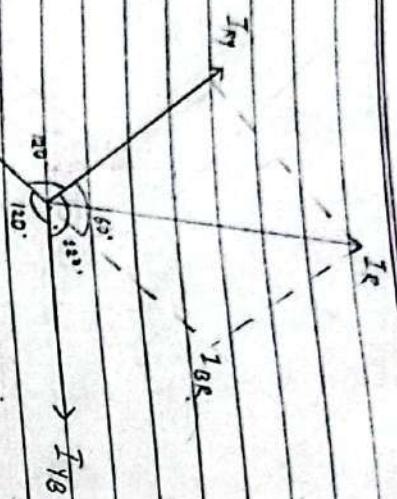Difference between star (Y) & Delta (Δ) connected system:



Applying parallelogram of vector addition:

$$I_R = \sqrt{I_{Ay}^2 + I_{Ax}^2 + 2 I_{Ay} I_{Ax} \cos 60^\circ}$$

$$= \sqrt{I_{Ay}^2 + I_{Ax}^2 + I_{Ay} \cdot I_{Ax}}$$

In Δ (delta) connected system:

$$I_R = I_B = I_y = I$$

Three Phase Power Measurement:

$$I_{Ay} = I_{Bx} = I_{Cz} = I_{ph}$$

$$\therefore I_L = \sqrt{I_{ph}^2 + I_{ph}^2 + I_{ph}^2}$$

$$\boxed{I_L = \sqrt{3} I_{ph}}$$

$$\text{And, } \boxed{V_L = V_{ph}}$$

This is the required relationship between line current and phase current in balanced delta

In the 3- ϕ power system

"Since the phase impedance of a balanced star or delta connected load contains equal component, the phase power is $\frac{1}{\sqrt{3}}$ rd of total power. As from the definition of power the voltage across load impedance and current in the impedance can be used to calculate the power for phase."

one, two or three wattmeters can be used to measure the total power. A wattmeter may be considered to be a voltmeter and an ammeter connected in the same box which has a deflection proportional to the $V_m I_{rms} \cos\phi$ which is equal to $VI \cos\phi$, where ϕ is the angle between voltage and current.

Hence, a wattmeter has two voltage terminals and two current terminals. It can be used for the power measurement in balanced or unbalanced star and delta connected system.

Three phase power measurement by two wattmeter methods:

Several methods are available for measuring the power delivered to the load. The most commonly used technique is two wattmeter method.

(i) Delta Connected system:


$$P.T.O$$

$$\text{or, } P = V_R I_R + V_Y I_Y + V_B I_B$$

$$\text{or, } P = V_R I_R + V_Y I_Y + I_A (V_R - V_Y)$$

$$\text{or, } P = V_R I_R + V_Y I_Y - V_R I_B - V_Y I_B$$
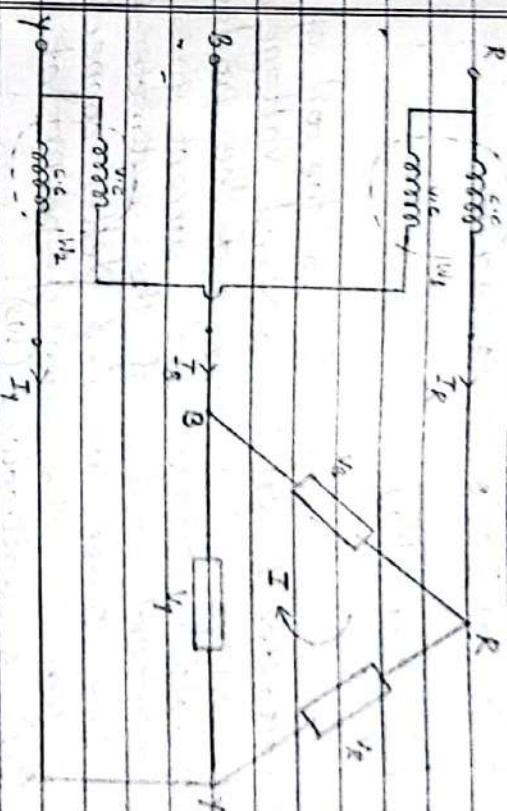
$$\text{or, } P = V_Y I_Y - V_Y I_B + V_R I_R - V_R I_B$$



C.C. \rightarrow Current coil
V.C. \rightarrow Voltage coil

$W_1, W_2 \rightarrow$ Wattmeter 1 & 2

Now, Applying kvl in the loop:

$$V_R + V_Y + V_B = 0$$

$$V_B = -(V_R + V_Y) \quad \dots \dots \dots (i)$$

Instantaneous Power is:


$$P = VI$$

$$\Delta P = V_I (I_p - I_B) + V_R (I_R - I_B)$$

$$\Delta P = W_1 + W_2$$

The current through the coil of wattmeter 1 (W_1) is I_p and voltage across its voltage coil is V_I and the product of V_I & I_p gives the resultant power of the wattmeter 1. Hence, power in 3- ϕ delta connected system is the sum of power at wattmeter 1 (W_1) & wattmeter 2 (W_2).

(ii) Star Connected System:

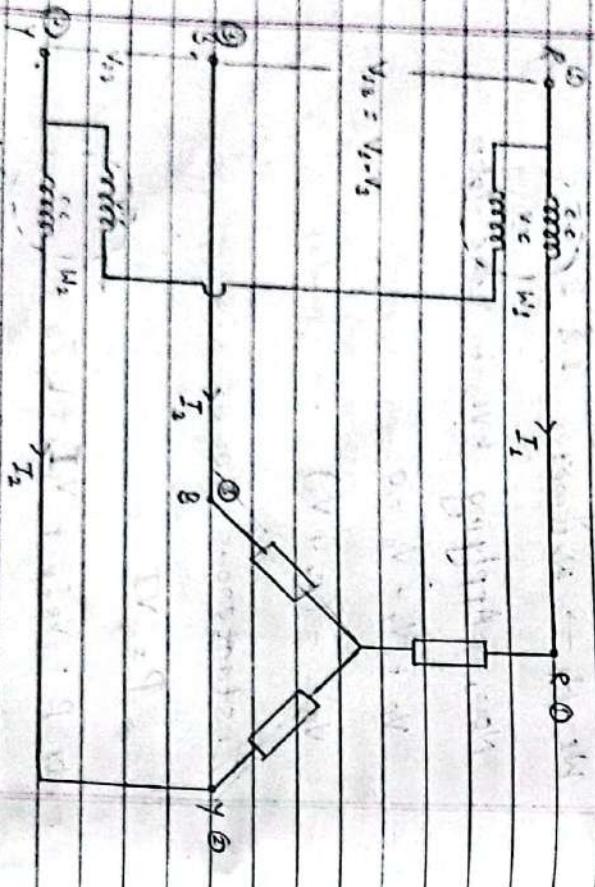

$$\Delta P = W_1 + W_2$$

power in star connection:

The total active or real power in the circuit is the sum of the individual 3- ϕ powers. Total active power $\Delta P = 3 \times$ individual power per phase = $3 V_{ph} I_{ph} \cos \phi$

$$= 3 \times V_{ph} I_{ph} \cos \phi = \sqrt{3} V_L I_{Lavg}$$

$$P = \sqrt{3} V_L I_{Lavg} \quad [V_L = \sqrt{3} V_{ph} \& I_{Lavg} = I_p]$$

$$Q = \sqrt{3} V_L I_{Lavg} \quad [V_L = \sqrt{3} V_{ph} \& I_{Lavg} = I_p]$$

$$\& \text{Total reactive power } Q = \sqrt{3} V_L I_{Lavg} \sin \phi \quad \phi = \angle(V_L, I_{Lavg})$$

Instantaneous power is:

$$P = VI$$

$$\Delta P = V_1 I_1 + V_2 I_2 + V_3 I_3$$

$$\Delta P = V_1 I_1 + V_2 I_2 - V_3 (I_1 + I_2)$$

$$\Delta P = I_1 (V_1 - V_3) + I_2 (V_2 - V_3)$$

$$\Delta P = I_1 V_{13} + I_2 V_{23}$$

Applying KCL at neutral point:

and total apparent power

$$(S) = \sqrt{3} V_L I_{Lavg}$$

$$I_1 + I_2 + I_3 = 0 \quad \dots \dots \dots (1)$$

Chapter-5

Electric Machines

Review of magnetic circuit:

A magnetic circuit is made up of one or more closed loop paths containing a magnetic flux. The flux is usually generated by permanent magnets or electromagnets and confined to the path by magnetic cores consisting of ferromagnetic materials like iron, although there may be air gaps or other materials in the path.

Magnetic circuits are employed to efficiently channel magnetic fields in many devices such as electric motors, generators, transformers, relays etc.

Terminologies:

(1) Magnetic flux (Φ):

The number of magnetic field lines of force created in a magnetic field is known as magnetic flux. Its unit is Weber (Wb).

(2) Flux Density (B):

The number of magnetic lines of force created in a magnetic circuit per unit

area normal to the direction of flux line is known as flux density.

ie

$$B = \frac{\Phi}{A}$$

Its unit is Weber / sq.m (Tesla).

(3) Magneto motive force (F) :

Force which drives or tends to drive the magnetic flux through a magnetic circuit is magneto motive force. i.e

$$\text{MMF} = \text{No. of turns} \times \text{current} = NI$$

Its unit is AT (ampere turns).

(4) Magnetic field strength (H):

The magneto motive force per meter length of the magnetic circuit is known as magnetic field strength (H). i.e

$$H = \frac{NI}{L}$$

Its unit is AT/meter.

(5) Permeability (μ):

A property of a magnetic material which indicates the ability of magnetic circuit

to carry electromagnetic flux is known as permeability.
It is also ratio of flux density to the magnetizing force.

$$\boxed{\mu = \frac{B}{H}}$$

Its unit is Henry/meter.

Permeability of free space or air or non-magnetic material is:

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

(6) Relative Permeability (μ_r):

The ratio of the flux density produced by a given MMF in a magnetic material to the flux density produced in a non magnetic material.

$$\mu_r = \frac{\mu}{\mu_0} = \frac{\mu H}{\mu_0 H} = \mu$$

$$\therefore \mu = \mu_0 \mu_r$$

(7) Reluctance (S):

It is the opposition of a magnetic circuit to setting up of a magnetic flux in it.

$$F = mmf = H \cdot l \quad [\because H = \frac{NI}{l}]$$

$$B = \mu H$$

$$\frac{\phi}{F} = \frac{BA}{H \cdot l} = \frac{\mu_0 \mu_r A}{l}$$

$$= \frac{\mu H A}{l}$$

$$\phi = \frac{F}{L} = \frac{A}{S} = \frac{A \cdot l}{\mu_0 \mu_r A} = \frac{l}{\mu_0 \mu_r}$$

$$\boxed{S = \frac{l}{\mu_0 \mu_r}}$$

'S' is called reluctance of the magnetic circuit.

$$\boxed{\text{Reluctance} = \text{MMF}/\text{magnetic flux}}$$


$$\text{Its unit is AT/Wb.}$$

Magnetic Circuit:

The complete closed path followed by any group of magnetic lines of flux is referred to a magnetic circuit.



Equivalent electrical circuit

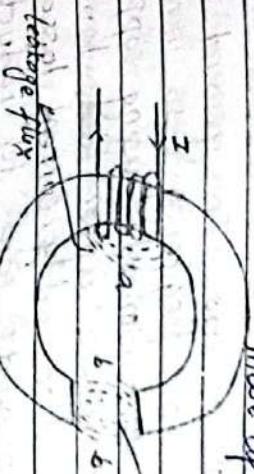

Analogy with Electric circuits:

Similarities:

Electric circuit	Magnetic circuit
Potential difference (EMF)	Magnetomotive force (MMF)
EMF, volt (V)	MMF, ampere turn(AT)

The flux that does not follow the intended path in the magnetic circuit is known as leakage flux.

Magnetic Circuits losses:

There are following two types of circuit losses:

(1) Eddy Current losses:

Eddy current losses are caused due to conduction of current and is reduced by laminating the core, and insulating to an extent, one leaf of the core from another.

Difference:

Electric circuit

Magnetic circuit

- (1) Current actually flows (2) flux is created but does not flow.

- (3) Circuit may be open (4) circuit is always closed.

- (5) Circuit is always closed.

leakage Flux: Eddy current losses can be reduced by using magnetic core made up of very thin lamination

(2) Hysteresis Losses:

Hysteresis loss is due to residual magnetization and depends on core. In general this loss increases as frequency is increased. The losses are minimized using copper wire for the coils, to reduce copper loss, laminating the core to reduce eddy current losses and selecting appropriate cores for reduction of hysteresis loss.

B to the energy required to

alternately magnetise & demagnetise the core as the magnetising current

represents the core loss.

figure of hysteresis loss

The Magnetic Hysteresis loop above shows the behavior of a ferromagnetic core graphically as the relationship between \mathbf{B}_B and \mathbf{H} is non-linear. Starting with an unmagnetised core both \mathbf{B} and \mathbf{H} will be at zero, point O on the magnetisation curve.

If the magnetisation current I is increased in a positive direction to some value the magnetic field strength H increases linearly with I and the flux density B will also increase as shown by the curve from point O to point a as it heads towards saturation.

Magnetic Hysteresis :

- The lag or delay of a magnetic material is known commonly as Magnetic Hysteresis, relates to the magnetisation

Now if the magnetising current in the coil is reduced to zero the magnetic field around the core reduces to zero but the

properties of a material by which it firstly becomes magnetised and then de-magnetised. We know that, the magnetic flux generated by an electromagnetic coil is the amount of magnetic field or lines of force produced within a given area and that it is more commonly called "Flux Density".

Given the symbol B with the unit of flux density being the Tesla (T).

$$B = \frac{\Phi}{A} \quad \text{and} \quad \Phi = \mu_0 H$$

magnetic field around the flux - area magnetic flux does not reach zero due to the residual magnetism present within the core and this is shown on the curve from point a to point b.

To reduce the flux density at point b to zero we need to reverse the current flowing through the coil. The magnetic force which must be applied to null the residual flux density is called a ' coercive force'. This ~~ext~~ coercive force reverses the magnetic field re-arranging the molecular magnets until the core becomes unmagnetised at point c.

An increase in the reverse current causes the core to be magnetised in the opposite direction and increasing this magnetisation current will cause the core to reach saturation but in the opposite direction, point d on the curve which is symmetrical to point a. If the magnetising current is reduced again to zero, the residual magnetism present in the core will be equal to the previous value but in reverse at point e.

Again, reversing the magnetising current flowing through the coil, this time into a positive direction will cause the magnetic flux to reach zero, (point f) on the curve and as before increasing the magnetisation

cured further in a positive direction will cause the core to reach saturation at point g.

Then the B-H curve follows the path of a-b-c-d-e-f-g as the magnetising current flowing through the coil alternates between a positive and negative value such as the cycle of an AC voltage. This path is called Magnetic hysteresis loop.

~~#~~ Transformer:

The transformer is very simple static (or stationary) electromagnetic passive electrical device that works on the principle of Faraday's law of induction.

It does this by linking together two or more electrical circuits using a common oscillating magnetic circuit which is produced by the transformer itself. A transformer operates on the principle of "electromagnetic induction" in the form of mutual induction."

A transformer is a device that connects one AC voltage to another AC voltage at the same frequency.

It consists of one or more coil(s) of wire wrapped around a common ferromagnetic core. These coils are usually not connected electrically together. However, they are connected through the common

magnetic flux confined to the core.

Working Principle:

A single phase voltage transformer basically consists of two electrical coils of wire, one called the 'primary winding' and another called the 'secondary winding' that are wrapped together around a closed iron magnetic iron circuit called a 'core'.

This soft iron core is not solid but made up of individual laminations connected together to help reduce the core's losses. These two windings are electrically isolated from each other but are magnetically linked through the common core allowing electrical power to be transformed from one coil to the other.

In other words, for a transformer there is no direct electrical connection between the two coil windings, thereby giving it the name also of an isolation transformer.

Generally, the primary winding of a transformer is connected to the input voltage supply and converts or transforms the electrical power into a magnetic field. While the secondary winding converts this magnetic field into electrical power producing the required output voltage as shown below:

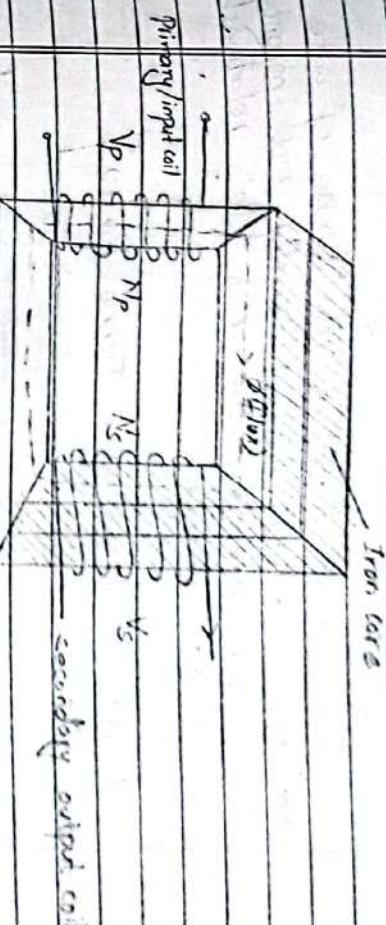


fig: Transformer Construction

fig: Transformer Symbols

Where,

$$V_p = \text{Primary Voltage}$$

$$V_s = \text{Secondary Voltage}$$

$$N_p = \text{No. of Primary Windings}$$

$$N_s = \text{No. of Secondary Windings}$$

$$\phi = \text{Flux linkage}$$

A transformer is all about 'ratios', and the turns ratio of a given transformer will be the same as its voltage ratio. In other words for a transformer:

turns ratio = voltage ratio

The actual number of turns of wire of any winding is generally not important just the turns ratio and this relationship is given as:

$$\frac{N_p}{N_s} = \frac{V_p}{V_s} = n = \text{Turns Ratio}$$

Note that the two coil windings are not electrically connected but are only linked magnetically.

A single phase transformer can operate to either increase or decrease the voltage applied to the primary winding.

When a transformer is used to increase the voltage on its secondary winding with respect to the primary it is called a Step-up Transformer.

When it is used to decrease the voltage on the secondary winding with respect to the primary it is called Step-down Transformer.

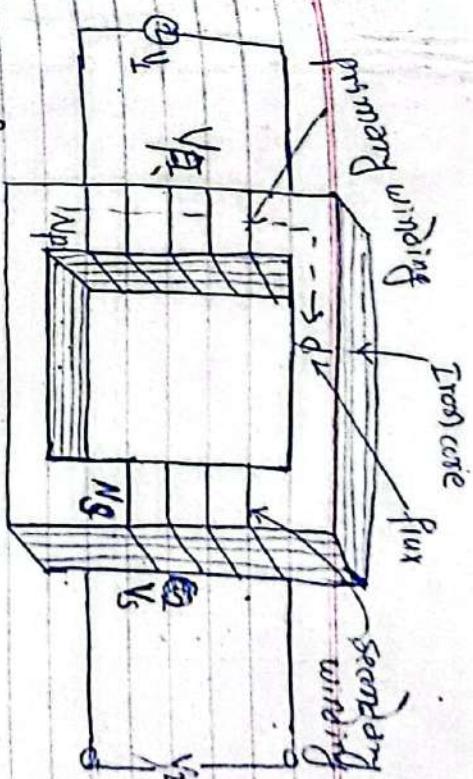


fig: construction of transformer

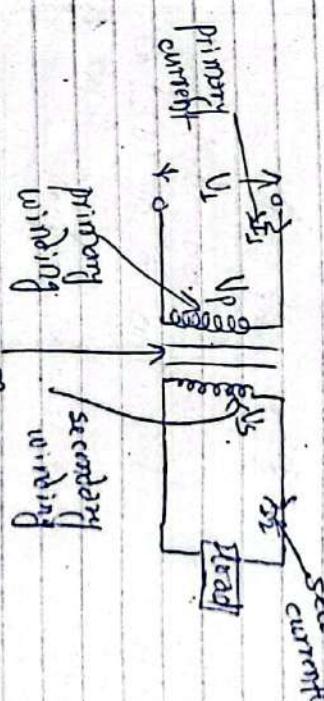


fig: Transformer circuit symbol with load

Ques:
EMF equation of transformer:

(N turns)

laminated Iron core

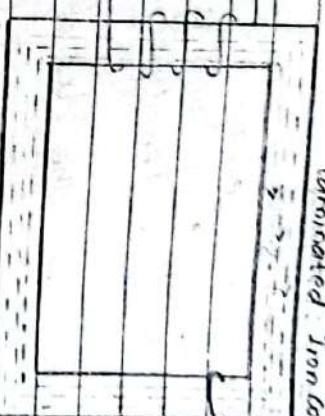
are
on
ba
or
pr
inc
wi

fig:

As the magnetic flux varies sinusoidally.

$$\phi = \phi_{\max} \sin \omega t$$

then the basic relationship between induced emf. (E) in a coil winding of N turns is given by:

$E = \text{turns} \times \text{rate of change of flux}$

$$E = N \cdot \frac{d\phi}{dt}$$

$$\left[\text{constant} = \sin(\omega t) \right]$$

$$E = N \times \omega \times \phi_{\max} \times \cos(\omega t)$$

$$= \sin \omega t$$

Now, for maximum emf $\cos(\omega t) = 1$, so we have:

$E_{\max} = N \omega \phi_{\max}$

$$E_{\text{rms}} = \frac{N \omega \times \phi_{\max}}{\sqrt{2}} \quad [\because E_{\text{rms}} = \frac{E_{\max}}{\sqrt{2}}]$$

$$= \frac{2\pi}{\sqrt{2}} f \times N \times \phi_{\max}$$

Topic:

B

$$\therefore \text{Ems} = 4.44 f N \phi$$

Thus, $E_p = 4.44 f N \phi$ where, f = flux frequency in Hertz

N = no. of coil windings
 ϕ = the flux density in webers.

This is known as the transformer emf equation.

For primary winding emf, N_p will be the number of primary turns & for the secondary winding emf, N_s will be the number of secondary turns (N_s).


Transformers require an alternating magnetic flux to operate correctly, transformers cannot therefore be used to transform DC voltages or currents, since the DC voltage or current in the secondary winding must be changing to induce magnetic field must be changing to induce a voltage in the secondary winding. In other words, transformer don't operate on DC voltages.

Equivalent Circuit of Transformer:


Equivalent impedance of transformer is essential for estimating different parameters of electrical power system, so it may be required to calculate total internal impedance of an electrical power transformer viewing prim from primary side or secondary side as per requirement. This calculation

requires equivalent circuit of transformer referred to primary or equivalent circuit of transformer referred to secondary sides respectively.

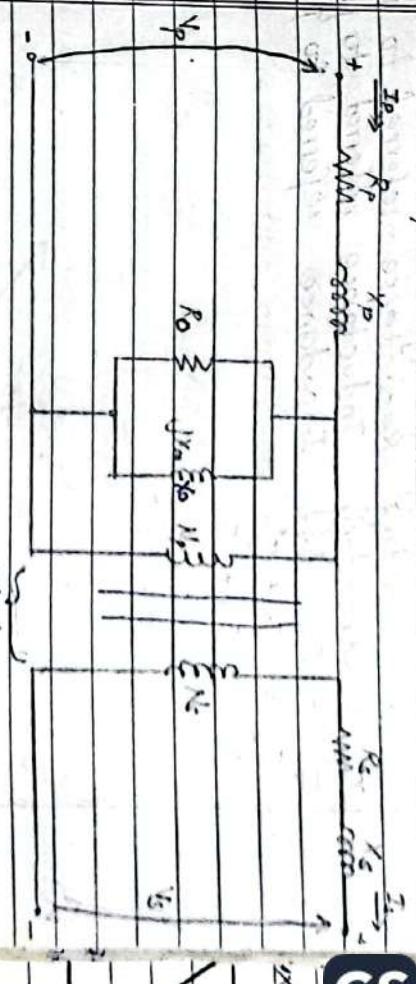The exact circuit diagram of real transformer:



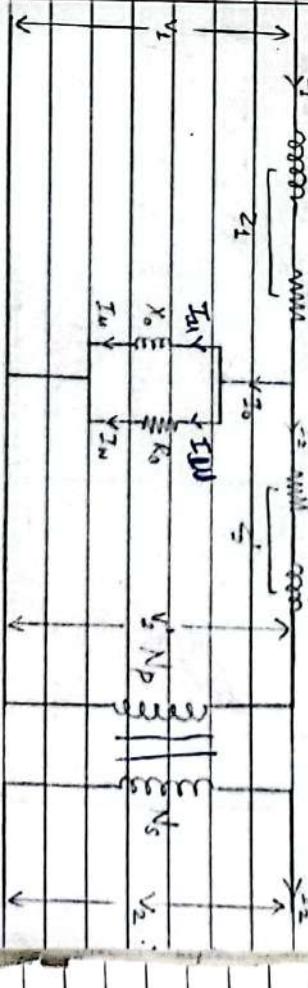Equivalent circuit of Transformer referred to Primary:



where, V_p = Primary voltage, I_p = no-load primary current R_o = core loss resistance X_o = magnetizing reactance

X_1 = Primary Inductance
 R_1 = Primary Resistance

Z_1 = Primary Impedance
 I_u = Magnitizing component of current

I_w = Core loss component of current
 I'_w = Secondary current referred to primary

V' = Secondary voltage referred to primary
 R'_2 = Secondary resistance referred to primary

Z'_2 = Secondary inductance referred to primary
 I_s = Secondary current referred to primary

$I_o = I_u + I'_w$
 $I_o = I_{ut} + I_w$

Now it is found that total primary current I_1 has two components one is no load component I_o and other is load component I'_1 . As this primary current has two components or branches so there must be a parallel path with primary winding of transformer. This parallel path of electric current is known as excitation branch of equivalent circuit of transformer.

The resistive and reactive branches of the excitation circuit can be represented as:

$$R_o = \frac{E_1}{I_o} \quad \text{and} \quad E_{X_o} = E_1 - I_o X_o$$

Let us consider the transformation ratio be:

$$k = \frac{N_2}{N_1} = \frac{I_o}{E_1}$$

Now, if we see the voltage drop in secondary from primary side then it would be $1/k$ times greater and would be written as:

$$Z_2 \cdot I_2 / k$$

Again, $I'_2 \cdot N_1 = I_2 \cdot N_2$

$$\Rightarrow I_2 = \frac{I'_2 \cdot N_1}{N_2}$$

$$\Rightarrow I_2 = I'_2 / k$$

Fig: Vector diagram of Transformer on load


$$\text{Therefore, } Z_2 \cdot I_2 / k = Z_2 \cdot I'_2 / k^2 = Z_2 \frac{I_2}{k^2} = \frac{I_2}{k^2} = \frac{I_2}{k^2}$$

From above equation,
Secondary impedance of transformer
referred to primary is:
 $Z_2' = Z_2/k^2$

Hence,

$$R_2' = \frac{R_2}{k^2}$$

$$\text{And, } X_2' = \frac{X_2}{k^2}$$

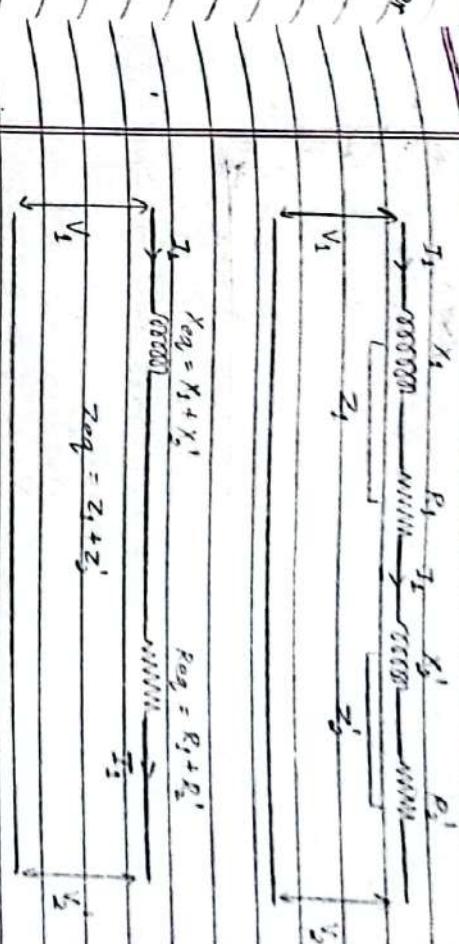

So, the complete equivalent circuit of transformer referred to primary is shown in the figure above.

Approximate Equivalent Circuit of Transformer:

Since I_0 is very small compared to I_1 , it is less than 5% of full load primary current. It changes the voltage drop insignificantly. Hence, it is good approximation to ignore the excitation circuit in approximate equivalent circuit of transformer.

The winding resistance and reactance being in series can now be combined into equivalent resistance and reactance of transformer referred to any particular side. In this case it is side.

Here, $V_2' = \frac{V_2}{k}$

Equivalent circuit of Transformer referred to Secondary:

In similar way approximate equivalent circuit of transformer referred to secondary can be drawn. Here, equivalent impedance of transformer referred to secondary, can be derived as:

$$Z_1' = Z_1 \cdot k^2$$

Therefore, $R_1' = R_1 \cdot k^2$

$$\text{and, } X_1' = X_1 \cdot k^2$$

$$\text{Here, } V_1' = V_1 \cdot k$$

P.T.O

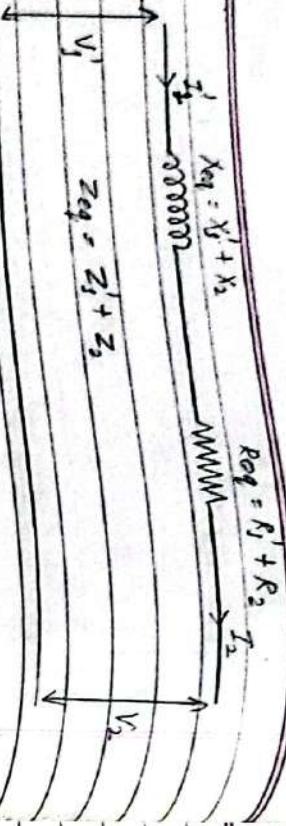


fig: Approximate equivalent circuit of transformer referred to secondary

Open Circuit Test:

The open circuit test, or no-load test is one of the methods used in electrical engineering to determine the no load impedance in the excitation branch of a transformer.

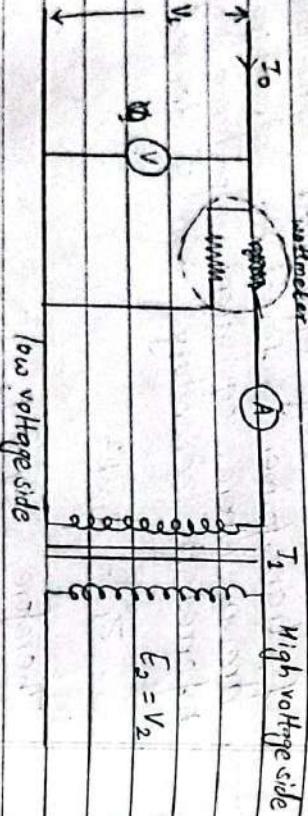


fig: circuit diagram for open circuit test
Short g.
The secondary of the transformer is left open-circuited. A wattmeter is connected to the primary. An ammeter is connected in series with the primary winding. A voltmeter is optional since the applied voltage is the same as the voltmeter reading. Rated voltage is applied at primary.

Now, the components of no-load circuit

$$I_o / I_m = \frac{V_1}{V_m} \sin \phi \quad I_o = \sqrt{I_{L0}^2 + I_{m0}^2}$$

$$R_o = \frac{V_1}{I_m}$$

These values are referred to LV side of the transformer. Where, V_1 is the wattmeter reading.


Hence it is seen V_1 is the applied rated voltage. That open circuit I_o is the no-load voltage. I_m is the magnetizing component of core losses. I_{L0} is no load current of transformer. I_m is the core loss component of transformer parameters - no load current of the equivalent circuit.

Short circuit test:

Short g.
The purpose of short circuit test is to determine the series branch parameters of the equivalent circuit of a real transformer.

P.T.O

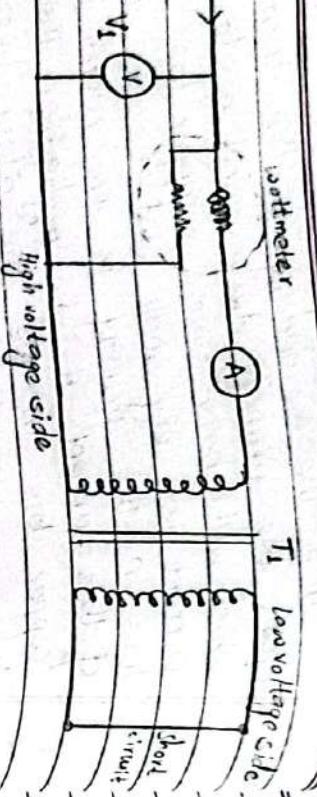X_1 is the reactance as viewed from the primary.



The test is conducted on the high voltage (H.V) side of the transformer where the low voltage (L.V) side or the secondary is short circuited. The supply voltage required to circulate rated current through the transformer is usually very small and is of the order of a few percent of the nominal voltage and this voltage is applied across primary. Thus the wattmeter reading measures only the full load copper losses.

$$W = I_1^2 R_{01}$$

short ckt test gives copper losses of transformer

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2}$$

resistance and reactance of the transformer.

$$Z_{01} = \frac{V_1}{I_1}$$

These values are referred to the H.V side of transformer where,

W is the full load copper loss.

V_1 is the applied voltage.

I_1 is the rated current

R_{01} is the resistance as viewed from the primary.

Z_{01} is the total impedance as viewed from the primary.

DC Machines:

A dc machine is a device which converts mechanical energy into electrical energy and vice-versa.

When the device converts mechanical energy into electrical, then it is called generator and if it converts electrical energy into mechanical energy then it is known as motor. Thus electrical machines can be made to work either a generator or motor.

Generators and motors are very similar to each other in essential parts and construction.

An electric motor is an electric machine that converts electrical energy into mechanical energy.

In normal motoring mode, most electric motors operate through the interaction between the an electric motor's magnetic field and winding currents to generate force within the motor. Of

Motor Construction:

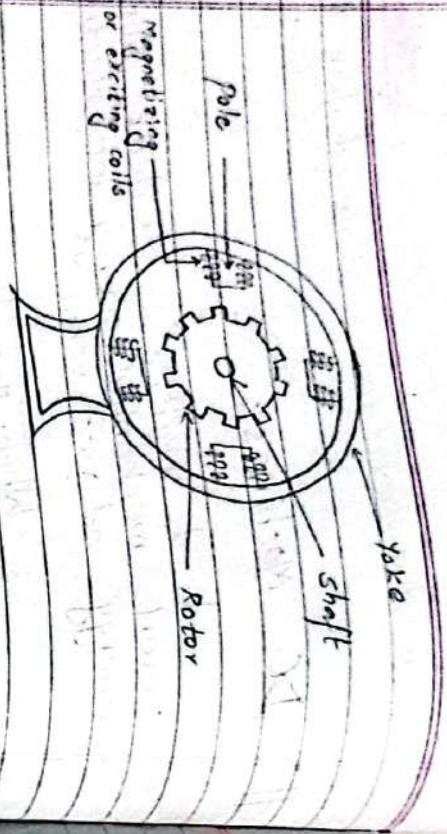


fig: construction of motor

(1)

Rotor:

In an electric motor the moving part is the rotor which turns the shaft to deliver the mechanical power. The rotor usually has conductors laid into it which carry currents that interact with the magnetic field of the stator to generate the forces that turn the shaft. However, some rotors carry permanent magnets, and the stator holds the conductors.

(2)

stator:

The stationary part is the stator, usually has either windings or permanent magnets.

(3)

Air gap:

In between the rotor and stator is the air gap. The air gap has important effects, and is generally as small as possible, as a large gap has a strong


Types of DC Generators:

The device which converts mechanical energy into electrical energy is known as generator. There are two types of DC generators: Ac generators & DC generator. There are two types of DC generators

- ① Separately excited DC generator
- ② Self excited DC generator

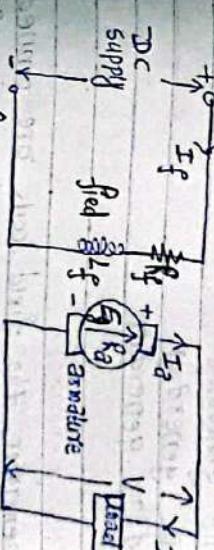(1) Separately excited DC generator:

A DC generator whose field winding (or coil) is energized by a separate or external DC source is called a separately excited DC generator. The flux produced by the poles depends upon the field current with the unsaturated region of magnetic materials of the poles i.e. flux is directly proportional to the field current. But in the saturated region, the flux remains constant. Separately excited DC generators are rarely used in practice.



Here, fig: separately excited DC generator

from. above circuit,

$$\text{terminal voltage} (V) = E_g - I_a R_a$$

If the contact brush drop is considered, then terminal voltage becomes

$$V = E_g - I_a R_a - 2V_b \text{ emf of motor.}$$

power developed across armature = $E_g \cdot I_a$

Where,

E_g = back emf

I_a = armature current

output power = $V \cdot I_a$

$$= V \cdot I_a \quad [\because I_a = I_f + I_a] \quad \text{or}$$

$$= E_g \cdot I_a - I_a^2 R_f$$

$$= I_a(E_g - I_a R_f)$$

$$= I_a V_A$$

(2) Self excited DC generators:

self excited DC generator is a device in which the current to the field winding is supplied by the generator itself. The self excited DC generator is further classified as:

- (a) series DC generator
- (b) shunt DC generator
- (c) compound DC generator

(i) Series DC generator:

In series DC generator, the field coils are connected in series with the armature winding. The series field winding carries the armature current. The series field winding consists of a few turns of wire of thick wire of larger cross-sectional area and having low resistance usually of the order of less than 1Ω because the armature current has a very large value. Such types of series DC generator is also rarely used in practice.

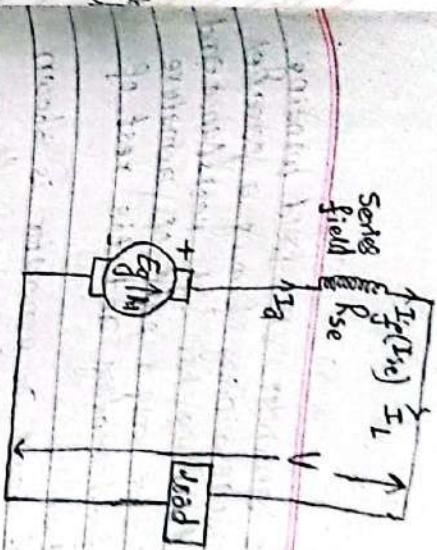


fig: Series DC generator

From figure, Terminal voltage is given by

$$V = E_g - I_a R_a - I_a R_{se} \quad [R_{se} = \text{series field resistance}]$$

$$\text{or } V = E_g - I_a R_a - I_a R_{se} \quad [R_{se} = \text{series field resistance}]$$

If the brush contact drop is included, then terminal voltage becomes,

$$V = E_g - I_a (R_a + R_{se}) - 2V_b$$

$$\text{power developed} = E_g I_a$$

$$\text{output power} = V \cdot I_a$$

Note: The flux developed by the series field winding is directly proportional to the current flowing through it.

(b) shunt DC generator

In a shunt DC generator, the field winding is connected across the armature winding forming a parallel circuit. The field winding has high resistance and more number of turns so that only a part of armature current passes through field winding and the rest of current passes through load.

The connection diagram of shunt DC generator is shown below.

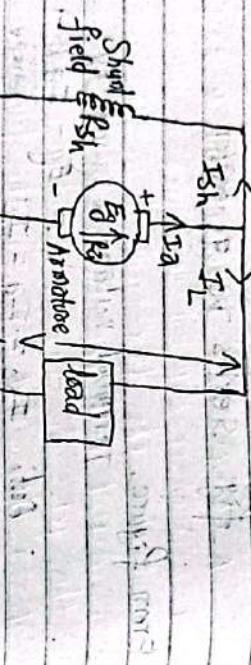


fig: Shunt DC generator

From circuit diagram,

$$I_{sh} (\text{shunt current}) = \frac{V}{R_{sh}}$$

Where, V = terminal voltage, R_{sh} = shunt field

terminal voltage (V) = $E_g - I_a R_a$. If the brush contact is included then V becomes as,

$$V = E_g - I_a R_a - \alpha V_b$$

developed power = $V I_a$

output power = $V I_L$

power, or range gap has a strong

(c) compound DC generator

A compound DC generator has two field windings; one is connected in series and another is connected in parallel with the armature windings. There are two types of compound DC generator.

(i) short shunt compound DC generator

(ii) long shunt compound DC generator

In short shunt compound DC generator, the short shunt winding is connected in parallel with the armature and series field winding is connected in series with the load as shown in figure below.

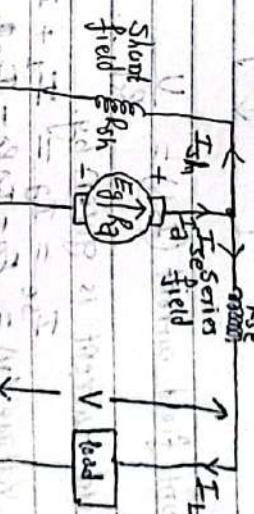


fig: Short shunt compound generator

from figure,

$$I_L = I_a e$$


$$I_{sh} = \frac{V + I_a R_{se}}{R_{sh}} = \frac{E_g - I_a R_a}{R_{sh}}$$

$$\text{Armature current } (I_a) = I_L + I_{sh}$$

$$\text{Terminal voltage } (V) = E_g - I_a R_a - I_{sh} R_{sh}$$

$$\text{If the brush contact drop is included then, } V = E_g - I_a R_a - I_{sh} R_{sh} - \alpha V_b$$

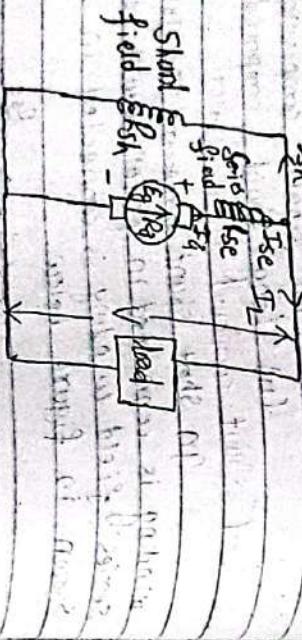(iii) Long Shunt compound DC generator: In long shunt compound DC generator, the shunt field winding is parallel with both armature and series field winding. The connection diagram of long shunt compound DC generator is shown below.



From figure,

$$\text{Shunt field current } (I_{sh}) = \frac{V}{R_h}$$

Series field current is given by

$$I_{se} = I_a = I_L + I_{sh}$$

$$\text{Terminal voltage } (V) = E_g - I_a R_a - I_{se} R_{se}$$

$$\therefore E_g - I_a R_a - I_{se} R_{se}$$

$$= E_g - I_a (R_a + R_{se})$$

If the brush contact drop is included then

$$V = E_g - I_a (R_a + R_{se}) - 2\eta_b$$

$$\text{developed power} = E_g I_a$$

$$\text{o/p power} = V I$$

1. Armature reaction: When a DC motor runs at no load, the air gap flux is uniform throughout the air gap. As the motor starts to rotate, the air gap flux becomes non-uniform due to the rotation of the armature. This causes a magnetic pull or reluctance force on the armature which tends to stop it. This effect is called armature reaction.

2. Brush contact drop: When a DC motor runs at no load, the brushes make good contact with the commutator segments. As the motor starts to rotate, the brushes move away from the commutator segments due to centrifugal force. This causes a voltage drop across the brush contact which is called brush contact drop.

3. Winding resistance: The windings of a DC motor have resistance. This causes a voltage drop across the windings which is called winding resistance.

EMF equation of DC machine:

The emf developed by a dc machine may be determined as follows:

Let us define the following symbols.

ϕ = magnetic flux per pole.

P = number of magnetic poles

N = speed of armature in rpm (rotation per minute)

Z = total number of armature conductors

A = Number of parallel paths in the armature winding.

Then,

Flux cut by one conductor in one rotation = ϕP

Flux cut by one conductor in N rotations = ϕNP

Flux cut per second by one conductor in N rotations = $\frac{\phi NP}{60}$

Number of conductors in series = Z/A

Flux cut per second by Z/A conductors = $\frac{\phi NP}{60} \times \frac{Z}{A}$

Hence, emf induced in the armature winding.

$$E = E_b = \frac{\phi NP}{60} \times \frac{Z}{A} = \frac{Z \phi N}{60} \times \frac{P}{A}$$

Torque equation of DC machine:

We know that, the generated electric power is equal to the generated mechanical power in DC machine like motor & rot generator.

$$\text{i.e. } E_b \cdot I_a = T_a \times 2\pi N$$

where,

$$\text{for rotating field } E_b = \text{back emf}, I_a = A \cdot C$$

$$T_a = \frac{P}{n} T \quad n = \text{speed in rpm}$$

possible, as a large gap has a

water turbines, steam turbines, internal

since, emf equation of d.c. machine is given by:

$$E_b = E = \frac{Z \phi N}{A} \times I_a$$

From eqn (i) & (ii), we get,

$$\frac{Z \phi N}{A} \times I_a = \frac{T_a}{J} \times 2\pi N$$


$$\text{or, } T_a = \frac{Z \phi N P X I_a}{60 \times A}$$

$$T_a = \frac{I_a}{60 \pi} \frac{Z \phi P}{A}$$

From this equation, we can say that

$T_a \propto \phi I_a$
i.e. Torque is directly proportional to the product
of armature current and magnetic flux per pole.

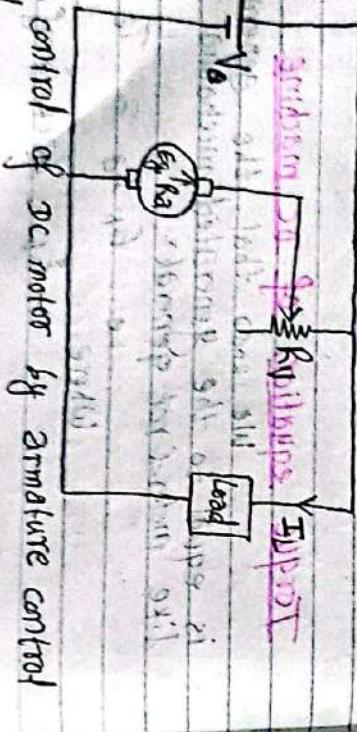Speed control of DC motor by armature control
method



We know,

No. E_b

So, when R_V is not connected then voltage drop
is less and back emf is larger and hence speed
is increased. i.e., when R_V is connected with armature
then there is more voltage drop and generated emf
is less and hence speed is decreased.

fig: Speed control of dc motor by armature control
method

possible, as a range goes on

The armature torque method depends upon magnetic flux per
and armature current.

i.e. torque $\propto \phi I_a$
If the variable resistance (R_V) is increased keeping the
load current constant then armature current remains
constant but potential difference across the armature will
decrease and hence speed of armature will decrease.
When R_V is zero then

$$E_b = V - I_a R_a \quad (\text{having } N_1 \text{ speed})$$

$$E_b = V - I_{a_2} R_a - I_{a_2} R_V$$

$$E_{b_2} = V - I_{a_2} (R_a + R_V) \quad (\text{having } N_2 \text{ speed})$$

Now, we know,

$$\frac{N_2}{N_1} = \frac{E_{b_2}}{E_b}$$

$$\left[\frac{N_2}{N_1} = \frac{V - I_{a_2} (R_a + R_V)}{V - I_{a_2} R_a} \right]$$

① Induction (asynchronous) motor

① Induction motor

Induction motor is also known as asynchronous motor.

Induction motor is an electric motor which operates from AC voltage source under the principle of electromagnetic induction. Stator windings of induction motor carry three-phase windings when three phase stator windings are supplied by three phase balanced voltage then three phase current will flow through stator windings. This three phase supply produces the rotating magnetic field. The synchronous speed (stator's speed) is given by-

$$N_s = \frac{120f}{P} \text{ rpm} \quad \text{or} \quad N_s = \frac{2f}{P} \text{ rps}$$

where,

N_s = synchronous speed

f = frequency of applied voltage

P = number of poles on stator

The rotor always rotates at the speed less than the synchronous speed.

i.e. $N_r < N_s$

We know the slip of the motor is

$$\text{Slip} = s = \frac{N_s - N_r}{N_s}$$

Induction motor is a three phase motor having three windings on the stator.

Three phases of the motor are connected to three phase power supply.

Three phases of the motor are connected to three phase power supply.


possible, as a large gap has a wider air gap, seems to be

wider air gap, seems to be

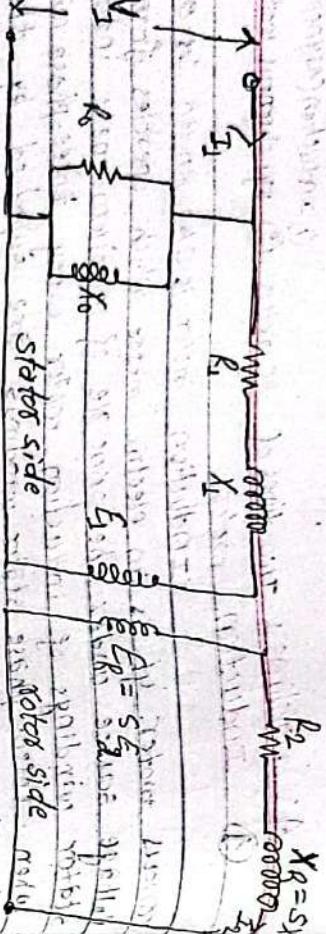(2)

Synchronous motor:

Synchronous motor operates on synchronous (constant) speed, hence this motor develops a constant torque in the direction of rotation.



The difference between the stator (synchronous) speed and rotor speed is simply called the slip of the motor.

3- ϕ induction motors are mostly used for various industrial applications because of their following advantages:

- They have an easy to construct the motor system.
- They are very reliable and having low cost.
- They have high efficiency and good power factor.
- Starting motor or any special starting arrangement is not required.
- Such motors are easier for maintenance.

Synchronous motors are not self-starting. such motors require some external trigger signal and bring their speed close to the synchronous speed. The speed of operation of is in synchronized synchronism with the supply frequency and hence for constant supply frequency they behave as constant speed motor. It is capable of being operated under a wide range of power factors both lagging and leading.

Synchronous motor having no load connected to its shaft is used for power factor improvement. Synchronous motor finds application where operating speed is less than (around 500 rpm) and high power is required.

① Applications of 1-Φ synchronous motor ② Differences between synchronous & induction motor

Winding :

Windings are wires that are laid in coils, usually wrapped around a laminated soft iron magnetic core so as to form magnetic poles when energized with current.

Some motors have conductors which consist of thicker metal, such as bars or sheets of metal, usually copper, although sometimes aluminum is used. These are usually powered by electromagnetic induction.

Commutator:

A commutator is a mechanism used to switch the input of certain AC and DC machines consisting of slip ring segments insulated from each other and from the electric motor's shaft.

Types of DC generators :

Energy can be converted from one form to other form.

A generator does the same - It converts mechanical energy to electrical energy. Mechanical energy can be created by using water turbines, steam turbines, internal combustion engines, wind turbines etc.


combustion engines etc. And a generator converts this mechanical energy broadly classified as ~~AC~~ generators and DC generators.

DC generators are classified based on their method of excitation. So on this basis there are two types of DC generators:

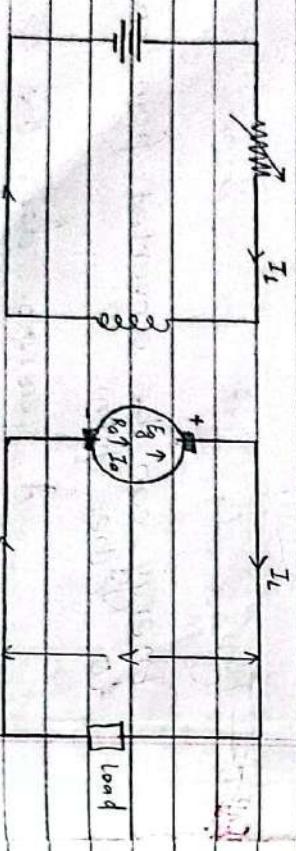(1) Separately Excited DC Generator:

As we can guess from the name itself, this DC generator has a field magnet winding which is excited using a separate voltage source (like battery). The output voltage depends on the speed of rotation of armature and field current. The higher the speed of rotation and current, the higher is the output emf.

Note: Separately excited DC generators are rarely used in practice.



These are generators in which the field winding is excited by the output of the flux generator itself. self excited DC generator can again be classified as:

- (a) Series DC generator
- (b) Shunt DC generator
- (c) Compound DC generator

(a) Series DC Generator:

A series DC generator is shown below in figure ~~fig 2~~ in which the armature winding is connected in series with the field winding so that the field current flows through the load as well as the field winding.

Field winding is a low resistance, thick wire of few turns. Series generators are also rarely used.

$$\text{Amature current, } I_a = I_s = I_A = I_{\text{load}}$$

$$\text{Terminal voltage, } V = E_g - I_s R_a$$

$$\begin{aligned} \text{Amature current, } I_a &= I_s \\ \text{Terminal voltage, } V &= E_g - I_s R_a \\ \text{Electric power developed} &= E_g I_s \\ &= I_s^2 R_a \\ &= I_a^2 R_a \\ &= V I_a \end{aligned}$$

Power developed in armature = $E_g I_a$

Power delivered to load = $E_g I_a - I_a^2 (R_a + R_{se})$

$$= I_a [E_g - I_a (R_a + R_{se})]$$

$$= VI_a \text{ or } VI_L$$

R_{se}
arm
 I_a

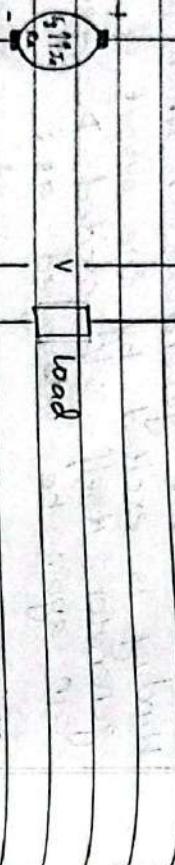


fig : Series DC generator

(b) Shunt DC Generator:

A shunt DC generator is shown in figure below, in which the field winding is parallel to armature winding so that the voltage across both are same.

The field winding has high resistance and more number of turns so that only a part of armature current passes through field winding and the rest passes through load.

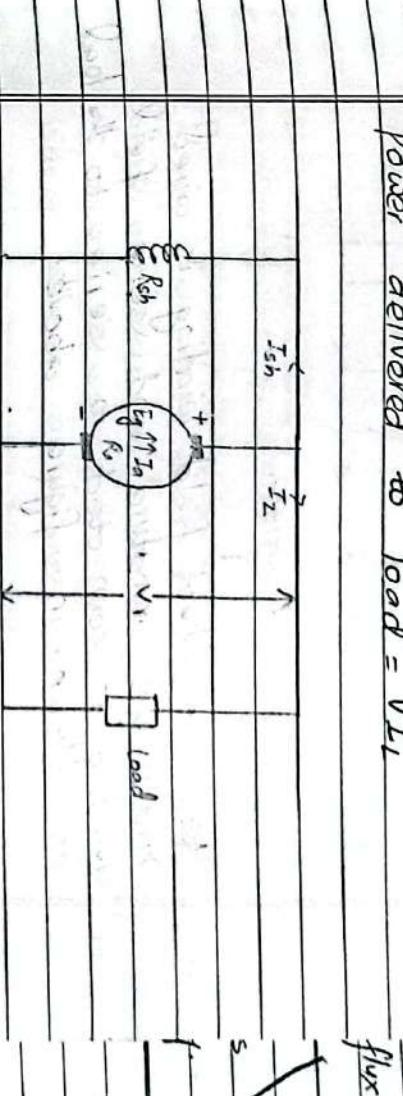


fig : Shunt DC generator

(c) Compound DC Generator:

A compound DC generator is shown below. It has two field windings namely R_{sh} and R_{se} . They are basically shunt winding (R_{sh}) and series winding (R_{se}).

Compound generators are of following two types.

Shunt field current, $I_{sh} = \frac{V}{R_{sh}}$

Armature current, $I_a = I_L + I_{sh}$

Terminal voltage, $V = E_g - I_a R_a$

Power developed in armature = $E_g I_a$

Power delivered to load = VI_L

(i) Short shunt:

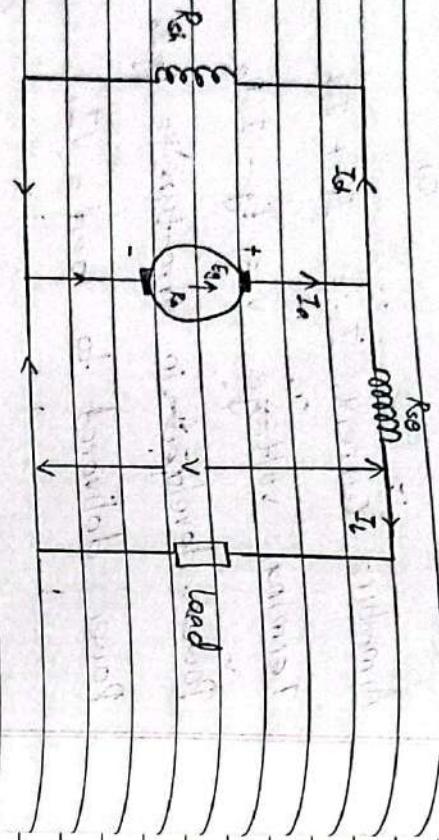


fig: short shunt.

Here, the shunt field winding is wired parallel to armature and series field winding is connected in series to the load as shown in figure above.

for short shunt :

$$\text{Series field current, } I_{se} = I_a$$

$$\text{Shunt field current, } I_{sh} = \frac{V}{R_{sh}} + I_{se} R_{se}$$

$$\text{Terminal voltage, } V = E_g - I_a R_a - I_{se} R_{se}$$

$$\text{Power developed in armature} = E_g I_a$$

$$\text{Power delivered to load} = VI_L$$

(ii) Long shunt:

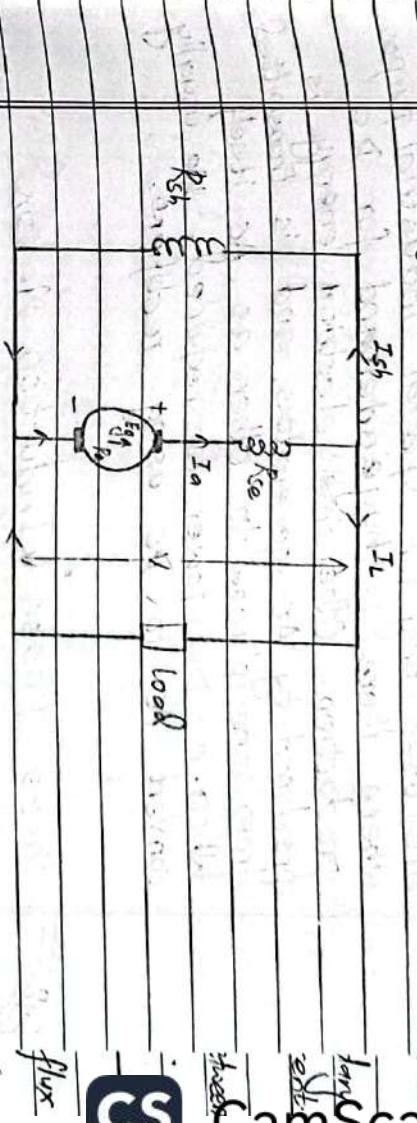


fig: long shunt.

Here, the shunt field winding is parallel to both armature and series field winding (R_{se} is wired in series to the armature). It is shown above.

for long shunt,

$$\text{Series field current, } I_{se} = I_a$$

$$\text{Shunt field current, } I_{sh} = \frac{V}{R_{sh}}$$

$$\text{Terminal voltage, } V = E_g - I_a (R_a + R_{se})$$

$$\text{Power developed in armature} = E_g I_a$$

$$\text{Power delivered to load} = VI_L$$

Now, we can say that these generators are used only for special industrial purposes where there is huge demand for DC production. Otherwise electrical energy is produced by AC generators and is transmitted from one place to other as AC itself. When a DC power is required, we usually convert AC to DC using rectifiers.

Three Phase Induction Motor:

An electric motor is such an electromechanical device which converts electrical energy into a mechanical energy.

In case of three phase AC operation, most widely used motor is Three phase induction motor as this type of motor does not require any starting device or we can say they are self starting induction motor.

The basic constructional feature of this motor consist of two major parts:

① Stator:

Stator of the three phase induction motor is made up of numbers of slots to construct a 3 phase winding circuit which is connected to 3 phase AC source.

The three phase windings are arranged in such a manner in the slots that they produce a rotating

magnetic field after AC is given to them. The stator of the motor consists of overlapping windings offset by an electrical angle of 120° . When the primary winding or the stator is connected to a 3-phase AC source, it establishes a rotating magnetic field which rotates at the synchronous speed.

② Rotor:

Rotor of three phase induction motor consists of cylindrical laminated core with parallel slots that can carry conductors. Conductors are heavy copper or aluminum bars which fits in each slots & they are short circuited by the end rings.

The number of magnetic poles of the revolving field will be same as the number of poles for which each phase of primary or stator winding is wound or wrapped. The speed at which the field produced by the primary current will revolve is called synchronous speed of motor and is given by:

$$N_s = 120 \times \frac{f}{P}$$

where N_s is the synchronous speed
 f is the frequency
 P is the no. of poles on stator.

Synchronous Motor:

The difference between the stator (synchronous speed) and rotor speeds is called the slip. The rotation of the magnetic field of an induction motor has the advantage that no electrical connections need to be made to the rotor.

Thus, the Three phase Induction Motor is:

- * Self-starting
- Robust in construction
- Economical
- Easier to maintain

It is electrically identical with an alternator or Ac generator. It runs either at synchronous speed or not at all ie while running it maintains constant speed. It is capable of being operated under a wide range of power factors both lagging and leading. It can be used for power correction purpose in addition to supplying torque to drive loads.

Uses of 1-Φ Synchronous Motor:

(1) They are small, constant speed motors.

(2) Built for the wide range of output and speed.

(3) Its power is on the range of 0.001 kw and are used in clocks, control apparatus timing devices etc.

Emf equation of dc machine:

Let us define,

ϕ → magnetic flux per pole

P → No. of magnetic pole

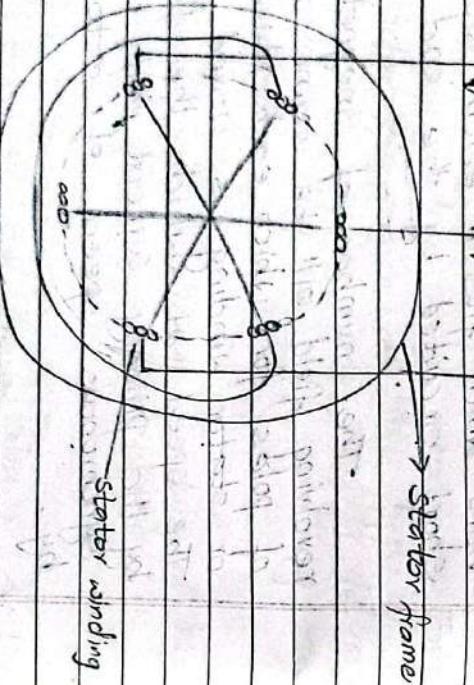


fig: 3-Φ induction motor

$Z \rightarrow$ Total no. of armature conductors
 $N \rightarrow$ speed of armature rpm (rotation per minute)

Now,

Average emf generated per conductor = $\frac{d\phi}{dt} \times \frac{\text{temp}}{A}$

The Magnetic flux cut by each conductor in one revolution = $\phi \times P$
 Time for one revolution (dt) = $\frac{60}{N}$

Let, A be the number of parallel paths in armature winding then number of conductor in series is = Z

\therefore Average emf generated per pole = $\frac{d\phi}{dt}$

Since, emf equation of dc machine is given by:

$$\bar{E}_b = E = \frac{Z \phi N}{60} \times \frac{P}{A} \text{ rpm} \quad \text{--- (ii)}$$

$$= \frac{\phi \times P \times N}{60} \times \frac{Z}{A}$$

Now,

total emf \bar{E} = Average emf \times no. of conductor in series

$$E = \frac{Z \phi N}{60} \times \frac{P}{A}$$

$$E = \frac{Z \phi N}{60} \times \frac{P}{A}$$

Note: $A = P$ for lap winding
 $A = 2$ for wave winding

Torque equation of dc machine:

We know in electric field,

Electric power generated = Mechanical power developed i.e.

$$\bar{E}_b I_a = T_a \times 2\pi N \quad \text{--- (i)}$$

Where,
 $\bar{E}_b \rightarrow$ back emf or generated emf (E_g)

$I_a \rightarrow$ Armature current

$T_a \rightarrow$ Torque
 $N \rightarrow$ Speed in rpm

$$a. \frac{2\phi N P I_a}{60 \times A} \times \frac{1}{2\pi N} = T_a$$

$$or, T_a = \frac{2\phi N P I_a}{120 \pi \times A}$$

$$\boxed{T_a = \frac{I_a \times 2\phi I_a P}{120 \pi A}}$$

From this eqn we can say that:

$$T_a \propto \phi I_a$$

i.e Torque is directly proportional to the product of armature current and magnetic flux per pole.

Speed control of DC motor by armature control method:

Now, we have :

$$\boxed{E_b = \frac{N_a}{R_a} I_a}$$

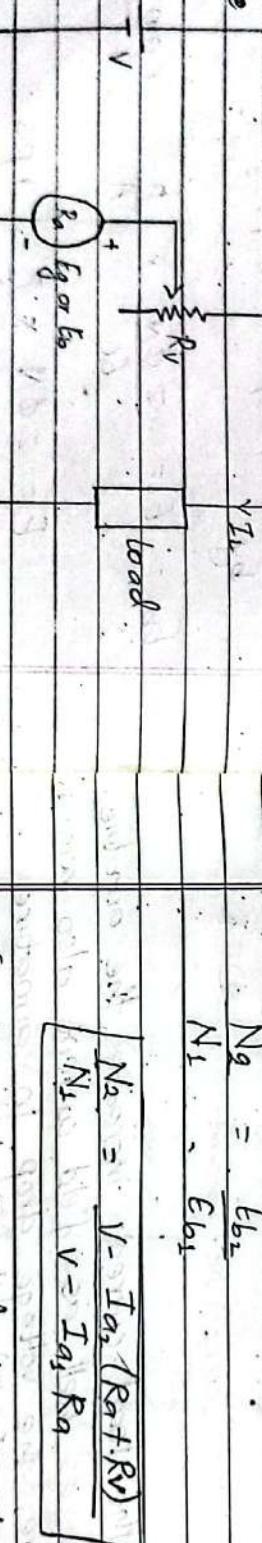


fig: speed control of d.c motor by armature control method

The armature torque method depends upon magnetic flux per pole and armature current.

i.e torque $\propto \phi I_a$

If the controller resistance or variable resistance (R_v) is increased keeping the load torque constant, the armature current remains constant but potential difference across the armature will decrease. Hence speed of armature will decrease.

let, N_L be the speed of motor at flux $R_v = \text{constant} > 0$

Then, back or generated emf is given by

$$E_{b1} = V - I_a (R_a + R_v)$$

$$E_{b2} = V - I_a (R_a + R_v)$$

Now, we have :

$$\boxed{\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}}$$

$$\boxed{\frac{N_2}{N_1} = \frac{V - I_a (R_a + R_v)}{V - I_a (R_a + R_v)}}$$

If $R_v = 0$, speed is maximum (full load)

If $R_v = \infty$, speed is minimum (no load)

Characteristics of DC Generators:

(A) Load characteristics:

(i) Series DC generator:

Let us consider a series DC generator as shown in figure below in which the armature winding is connected in series with field winding so that same field current flows through the load as well as the field winding.

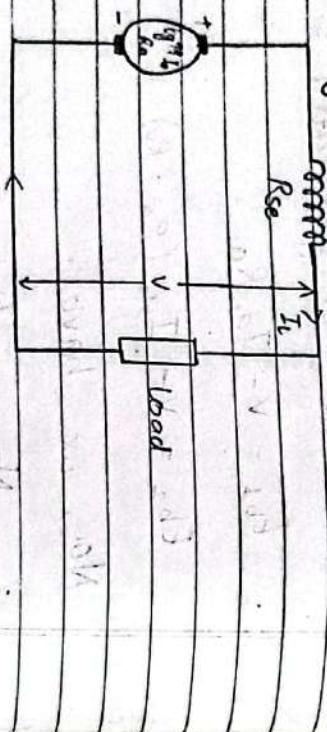


Fig: series DC generator

When the load current increases, the armature current as well as field current also increases. Therefore, the voltage drop in armature resistance ($I_a R_a$) will also increase and other hand the flux per pole also increase. Therefore, the emf will also increases.

Hence, a series DC generator have a raising voltage characteristics as shown in figure below:



Fig: Load characteristics

"But at over loaded condition, the voltage starts decreasing due to excessive demagnetizing effect of armature reaction and saturation flux effect."

(ii) Shunt DC generator:

Let us consider a shunt DC generator as shown in figure below in which the field winding is connected in parallel to armature winding so that the voltage across both are same.

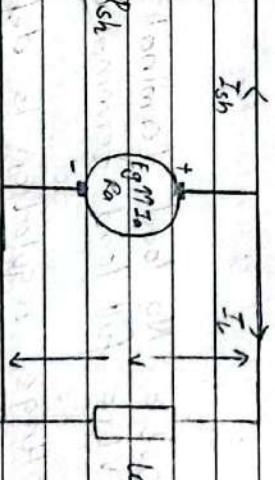


Fig: shunt DC generator

When there is no load current, the armature current (I_a) is equal to the field

current (I_{sh}) i.e $I_a = I_{sh}$. Since, load current (I_L) is equal to zero,

which is very small current with compare to full load current. Therefore, the voltage drop in armature is very small. Hence, the terminal voltage V is nearly equal to E_g .

When the generator is loaded then the armature current ($I_a = I_{sh} + I_L$) will increase. Now, the terminal voltage is given by:

$$V = E_g - I_a R_a$$

Therefore, the terminal voltage V will decrease with increase in load current (I_L) as shown in figure below:



Compound DC Generator:

We have seen that, a series DC generator has a raising voltage characteristics and a shunt DC generator has a dropping voltage characteristics. A compound DC generator has a characteristics lying between shunt and series DC generator. A shunt DC generator can be modified into a compound generator to supply constant voltage by adding few times flux of field winding in series with load or armature. as show below:

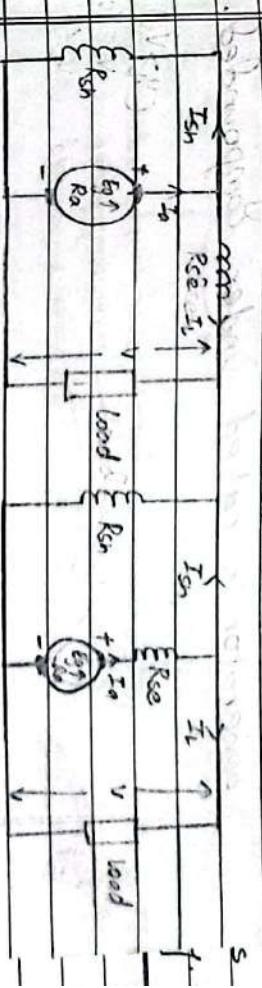


fig: short shunt
(field winding series with load)

fig: long shunt
(field winding series with armature)

Let, OVL = No load terminal voltage
 FVL = full load terminal voltage
Then, voltage regulation is defined as follow:

$$\text{Voltage regulation} = \frac{OVL - FVL}{OVL} \times 100\%$$

As the load current increases, the current through the series field winding also increases thereby increasing flux per pole. Due to increase in flux per pole, the emf also increases.


Hence, shunt DC generator have a dropping voltage characteristics.

By adjusting the number of series turn the terminal voltage ' V ' can be controlled in different ways.

If the series field 'ampere' turns are such that the voltage at rated load and no load voltage are same, then the generator is called flat compounded.

If the series field 'ampere' turns are such that the voltage at rated load is greater than no load voltage then the generator is called over compounded.

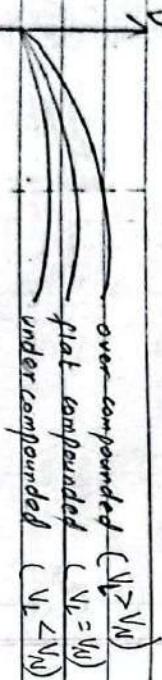If the series field 'ampere' turns are such that the voltage at rated load is less than the no load voltage then the generator is called under compounded.



$$I_f \propto \frac{1}{V}$$

(b) No-load characteristics:

It is a curve showing the values of emf generated across the armature at different no load for different values of field current at constant speed.

The 'load characteristics' of separately excited shunt and series generator can be partially obtained in a similar way. The circuit arrangement for

obtaining the data for no load characteristic is shown below:

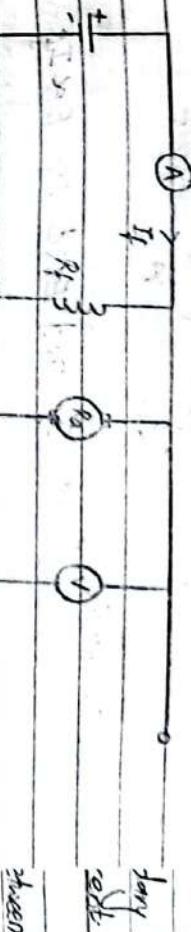


fig: open circuit curve

In case of shunt and series generator, the field windings has to be disconnected temporarily and connected them as shown above.

The armature of the generator is rotated at constant speed by prime mover and emf induced across the armature at different value of field current are measured. The resulting curve as shown in fig. where OA is the emf generated across the armature due to residual flux in the pole even in absence of field current.

rotated at constant speed by prime mover and emf induced across the armature at different value of field current are measured. The resulting curve as shown in fig. where OA is the emf generated across the armature due to residual flux in the pole even in absence of field current.

"We know that:"

$$t = \frac{2\phi N}{60} \times \frac{P}{n} \text{ volt}$$

we know,

$\phi \propto I_f$ and $E \propto \phi$ so $E \propto I_f$


Since, armature current is driven at constant speed, $E \propto \phi$ At constant speed we can write

$$t \propto I_f$$

Therefore, the no-load characteristic curve is a straight line indicating that the emf increases proportionally with I_f up to point B. After point B the magnetic poles get saturated and emf does not increases even if the I_f is increased.

Note:

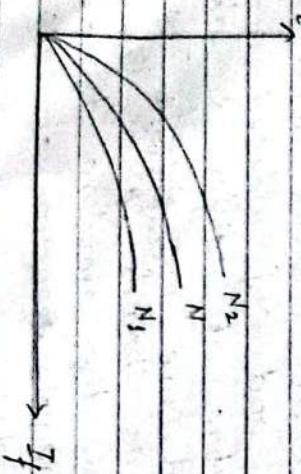No-load characteristic curve for higher speed will be above this curve and for the lower speed it will be below this can shown as:



$N_0 > N > N_1$

We know that, torque equation of DC machine is, $T_a \propto \phi \cdot I_a$

$$\text{And, } \phi \propto I_f$$

In a dc shunt motor the field current is constant provided that the applied voltage is constant.

$$\therefore T_a \propto I_a$$

Hence, $T_a - I_a$ characteristics of DC shunt motor is a straight line which indicate that the armature torque increases proportionally with the armature current. The net shaft torque is always less than the armature torque because of loss of torque due to friction loss.

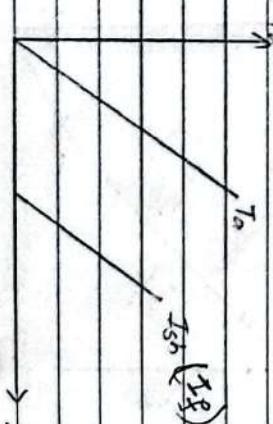


fig: $T_a - I_a$ characteristics

(ii) speed Torque characteristics:

It is a curve showing the speed of the motor at different values of armature torque developed by the motor.

We know that,

$$N \propto \frac{E_b}{\phi}$$

where, N is speed of DC shunt motor and ϕ is constant for DC shunt motor.

When the speed of motor decreases the back emf E_b will also decrease.

Then, Amature current ($I_a = V - E_b/R_g$)

will increase as the armature torque (T_a) will also increase but the speed of

motor is inversely proportional to the torque of the motor.

Hence, $N - T_a$ characteristics of DC

shunt motor will be as follows:

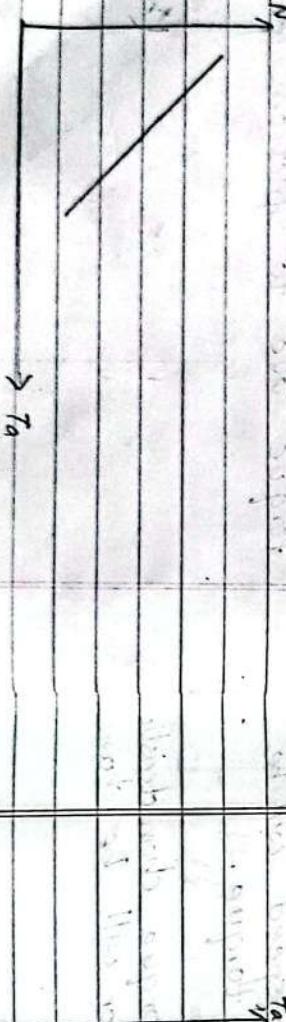


fig : $N - T_a$ characteristics

Characteristics of DC series motor:

(i) Torque - Amature current characteristics:

In a DC series motor, the armature winding and field winding are connected in series. Therefore, the flux per pole is not constant but it varies with the armature current.

We know that,

$$T_a \propto \phi I_a$$

$$I_a \propto T_a^2$$

Hence, $T_a - I_a$ (Torque - Amature current) characteristic of DC series motor is parabolic as shown in figure below.

After saturation the flux per pole is almost independent of I_a and hence T_a & I_a only. Therefore, the characteristic becomes a straight line after saturation.

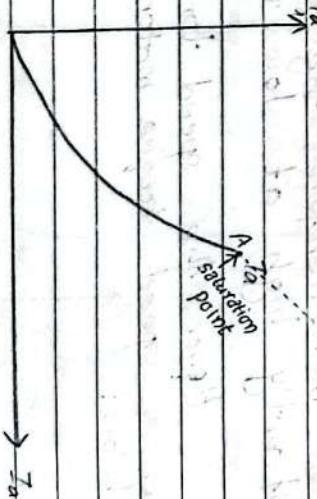


fig : $T_a - I_a$ characteristic

(ii) Speed-Torque characteristics:

We know that :

$$N \propto \frac{E_b}{\phi}$$


$$\text{Ind, } E_b = V - I_a R_a$$

$$\text{and, } T_a \propto \phi I_a$$

At heavy load (ie at high I_a), the armature current is high. Therefore, the back emf E_b will reduce to allow high armature current. But flux per pole (ϕ) is proportional to series I_a in series motor. Hence, the speed will be significantly low at high torque.

At no load (ie at low I_a), the armature current is low. Therefore, the back emf E_b will be comparatively high to allow low armature current. Since the armature current is low the flux per pole will be low. Therefore, the speed will be significantly high at low torque.

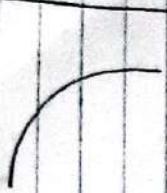Hence, the speed torque characteristic of series speed torque motor will be shown as below:



- # Difference between Generator & Motor:
- | Generator | Motor |
|--|---|
| (1) It converts mechanical energy into electrical energy. | (1) It converts electrical energy into mechanical energy. |
| (2) It generates an emf or voltage when conductor (or moving coils) are moved in a magnetic field. | (2) It develops a twisting effort or torque when a current is passed across the moving coil held in a magnetic field. |
| (3) It is generally employed to get a variable dc voltage. | (3) It is usually employed at a place where wide range of speed control is required. |

From this characteristics it is clear that at the starting where the speed is very low, DC series motor develops a high torque. On the other hand at no load the speed will be very high. Hence a DC series motor should not be started at no load otherwise it may develop excess speed and mechanical failure may occur due to heavy centrifugal force.

Armature Reaction:

The interaction between the flux produced by the field windings and by the current carrying armature windings is known as armature reaction.

It is a term used to describe the effect of armature magnetomotive force (mmf) on the operation of dc machine. It affects both the flux distribution and flux magnitude in the machine.

In generator, the effect of armature reaction is to twist or distort the flux in the direction of rotation, whereas in the case of motors it shifts the magnetic neutral plane backwards opposing the direction of rotation.

$$\text{Voltage Regulation/Regulation} = \frac{I_{sc} R_{sc} \cos \alpha + I_s X_{sc} \sin \theta}{E_2}$$

for lag react. rest.

$$R_{sc} = \frac{V_{sc}}{I_{sc}} = \frac{360}{10.5} = 34 \Omega$$

flux

$$Z_{sc} = \frac{V_{sc}}{I_{sc}} = \frac{86}{10.5} = 8.1 \Omega$$

$$X_{sc} = \sqrt{Z_{sc}^2 - R_{sc}^2} = \sqrt{8.1^2 - 34^2} = 32.5 \Omega$$

$$\therefore V.R = 10.5 \times R_{sc} \times 0.8 + 10.5 \times X_{sc} \times \sin(90^\circ)$$

$$= 220$$

η = Output power
 input Power
 = Output power
 Output power + copper loss + iron loss

$$\text{For Full load } \lambda = 1$$

$$\text{" Half load } \lambda = \frac{1}{2}$$

$$P_c \rightarrow \text{Copper Loss} = \text{Short circuit power} = 360 \text{ W}$$

$$P_i \rightarrow \text{iron loss} = \text{Open circuit power} = 148 \text{ W}$$

Transformer

- (1) BCD → R.M.S. → Q. Answ. —
 - Digital logic system. — 1st sem
 - Microprocessor — 2nd sem

- (2) BE (Computer) — 1st sem — Dr. Gopal. (1)
 - BEC — 3rd sem — " "
 - New theory: — " → Q. Answ. (2)
 - Material — " — " (3)
 - IOT circuit — " → " (4)
 - Electronic Device Lab. — " (5)

- (3) BE (Computer) — 5th sem — KAM SIR.
 - MSI — 7th sem. — Cr. (6)

- (4) BCD → R.M.S. → Q. Answ. —
 - DSP — " "
 . BE Civil. — 1st sem. — Dr. Gopal. (7)

Induction Machine

- (1) It is stationary (1)
 - Primary and secondary frequencies are same. (2)

- (2) It does not have any air gap between primary & secondary. (3)
 - There is air gap between rotor and stator. (4)

- (3) Magnetic flux is not rotating. (5)
 - Rotating magnetic flux (φ) is induced. (6)

- (4) Energy received is electrical energy. (7)
 - Energy received is mechanical energy. (8)

Active Elements: those which have Active elements are those which have their own energy and they transfer energy to the passive elements.

Eg: voltage, current

Passive Elements: those which don't have their own energy and they receive energy from active elements.

Eg: Resistor, capacitor

